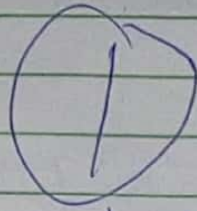


NAME: ROTIMI ESTHER ARAMIDE
MATIC NO: 15/FY604/053
COURSE CODE: EE554



a Contingency planning deals with the identification of actions to be taken for the supply-demand equation to be balanced.

b methods of voltage control

- Regulating transformers
- Reactive power sinks or sources
- Excitation control
- Line reactance compensators

The

c \rightarrow Steady stability limit of a power system is the maximum power that can be transmitted to the receiving end without loss of synchronism.

d methods of improving transient stability

- Use of High Speed circuit breaker
- Increasing the system voltage

e
$$P_{max} = \frac{E_0}{X}$$

$$P_e = P_{max} \sin \delta$$




Prefault condition

$$X_1 = j \left[0.28 + \frac{0.16 + 0.24 + 0.16 + 0.16}{2} \right]$$
$$= 0.72 \mu$$

$$P_{max1} = \frac{1.25 \times 1}{0.72} = 1.736$$

$$P_e = 1.736 \sin \delta$$

During fault -

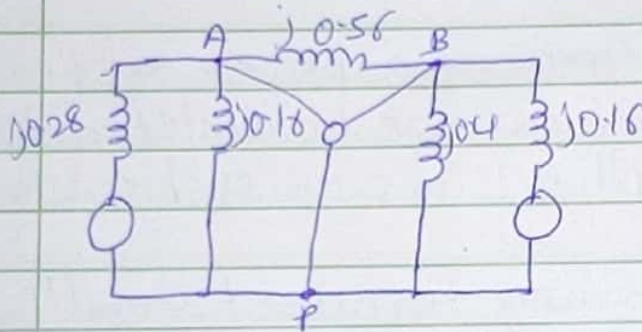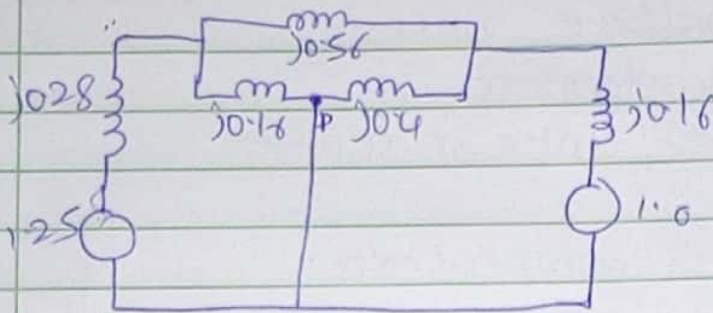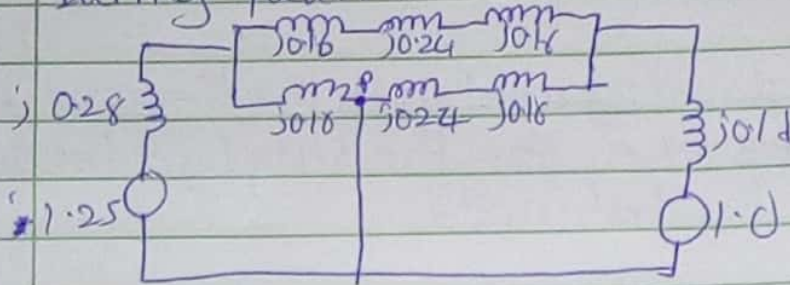



Converting Δ to Y

$$X_{AP} = j \left[\frac{0.56 \times 0.16}{0.56 + 0.16 + 0.4} \right] = j0.08$$

$$X_{BP} = j \left[\frac{0.56 \times 0.4}{0.56 + 0.16 + 0.4} \right] = j0.2$$
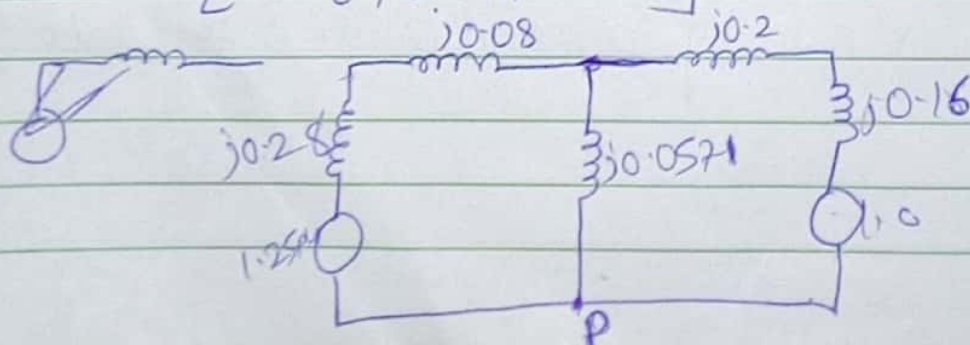
$$X_{BP} = j \left[\frac{0.16 \times 0.4}{0.56 + 0.16 + 0.4} \right] = j0.0571$$



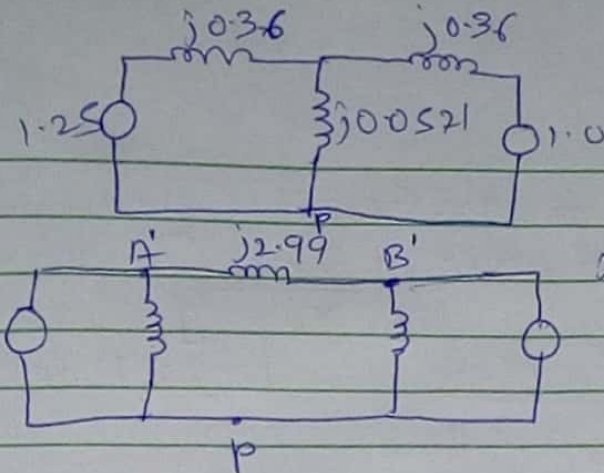

Converting $\gamma - \Delta$

$$X'_{AB} = \frac{0.36 \times 0.0571 + 0.36 \times 0.36}{0.0571} = j2.99$$

$$x_2 = j2.99$$

$$P_{max2} = \frac{1.25 \times 1}{2.99} = 0.418$$


$$P_{e2} = 0.418 \sin \delta$$

During post fault.

$$x_3 = j0.28 + j0.16 + j0.24 + j0.16 + j0.16 = 1$$

$$P_{max3} = \frac{1.25 \times 1}{1} = 1.25 \text{ pu}$$

$$P_{e3} = 1.25 \sin \delta$$

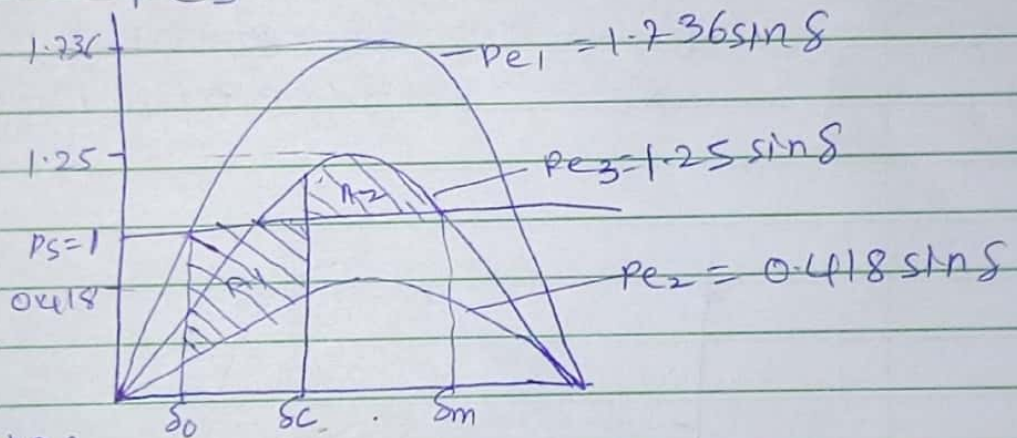

(17) Using

$$\cos \delta_c = \frac{(\delta_m - \delta_0) \sin \delta_0 - \gamma_1 \cos \delta_0 + \gamma_2 \cos \delta_m}{\gamma_2 - \gamma_1}$$

$$\gamma_1 = \frac{P_{max2}}{P_{max1}} = \frac{0.418}{1.736} = 0.241 \text{ pu}$$

$$\gamma_2 = \frac{P_{max3}}{P_{max1}} = \frac{1.25}{1.736} = 0.720 \text{ pu}$$

$$\text{Initial load angle } \delta_0 = \sin^{-1} \frac{P_s}{P_{max1}} = \sin^{-1} \frac{1}{1.736}$$

-35.17° or 0.614 rad (electrical)

$$\text{load angle } \delta_m = 180 - \sin^{-1} \left[\frac{\sin \delta_0}{\gamma_2} \right] = 180 - \sin^{-1} \left[\frac{\sin(35.17)}{0.720} \right]$$

$$= 180 - \sin^{-1} \left[\frac{0.5760}{0.720} \right] = 126.87^\circ \text{ or } 2.214 \text{ rad (electrical)}$$

$$\cos \delta_c = \frac{(2.214 - 0.614) \times \sin(0.614) - 0.214 \times \cos(0.614) + 0.720 \times \cos(2.214)}{0.720 - 0.241}$$

$$\cos \delta_c = \frac{0.9216 - 0.197 - 0.432}{0.720 - 0.241}$$

$$\cos \delta_c = 0.6109$$

$$\delta_c = \cos^{-1}(0.6109)$$


$$\delta_c = 52.35 \text{ electrical degrees}$$

2

f classification of power system stability

- steady state
- dynamic
- transient

g

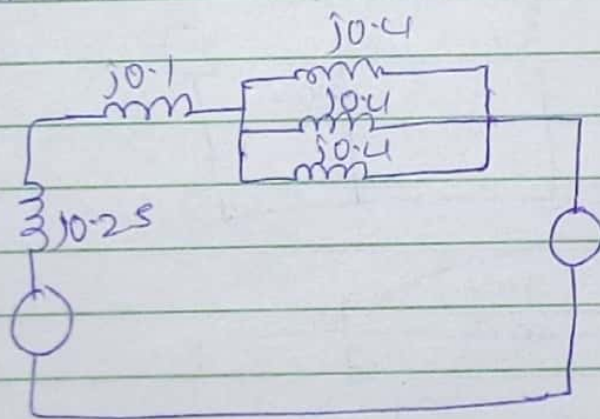

$$V_t = |V_t| \angle \alpha = 1 \angle \alpha$$

$$P_e = \frac{V_t |V| \sin \alpha}{X} = 1$$

$$\frac{1 \times 1}{0.25 + 0.1} \sin \alpha = 1$$

$$\sin \alpha = 0.25 + 0.1$$

$$\sin \alpha = 0.35$$

$$\alpha = \sin^{-1} 0.35 = 20.5^\circ$$

The current flowing into the infinite bus is given as:

$$I = \frac{V_f \angle \alpha - |V| \angle 0}{X}$$

$$I = \frac{1 \angle 20.5 - 1 \angle 0}{j0.35}$$

$$= -1 + j0.18$$

$$= 1.017 \angle 10.25^\circ$$

EMF behind the transient reactance is given as



$$E' = |V| \angle 0 + I X$$

$$X_a = j0.25 + j0.1 + \frac{j0.4}{3} = j0.483$$

$$E' = 1 \angle 0 + (1 + j0.18) j0.483$$

$$E' = 0.913 + j0.483 = 1.033 \angle 27.878^\circ$$

(ii) When one line is shorted

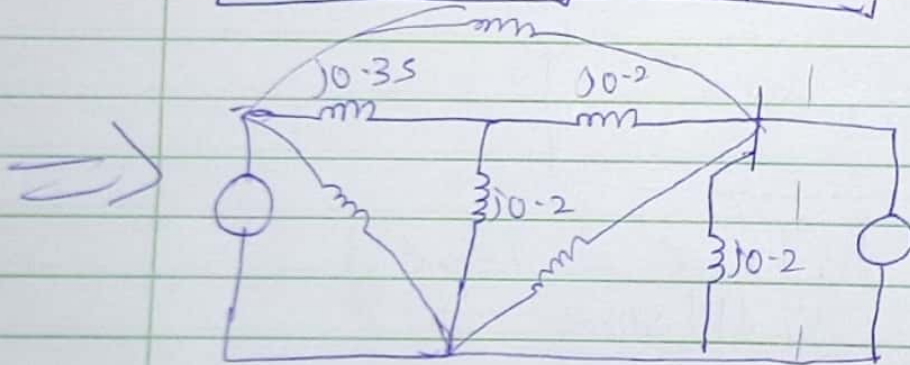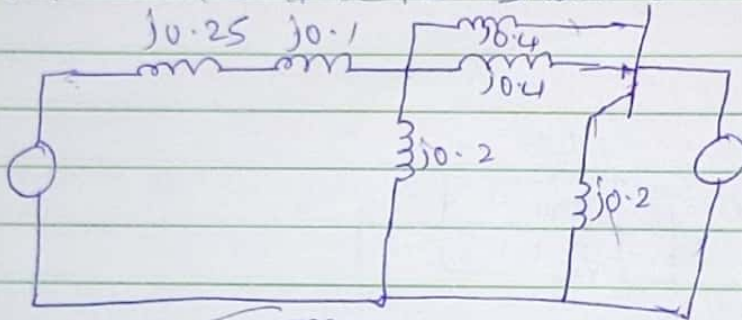

Converting $Y \rightarrow \Delta$

$$x_b = \frac{0.35 \times 0.2 + 0.2 \times 0.2 + 0.35 \times 0.2}{0.2}$$

$$= 0.9$$

$$P_{max} = \frac{|V| |E|}{x_b}$$

$$P_{max} = \frac{1 \times 1.033}{0.9}$$

$$P_{max} = 1.148 \text{ pu}$$