


Iwatt Erobong udo
181 Eng 04/080

Electrical / Electronics

EEE 322 : Circuit theory.

Assignment

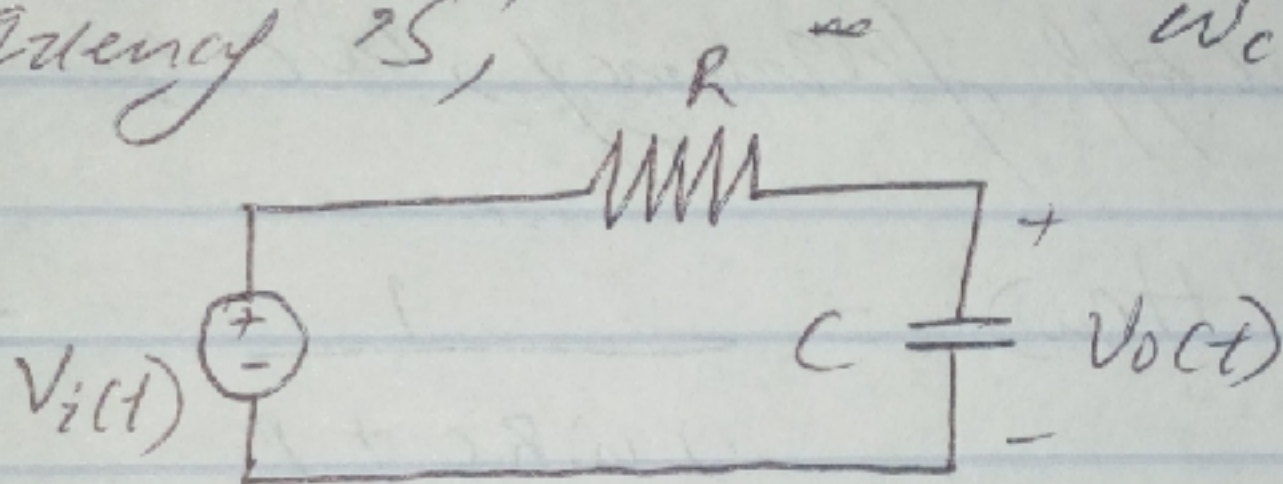Determine the type of filter shown below, & show that its cut-off frequency is; $\omega_c = 1/RC$



$$Z_f = \frac{1}{j\omega C}$$

$$V_o = \frac{1}{j\omega C}, \quad V_i = R + \frac{1}{j\omega C}$$

$$H(\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_i} = \left[\frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right] V_i$$

$$= \frac{1}{j\omega C} \times R + \frac{1}{j\omega C}$$

$$= \frac{1}{j\omega RC + 1}$$

when $(H\omega) = 0$, $H = 1$

when $(\omega) = \infty$, $H = 0$

\therefore Cut off frequency, ω_c ;

$$|H(\omega)| = \frac{1}{|j\omega RC + 1|} = \frac{1}{\sqrt{2}}$$

(ω_c is the magnitude of $H(\omega)$ to $\frac{1}{\sqrt{2}}$)

$$\Rightarrow = \frac{\sqrt{1^2}}{\sqrt{1^2 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega^2 R^2 C^2)}}$$

$$= \frac{1}{\sqrt{2}}$$

$$\Rightarrow 2 = 1 + \omega^2 R^2 C^2$$

Squaring both sides.

$$2 = 1 + \omega^2 R^2 C^2$$

$$2-1 = \omega^2 R^2 C^2$$

$$1 = \omega^2 R^2 C^2$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \omega_c$$

$$\Rightarrow \omega_c = \frac{1}{RC}$$

It is a low pass filter &
it's an RLC circuit.

$$\begin{aligned} \omega_c &= 2 \\ \omega &= \frac{2}{5} \end{aligned}$$

$$\omega_c = \frac{1}{RC}$$