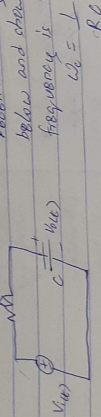


Name: Manvika Chakraborty  
 Roll no: 17EE004102  
 Department: Electrical/Electronics Engineering

EEE 322

Determine the type of filter shown below and state that its cut-off frequency is



$\omega_c = \frac{1}{RC}$

Sol  
 Converting to frequency domain

$R \rightarrow R$

$C \rightarrow \frac{1}{j\omega C}$

$H(\omega) = \frac{V_o}{V_i}$

Using Kirchhoff voltage law (series connection)

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega RC}{R + j\omega RC} = \frac{j\omega RC}{R(1 + j\omega RC)}$$

$H(\omega) = 1$

$\frac{1}{1 + j\omega RC}$

when  $H(\omega) = 1$ ,  $H(\omega) = 0$

The half power frequency which is equivalent to the corner frequency in the Bode plots but in the context of filters is usually known as cut-off frequency  $\omega_c$ , is obtained by setting magnitude of  $H(\omega)$  equal to  $\frac{1}{\sqrt{2}}$

Substituting  $\omega_c$

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

making  $\omega_0$  subject of formula

Taking square of both sides

$$\frac{1}{1 + \omega_0^2 R^2 C^2} = \frac{1}{2}$$

Cross multiply

$$2 \times 1^2 = 1 + \omega_0^2 R^2 C^2$$

$$2 = 1 + \omega_0^2 R^2 C^2$$

$$2 - 1 = \omega_0^2 R^2 C^2$$

$$1 = \omega_0^2 R^2 C^2$$

Taking square root of both sides

$$\sqrt{1} = \sqrt{\omega_0^2 R^2 C^2}$$

$$1 = \omega_0 R C$$

Divide both sides by  $RC$

$$\omega_0 = \frac{1}{RC}$$

✓