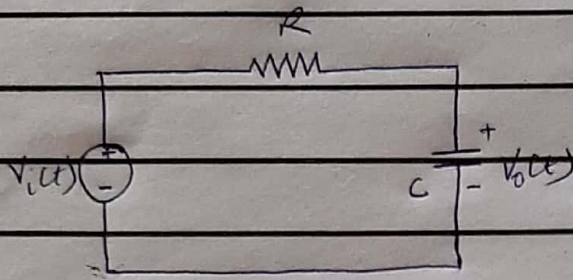


EEE328 ELECTRICAL CIRCUIT THEORY



$$C = \frac{1}{sC}$$

$$R = R$$

$$V_i(s) = V_i(s)$$

$$V_o(s) = V_o(s)$$

This is a low pass filter.

$$H(s) = \frac{V_o}{V_i} = \frac{1}{sC} \div R + \frac{1}{sC}$$

$$\frac{1}{sC} \div \frac{Rsc + 1}{sC}$$

$$\frac{1}{sC} \times \frac{sC}{Rsc + 1}$$

$$H(s) = \frac{1}{Rsc + 1} \quad ; \quad s = j\omega$$

Cut off frequency ω_c is obtained by setting the magnitude of $H(s)$ to $\frac{1}{\sqrt{2}}$

therefore

$$|H(s)| = \left| \frac{1}{Rsc + 1} \right| = \frac{\sqrt{1^2}}{\sqrt{R^2 s^2 + 1^2}}$$

recall $s = j\omega$ $j^2 = -1$

$$\frac{\sqrt{1^2}}{\sqrt{(\omega R C)^2 + 1^2}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

recall $H(\omega) = \frac{1}{\sqrt{2}}$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\sqrt{2} = \sqrt{1 + \omega^2 R^2 C^2}$$

Squaring both sides

$$2 = 1 + \omega^2 R^2 C^2$$

$$2 - 1 = \omega^2 R^2 C^2$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

Square root both sides

$$\sqrt{\omega^2} = \frac{\sqrt{1}}{\sqrt{R^2 C^2}}$$

$$\omega_c = \frac{1}{RC} \quad Q \Rightarrow$$

2