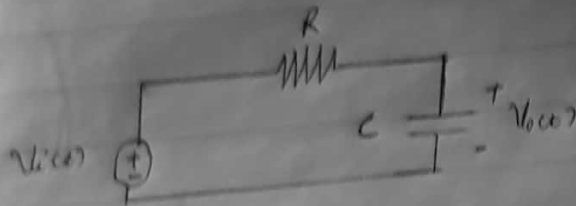


Atou Tukurwa  
17/05/2012  
Elec/Elec Engineering  
Circuit Theory

Question

Determine the type of filter shown below and show that its cut-off frequency is  $\omega_c = 1/Rc$



$$Z_F = \frac{1}{j\omega C}$$

$$V_0 = \frac{1}{j\omega C}$$

$$Z_1 = R + \frac{1}{j\omega C}$$

$$H(\omega) = \frac{V_0}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_0}{V_i} = \left[ \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \right] V_i = \frac{1}{j\omega C} \times \frac{1}{R + \frac{1}{j\omega C}}$$

$$= \frac{1}{j\omega RC + 1}$$

when  $(\omega) = 0$   $H = -1$  when  $(\omega) \infty$   $H = 0$

So therefore the cut off frequency  $\omega_c$  is obtained the magnitude of  $H(\omega)$  to  $\frac{1}{\sqrt{2}}$  which is

$$H(\omega) = \frac{1}{j\omega RC + 1} = \frac{1}{\sqrt{2}}$$

$$|H(\omega)| = \frac{\sqrt{1^2}}{\sqrt{1^2 + (\omega RC)^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{2} = \sqrt{1 + \omega^2 R^2 C^2}$$

Squaring both sides

$$2 = 1 + \omega^2 R^2 C^2$$

$$2 - 1 = \omega^2 R^2 C^2$$

$$1 = \omega^2 R^2 C^2$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

$$\omega = \omega_c$$

$$\omega = \frac{1}{RC}$$

It is a Low pass filter  $\therefore$  It is an RC circuit