

# Answer for Question

17 (Electrical  
Mechanics Spring)


Answer

Given a typical low pass filter is found when the output of an AC source is taken off the capacitor as shown below

i. The transfer function

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

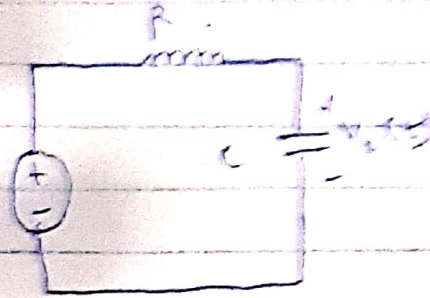

Hence  $H(\omega) = 1$  at  $\omega = 0$  and  $H(\infty) = 0$ .  
i) When the circuit is a low pass filter

~~By setting~~ By setting the magnitude of  $H(\omega)$  equal to  $1/\sqrt{2}$  to obtain cut off frequency.

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$1 = 1$$

$$\sqrt{1 + \omega_c^2 R^2 C^2} = \sqrt{2}$$

$$1 + \omega_c^2 R^2 C^2 = 2$$

$$\omega_c^2 R^2 C^2 = 2 - 1$$

$$\omega_c^2 R^2 C^2 = 1$$

$$(\omega_c RC) = \sqrt{1}$$

$$\omega_c RC = 1$$

$$\omega_c = \frac{1}{RC}$$