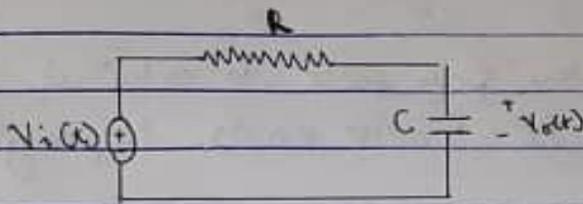


LOMOWEWE RASHIDA OMOJUNMI

171EM9041057

ELECTRICAL ELECTRONICS ENGINEERING CIRCUIT THEORY (EEE 322)

QUESTION:



Determine the type of filter shown and show that its end-off frequency is $\omega_c = 1/RC$.

SOLUTION:

1. The type of filter shown above is a LOW PASS RC FILTER.

This type of filter is generated when the output of R is removed from capacitor.

2. Show that $\omega_c = 1/RC$.

From the circuit above;

* Using the voltage division rule;

* Converting the components from time domain to frequency domain;

$$R(t) = R(s)$$

$$C(t) = 1/sC$$

* using voltage division rule;

The voltage across the capacitor $1/sC$ is V_o

* Note: Transfer function

$$H(\omega) = \frac{V_o}{V_i}$$

$$H(\omega) = \frac{V_o}{V_i} = \left(\frac{1/sC}{R + 1/sC} \right) * V_i$$

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/sC}{R + 1/sC}$$

* (multiply this by sC)

$$H(\omega) = \frac{V_o}{V_i} = \frac{1}{RSC + 1}$$

Where $S = j\omega$

$$\therefore H(\omega) = \frac{V_o}{V_i} = \frac{1}{j\omega RC + 1}$$

Noting that

$$H(0) = 1$$

$$H(\infty) = 0$$

\therefore The Cutoff frequency of a low pass filter is obtained by setting the magnitude of $H(\omega)$ to $1/\sqrt{2}$. In other words, frequency above $1/\sqrt{2}$ will be eliminated.

$$\therefore |H(\omega)| = \left| \frac{1}{j\omega RC + 1} \right|$$

$$\frac{1}{\sqrt{2}} = \frac{\sqrt{1^2}}{\sqrt{1^2 + (j\omega RC)^2}}$$

$$\therefore \sqrt{2} = \sqrt{1^2 + (j\omega RC)^2}$$

$$\therefore \sqrt{2} = \sqrt{1 + \omega^2 R^2 C^2}$$

Finding the squares of both sides;

$$\therefore (\sqrt{2})^2 = (\sqrt{1^2 + (j\omega^2 R^2 C^2)})^2$$

$$\therefore 2 = 1 + (\omega^2 R^2 C^2)$$

$$2 - 1 = \omega^2 R^2 C^2$$

$$1 = \omega^2 R^2 C^2$$

$$\omega^2 = \frac{1}{R^2 C^2}$$

\therefore Square root all sides;

$$\omega_c = \frac{1}{RC}$$

a.e.d

\therefore The cutoff frequency $\omega_c = \frac{1}{RC}$ is also called rolloff frequency.

Representing the cut-off frequency graphically on a low pass filter graph.

