

Name: Agiamah Benjamin

Matric no: 17/ENG05/005

Department: mechatronics engineering

NAME: AGIAMAH BENJAMIN

MATRIC NO: 17/ENG05/005


SIGNATURE: O.D.

COURSE CODE: ENG322

DEPARTMENT: MECHATRONICS ENGINEERING

Demonstrate the type of filter shown below, and show that its cut-off frequency

$$\omega_c = 1/RC$$

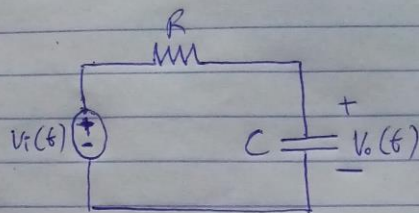

Soln

It is a low pass filter

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C}$$
$$= \frac{1}{1 + j\omega RC}$$

$$H(0) = 1$$

$$H(\infty) = 0$$

The cut off frequency,  $\omega_c$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{1 + \omega^2 R^2 C^2} = \sqrt{2}$$

$$1 + \omega^2 R^2 C^2 = 2$$

$$\omega^2 R^2 C^2 = 1$$

$$\omega = \frac{1}{RC}$$