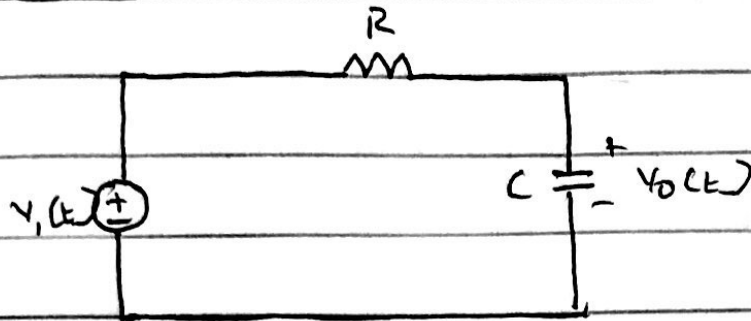


Tanarami Kluwvornitsela Adrie L

17/ENG031038

Mechatronics

EEF 322



Solution

Converting to Frequency domain

$$R \rightarrow R$$

$$C \rightarrow \frac{1}{j\omega C}$$

$$H(\omega) = \frac{V_o}{V_i}$$

Using KVL (Series Connection)

$$\begin{aligned} H(\omega) = \frac{V_o}{V_i} &= \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{\frac{1}{j\omega C}}{\frac{Rj\omega C + 1}{j\omega C}} \\ &= \frac{1}{1 + j\omega RC} \end{aligned}$$

When $H(0) = 1$, $H(\infty) = 0$

The half power frequency which is equivalent to 1/2 corner frequency on the Bode plots but in the context of filters is usually known as

Cut-off frequency ω_c , is obtained by setting magnitude of $H(\omega)$ equal to $1/\sqrt{2}$

Substituting ω_c

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

making ω_c subject of formula

Taking square of both sides

$$\frac{1^2}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2}$$

$$2 \cdot 1^2 = 1 + \omega_c^2 R^2 C^2$$

$$2 = 1 + \omega_c^2 R^2 C^2$$

$$2 - 1 = \omega_c^2 R^2 C^2$$

$$1 = \omega_c^2 R^2 C^2$$

$$1 = \omega_c R C$$

(Taking square root of both sides)

$$\omega_c = \frac{1}{RC}$$