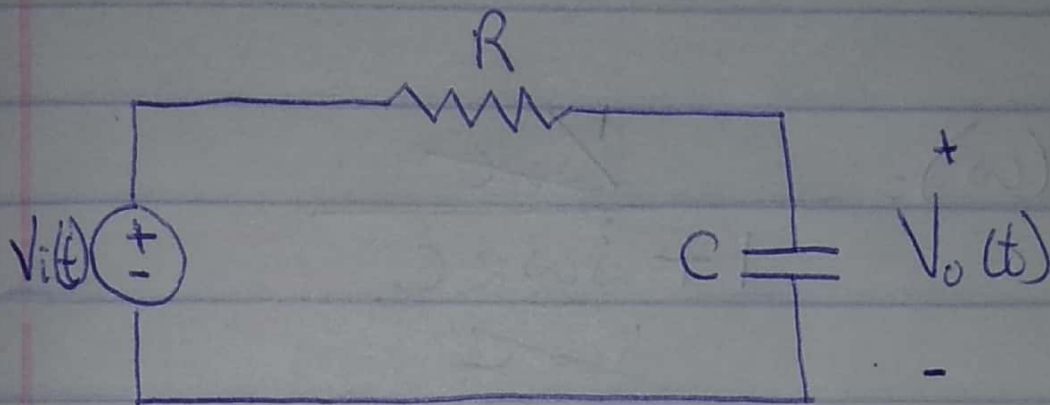


Collins David. C
17/ENG05 2010
Mechatronics Engineering



The filter shown above is a lowpass filter. A lowpass filter is formed when the output of an RC circuit is taken off the capacitor.

To obtain the cut off frequency, we first obtain the transfer function.

$$H(\omega) = \frac{V_o}{V_i}$$

$$e = \frac{1}{j\omega C} \quad , \quad R = R$$

$$H(\omega) = \frac{1/j\omega C}{R + 1/j\omega C} \quad \left. \vphantom{H(\omega)} \right\} \text{from Voltage division}$$

$$= \frac{1/j\omega C}{j\omega RC + 1}$$

$$\therefore A(\omega) = \frac{1/j\omega C}{1 + j\omega RC}$$

$$\left[H(\omega) = \frac{1}{1 + j\omega RC} \right]$$

Cutoff frequency ω_c , is obtained by setting the magnitude of $H(\omega)$ equal to $1/\sqrt{2}$.

$$\therefore H(\omega_c) = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}}$$

$$\omega_c RC + 1 = 2$$

$$\omega_c RC = 2 - 1 = 1$$

$$\left[\omega_c = \frac{1}{Rc} \right] //$$