

ADDA TOLUKWILI v.

17/ENG041013

ELECTRICAL / ELECTRONICS ENGINEERING I

ERC 500 : Electrical Machines II

Assignment

$S_r = 25 \text{ kVA}$, $V_n = 415 \text{ V}$, 3- ϕ , 4-pole $f = 60 \text{ Hz}$,
 $X_s = 1.5 \Omega$, $R_s = 0$ $\cos \theta \rightarrow P.f = 0.8$ lagging

Answer

$$1) \quad E_a = V_p + jX_s I_a + R_s I_a \\ = V_p + jX_s I_a$$

$$\cos \theta = 0.8$$

$$\theta = 36.87^\circ$$

$$V_L = 415 \quad \rightarrow \quad V_p = \frac{415}{\sqrt{3}}$$

$$= 239.6$$

$$I_a = \frac{S_r}{\sqrt{3} V_L} = \frac{25 \times 10^3}{\sqrt{3} \times 415} = 34.78 \\ \approx 34.78 \angle -36.87^\circ$$

$$E_a = V_p + jX_s I_a$$

$$E_a = 239.6 \angle 0^\circ + 1.5 \angle 90^\circ \times 34.78 \angle -36.87^\circ \\ = 270.9 + j417.4 \\ \approx 274.1 \angle 57.76^\circ \text{ V}$$

2) If I_a increased 20%, find the I_a , R_s & θ

$$I_a = \frac{E_a - V_p}{jX_s}$$

$$I_a = \frac{E_a - V_p}{jX_s}$$

$$E_{av} = 1.2 \times E_a = 1.2 \times 274.1 = 328.92$$

$$E_1 \sin \alpha = E_2 \sin \beta$$

$$\sin \beta = \frac{E_1 \sin \alpha}{E_2} = \frac{214.1 \sin 8.76}{328.92}$$

$$\sin \beta = 0.129$$

$$\beta = 7.47$$

$$I_a = \frac{328.92 \angle 7.47 - 259.6 \angle 0}{1.5 \angle 90}$$

$$= 28.51 - j57.69$$

$$I_a \approx 64.85 \angle -63.79$$

$$\text{ii) } P_f = \cos \theta$$

$$= \cos(-63.7)$$

$$= 0.4 \text{ Lagging}$$

$$\text{iii) } Q = \sqrt{3} \times V_L \times I_L \times \sin \theta$$

$$= \sqrt{3} \times 415 \times 64.85 \times \sin 63.7$$

$$= 41466.85$$

$$\approx 41.5 \text{ kVAR}$$

$$\text{3) } \underline{I_a} = \frac{\sum \underline{I_a} - \underline{I}}{\sqrt{3} X_2}$$

Since its using the same condition as in 2)

$$\rightarrow = \frac{274.1 \angle 90^\circ - 259.6 \angle 0}{1.5 \angle 90}$$

$$= 167.73 + j159.73$$

$$I_{a1} \approx 229.46 \angle 44.12$$

I_{a2}

$$\text{ii) } P_f = \cos \theta$$

$$= \cos(44.12)$$

$$= 0.7 \text{ leading}$$

$$\text{iii) } Q = \sqrt{3} \times V_L \times I_L \times \sin \theta$$

$$= \sqrt{3} \times 415 \times 229.46 \times \sin 44.12$$

$$= 114822.48$$

$$\approx 11.5 \text{ kVAR}$$