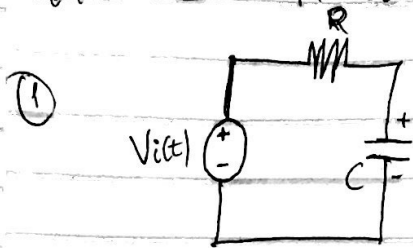


Name:- Adeboye Caleb
 Department:- Mechatronics
 Matrix No:- 17/ENWAS/001



Soln

Converting to frequency domain.

$$R = R$$

$$C = \frac{1}{j\omega C}$$

$$H(\omega) = \frac{V_2}{V_1}$$

Using KVL (Series Connection).

$$H(\omega) = \frac{V_2}{V_1} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1/j\omega C}{Rj\omega C + 1/j\omega C}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

When $H(\omega) = 1$, $H(\infty) = 0$

The half power frequency which is equivalent to the corner frequency on the BODE plot, but in the context of filters is called cut-off frequency.

ω_c is obtained by setting magnitude of $H(\omega) = 1/\sqrt{2}$

Substituting ω_c

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2}$$

$$2 \times 1^2 = 1 + \omega_c^2 R^2 C^2$$

$$2 = 1 + \omega_c^2 R^2 C^2$$

$$2 - 1 = \omega_c^2 R^2 C^2$$

$$1 = \omega_c^2 R^2 C^2$$

Taking square root of both sides

$$\sqrt{1} = \sqrt{\omega_c^2 R^2 C^2}$$

$$1 = \omega_c RC$$

$$\omega_c = \frac{1}{RC}$$