


NAME: ORILADE EMMANUEL, O.

DEPT: MECHATRONICS ENGINEERING

MATRIC NO: 17/ENG205/037

Assignment: Electric Circuits Theory II

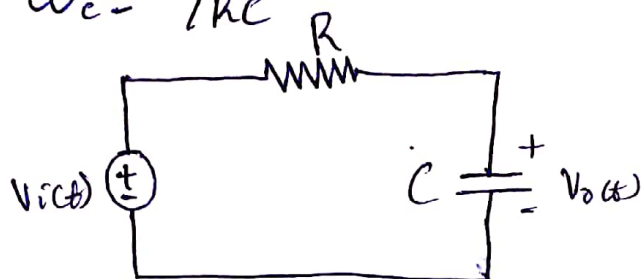
1. Determine the type of filter shown below, and show that its cut-off frequency is $\omega_c = 1/RC$



Solution

Convert the circuit from the "time domain to the frequency domain".

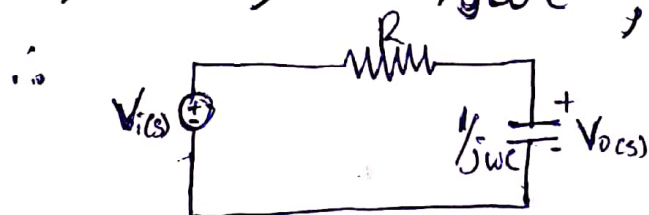$V_i(s) \Rightarrow V_i(s)$; $R \Rightarrow R$; $C \Rightarrow 1/j\omega C$; $V_o(s) \Rightarrow V_o(s)$



Using voltage division rule we would find the voltage across the capacitor; $V_o(s)$

$$\therefore V_o(s) = \left(\frac{1/j\omega C}{1/j\omega C + R} \right) \times V_i(s) \Rightarrow \left(\frac{1}{j\omega C} \times \frac{j\omega C}{1 + Rj\omega C} \right) \times V_i(s)$$

$$\therefore V_o(s) = \left(\frac{1}{1 + Rj\omega C} \right) \times V_i(s)$$

The transfer function of the filter will be;

$$H(\omega) = \frac{V_o}{V_i} = \frac{1}{1 + Rj\omega C}$$

$$\textcircled{a} H(0) = \frac{1}{1} = 1$$

$$\textcircled{a} H(\infty) = \frac{1}{\infty} = 0$$

(1)

The cut-off frequency ω_c is obtained by equating the magnitude of $H(\omega)$ to $1/\sqrt{2}$

$$\therefore |H(\omega)| = \left| \frac{1}{1+j\omega RC} \right| \Rightarrow \frac{\sqrt{1^2}}{\sqrt{1^2 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$|H(\omega)| = 1/\sqrt{2} \quad \therefore \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\therefore \sqrt{2} = \sqrt{1 + \omega^2 R^2 C^2}$$

By squaring both sides, we have:

$$2 = 1 + \omega^2 R^2 C^2$$

$$1 = \omega^2 R^2 C^2$$

$$\therefore \omega^2 = \frac{1}{R^2 C^2}$$

$$\therefore \omega = \frac{1}{RC}$$

\therefore The cut-off frequency, $\omega_c = \underline{\underline{1/RC}}$

i) NOTE: The filter is a low-pass filter. This is because the output of the RC series circuit is taken off the capacitor as shown in the circuit diagram.