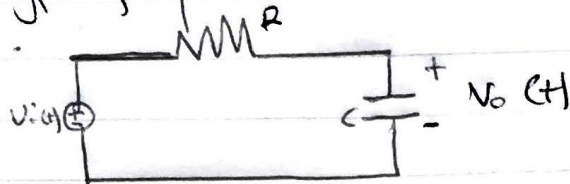


ELECT/ELECT

CIRCUIT THEORY ASSIGNMENT

Determine the type of filter below and show that its cut-off frequency

$$\text{is } \omega_c = \frac{1}{RC}$$

Answers

1) The diagram above is a low pass filter as shown by the capacitor coming out of the capacitor

2) Converting from the time domain to the frequency domain  $R \rightarrow R$  &  $C \rightarrow \frac{1}{sC}$   
 $H(\omega) = \frac{V_o}{V_i}$  but  $V_o = \frac{1}{sC}$  and  $V_i = R + \frac{1}{sC}$

$$\therefore H(\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{sC}}{\frac{sCR + 1}{sC}} = \frac{1}{sC} \times \frac{sC}{sCR + 1} = \frac{1}{sCR + 1}$$

But the cut-off frequency ( $\omega_c$ ) is obtained when the magnitude of the is set to  $\frac{1}{\sqrt{2}}$  (this)

$$|H(\omega)| = \frac{V_o}{V_i} = \frac{1}{\sqrt{sCR + 1}}$$

equating this to  $\frac{1}{\sqrt{2}}$  we then have

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{sCR + 1}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{(\sqrt{1})^2 + (\sqrt{sCR})^2 + (\sqrt{1})^2}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (sCR)^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + (j\omega CR)^2}}$$

substituting  $s = j\omega$ 

cross multiply and squaring both sides

giving  $\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \omega^2 C^2 R^2}}$

$$\left(\frac{1}{\sqrt{2}}\right)^2 = \frac{1}{1 + \omega^2 C^2 R^2}$$

$$2 = 1 + \omega^2 C^2 R^2$$

collecting like terms

$$2 - 1 = \omega^2 C^2 R^2$$

$$1 = \omega^2 C^2 R^2$$

dividing through by  $C^2 R^2$ 

$$\frac{1}{C^2 R^2} = \omega^2$$

$$\omega = \frac{1}{RC}$$

$$\therefore \omega_c = \frac{1}{RC}$$