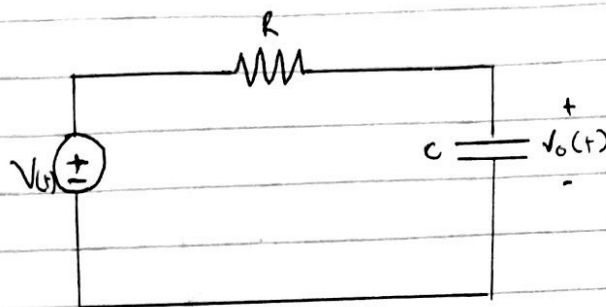


Emerode Chigoeme Ikenna  
MECHATRONICS ENGINEERING  
17ENG051012

Determine the type of filter shown below & Show that its cut off frequency is

$$\omega_c = 1/Rc$$



Solution

A typical low pass filter is shown above. The output is taken off the capacitor

$$\text{Recall } H(\omega) = \frac{V_0}{V_i} = \left( \frac{1/sC}{R + 1/sC} \right)$$

$$H(0) = 1$$

$$H(\infty) = 0$$

The cut off frequency  $\omega_c$  is obtained by setting the magnitude of  $h(\omega)$  to  $= 1/\sqrt{2}$

$$|H(\omega)| = \left| \frac{1}{sRC + 1} \right| = \frac{1}{\sqrt{2}}$$

$$= \frac{\sqrt{1^2}}{\sqrt{1^2 + (W^2 R^2 C^2)}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 + W^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$
$$\sqrt{2} = \sqrt{1 + W^2 R^2 C^2}$$

Squaring both sides

$$2 = 1 + W^2 R^2 C^2$$

$$2 - 1 = W^2 R^2 C^2 = 1$$

$$W^2 = \frac{1}{R^2 C^2}$$

$$W_0 = \frac{1}{RC}$$