


BASSEL SALOUH JOSEPH

16/ENG05/015

MECHATRONICS ENGINEERING

EE222 - CIRCUIT THEORY

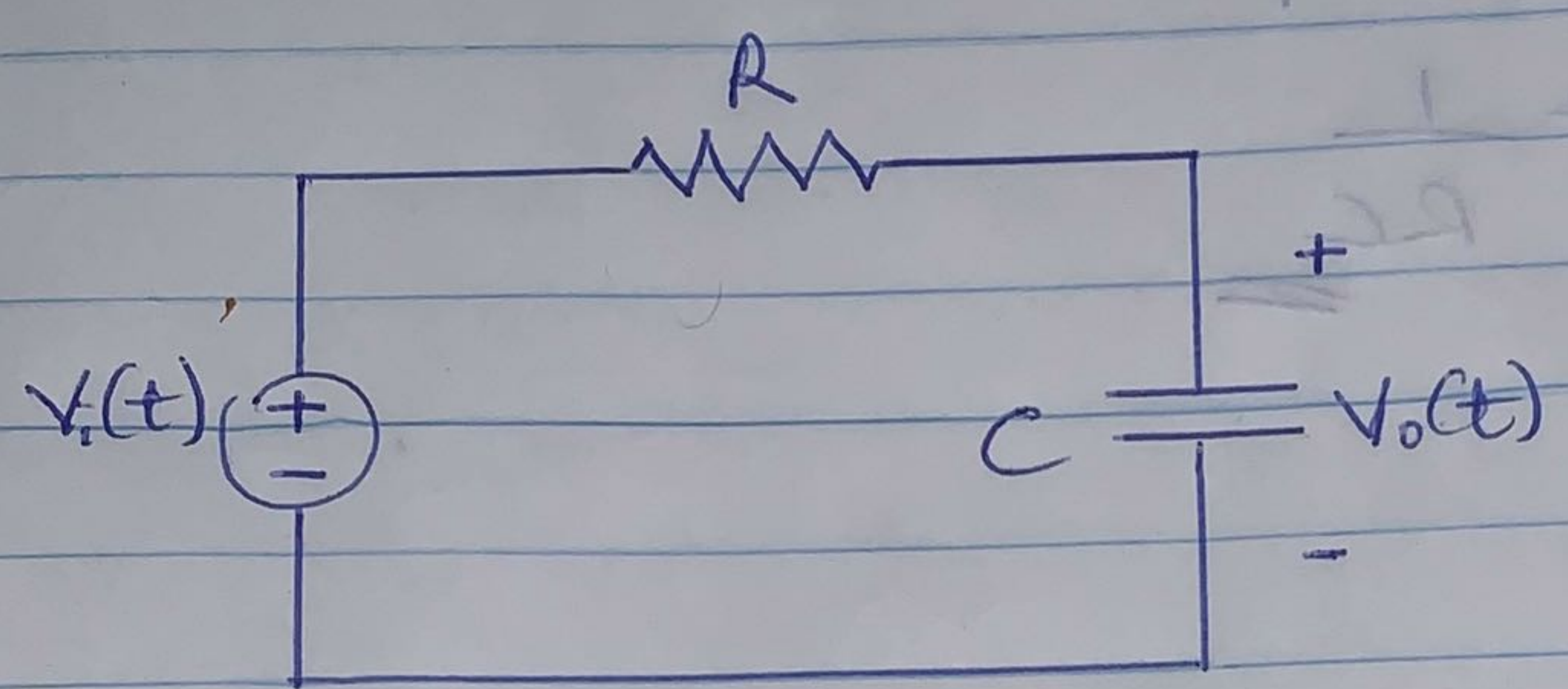1) Determine the type of filter shown below, and show that its cut-off frequency is  $\omega_c = 1/RC$



Solution

Converting to frequency domain

$$R = R$$

$$C = 1/j\omega C$$

$$H(\omega) = V_o/V_i$$

using KVL (Series Connection)

$$H(\omega) = \frac{V_o}{V_i} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$= \frac{1}{j\omega C} \times \frac{j\omega C}{Rj\omega C + 1}$$

$$= \frac{1}{Rj\omega C + 1}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

when  $H(0) = 1$ ,  $H(\infty) = 0$

(i) Hence, the circuit is a Low Pass Filter

By setting the magnitude of  $H(\omega)$  equal to  $1/\sqrt{2}$  to obtain cut-off frequency.

$$H(\omega_c) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$1 = 1$$

$$\sqrt{1 + \omega_c^2 R^2 C^2} = \sqrt{2}$$

$$1 + \omega_c^2 R^2 C^2 = 2$$

$$\omega_c^2 R^2 C^2 = 2 - 1$$

$$\omega_c^2 R^2 C^2 = 1$$

$$(\omega_c R C) = \sqrt{1}$$

$$\omega_c R C = 1$$

$$\omega_c = \frac{1}{RC}$$

$$\underline{\underline{RC}}$$