

Modulim Tochukwu Adrian

17/Eng04/041


Electrical / Electronics Engineering  
Circuit Theory II EEE 322

D) Determine the type of filter shown below and show its cut off frequency is  $\omega_c = 1/Rc$

Solu

This is a low pass filter. A typical low pass filter is formed when the output of an RC circuit is taken off the capacitor

1sm diagram R

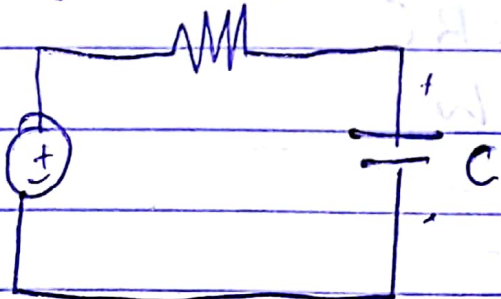

Converting to frequency domain

$$R \rightarrow R, \quad C \Rightarrow \frac{1}{j\omega C}, \quad H(\omega) = \frac{V_o}{V_i}$$

Using Kirchoff Voltage law

$$H(\omega) = \frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \Rightarrow \frac{1}{1 + j\omega RC}$$

17/Eng 04/04/

When  $H(\omega) = 1$ ,  $\angle H(\omega) = 0$

The half power frequency which is equivalent to the corner frequency on the bode plot is obtained by setting magnitude of  $H(\omega) = 1/\sqrt{2}$

Substituting  $H(\omega) = 1/\sqrt{2}$

$$\frac{1}{\sqrt{2}} = H(\omega) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

Taking square

$$\frac{1}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2}$$

$$2 = 1 + \omega_c^2 R^2 C^2$$

$$\therefore 1 = \omega_c^2 R^2 C^2$$

Square rooting both sides

$$1 = \omega_c R C$$

$$\therefore \frac{1}{R C} = \omega_c$$