

UMER DANIEL CHAZAM

17/eng04/068

Elect/Elect

- A typical resonance filter is formed when the output of an RC is turned off in a circuit as shown below


Therefore, the transfer

$$T(\omega) = \frac{V_1}{V_2} = \frac{I_{AVC}}{R + \frac{1}{j\omega C}}$$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

$$H(\omega) = 1$$

$$H(\infty) = 0$$

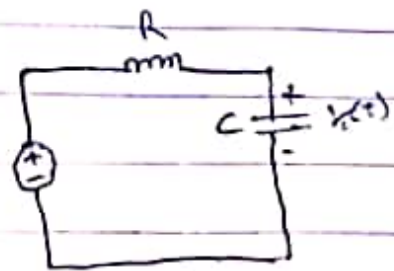

i) Hence the circuit is a low pass filter

By setting the magnitude of $H(\omega)$ equals $\frac{1}{\sqrt{2}}$ to obtain cut off frequency

$$H(\omega) = \frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{1 + \omega_c^2 R^2 C^2} = \sqrt{2}$$

$$1 + \omega_c^2 R^2 C^2 = 2$$

$$\omega_c^2 R^2 C^2 = 2 - 1$$

$$\omega_c^2 R^2 C^2 = 1$$

$$(\omega_c RC) = \sqrt{1}$$

$$\omega_c RC = 1$$

$$\omega_c = \frac{1}{RC}$$