


Ejike David Chindru

18/ENG04/018

Electrical/Electronics Engineering

Circuit Theory

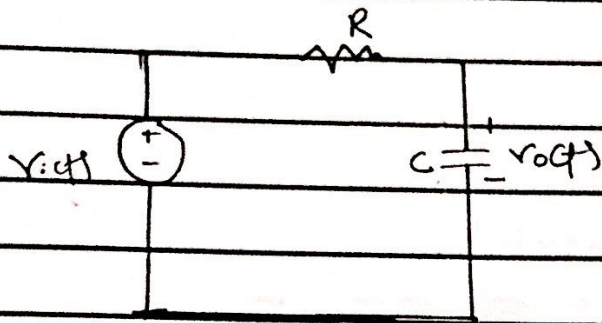• Determine the type of filter shown below and show that its cut-off frequency is $\omega_c = 1/RC$



→ If a low pass filter, when the output of an RC circuit is taken off the capacitor then a low pass filter is formed.


The transfer function can be given as: $H(\omega) = \frac{V_o}{V_i} = \frac{1}{R + j\omega C}$

$$H(\omega) = \frac{1}{1 + j\omega RC}$$

But $H(0) = 1, H(\infty) = 0$

The half-power frequency that's equivalent to the corner frequency on the Bode plots but in the context of filters is usually known as the cut-off frequency ω_c is obtained by setting the magnitude of $H(\omega)$ equal to $1/\sqrt{2}$ thus
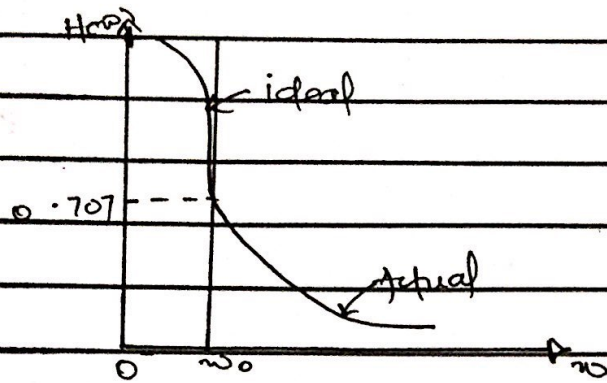
$$H(\omega) = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$



Ideal and Actual frequency response of low pass filter

The cut off frequency is also called the rolloff frequency