

## Assignment on Power-factor correction

Name: Shonubi Emmanuel

Dept: Mechanical Engineering

Mat no: H12ANG061075

Course code: EE326

(A)  $E_2 = V_t - jI_2 X_1$

$V_t = 415V, S = 25kVA = 25000VA$

$V_t = \frac{V_1}{\sqrt{3}} = \frac{415}{\sqrt{3}} = 239.6V$

$X_1 = 1.5\Omega, pf = 0.8 \text{ lagging}$

$\therefore \theta = \cos^{-1}(0.8) = 36.87^\circ$

$I_2 = \frac{S}{\sqrt{3} V_t} = \frac{25000}{415\sqrt{3}}$

$34.78A \angle 143.13^\circ$

$\therefore E_2 = 239.6 - j [34.78 \times 1.5] \angle 143.13^\circ$

$E_2 = 270.90 + j41.74$

$E_2 = 274.098V \angle 8.76^\circ$

(B) 20% increase = 1.2

$\theta = 8.76^\circ$

$E_2' = 1.2 \times 274.098 = 328.92V$

$\frac{V_t E_2' \sin \theta'}{X_1} = \frac{V_t E_2' \sin \theta}{X_1} \therefore \sin \theta' = \frac{E_2 \sin \theta}{E_2'} = \frac{274.098 \times \sin 8.76^\circ}{328.92}$

$\sin \theta' = 0.1269$

$\therefore \theta' = \sin^{-1}(0.1269)$

$\therefore \theta' = 7.29^\circ$

$I_{A'} = \frac{E_2' - V_t}{jX_0} = \frac{328.92 \angle 7.29^\circ - 239.6 \angle 0^\circ}{j1.5} = 27.82 - j57.77$

$I_{A'} = 64.13A \angle -64.28^\circ$

(C)  $P_1 = \cos(-64.28) = 0.434$

$$(1) Q = 3V + I_{2 \text{ max}} \sin \theta = 3 \times 239.6 \times 64.13 \times 1.17 (64.28) = 41529.65 \text{ VAR}$$

(C) At maximum power,  $\delta = 90^\circ$

$$P_{\text{max}} = \frac{3E_2 V_t}{X_s} = \frac{3 \times 274.098 \times 239.6}{1.5} = 131347.76 \text{ W} = 131.35 \text{ KW}$$

$$I_{\text{max}} = \frac{E_2 - V_t}{X_s} = \frac{274.098 \angle 90^\circ - 239.6 \angle 0^\circ}{1.5j} = 242.71 \angle 41.16^\circ$$

$$P_f = \cos(41.16^\circ) = 0.7529 \text{ leading pf}$$

$$Q_{\text{max}} = 3V + I_{2 \text{ max}} \sin(41.16^\circ) = 3 \times 239.6 \times 242.71 \times 0.6582 = 114820.54 \text{ VAR} = 114.83 \text{ KVAR}$$