

JUTTO-OKOR EBEROCHINE  
11/ENCA06/042

MECHANICAL ENGINEERING

A 25kVA, 415V, three-phase, 4 pole, 60Hz wire-connected synchronous generator has a synchronous reactance of  $1.5\Omega$ /phase and negligible stator resistance. The generator is connected to an infinite bus of constant voltage magnitude and constant frequency of 415V and 60Hz

(a) Determine the excitation voltage,  $E_a$  when the machine is delivering rated

kVA of 0.8 pf lagging

$$E_a = V_t - j I_a X_s ; V_t = 415V, S = 25kVA = 25000VA$$

$$V_t = \frac{415}{\sqrt{3}} = 239.6V$$

$$X_s = 1.5\Omega ; PF = 0.8 \text{ lagging} ; \therefore \theta = \cos^{-1}(-0.8) = 143.13^\circ$$

$$I_a = \frac{S}{\sqrt{3} V_t} = \frac{25000}{\sqrt{3} \cdot 415} = 34.78A \angle 143.13^\circ$$

$$\therefore E_a = 239.6 - j(34.78 \angle 143.13^\circ)(1.5)$$

$$E_a = 270.90 + j11.74$$

$$E_a = 274.098V \angle 8.76^\circ$$

(b) The field excitation current  $I_f$  is increased by 20% without changing the power input from the prime mover. Find the stator current  $I_a$ , Power factor and reactive power  $Q$  supplied by the machines.

$$\therefore 20\% \text{ increased} = 1 + 0.2 = 1.2$$
$$\delta = 8.76^\circ$$

$$E_a' = 1.2 \times 274.098 = 328.92V$$

$$\therefore \frac{V_t E_a \sin \delta}{X_s} = \frac{V_t E_a' \sin \delta'}{X_s} ; \sin \delta' = \frac{E_a \sin \delta}{E_a'} \rightarrow \frac{274.098 \times \sin 8.76}{328.92}$$

$$\sin \delta' = 0.1269 ; \therefore \delta' = \sin^{-1}(0.1269)$$
$$\delta' = 7.29^\circ$$

$$I_a' = \frac{E_a' - V_t}{jX_s} = \frac{328.92 \angle 7.29^\circ - 239.6 \angle 0^\circ}{j1.5} = 27.82 - j57.77$$

$$(ii) \text{ Power factor} = \cos(-64.28^\circ) = 0.434 \text{ lagging}$$

$$(iii) Q = 3V_t I_a \sin \theta = 3 \times 239.6 \times 64.13 \times \sin(64.28^\circ) = 41527.65 \text{ VAR}$$

c) With the field excitation current  $I_f$  as in part (c), the input power from the prime mover is increased very slowly. What is the steady state limit? Determine stator current  $I_a$ , power factor and reactive power  $Q$ .

At max power  $\delta = 90^\circ$

$$P_{\max} = 3E_a V_t = 3 \times 274.098 \times 239.6 = 131347.79 \text{ W} = 131.347 \text{ kW}$$

$$X_s = 20 \times 1.5 = 30 \text{ } \Omega$$

$$I_{\max} = \frac{E_a - V_t}{X_s} = \frac{274.098 \angle 90^\circ - 239.6 \angle 0^\circ}{30} = 242.21 \text{ A} \angle -41.16^\circ$$

$$\text{Power factor} = \cos(41.16^\circ) = 0.7529 \text{ leading}$$

$$Q_{\max} = 3V_t I_a \sin(41.16^\circ) = 3 \times 239.6 \times 242.21 \times 0.6582 = 114829.54 \text{ VAR}$$

$$\text{Power factor} = 0.7529 \text{ leading}$$