

SUMMARY OF ANALOG MULTIPLIERS

In an analog signal processing, the term analog multipliers refer to a circuit that takes two analog inputs and produces an output proportional to their product.

In this note, we take a close look on several types of analog multipliers that depend on **exponential transfer function of bipolar transistors**. A few are listed below;

- ✓ The emitter coupled pair as a simple multiplier
- ✓ Two quadrant restriction
- ✓ Gilbert multiplier cell
- ✓ Gilbert cell-DC analysis
- ✓ Gilbert cell applications
- ✓ Gilbert cell as multiplier
- ✓ Pre-warping circuit-inverse hyperbolic tangent
- ✓ Complete analog multipliers
- ✓ Gilbert cell as a balanced modulator
- ✓ Spectra for balanced modulator
- ✓ Gilbert cell as a phase detector

- **Emitter-coupled pair** by itself can be seen /used as a primitive multiplier
Since we assume, $(V_{id} / 2V_T) \ll 1, \Rightarrow \Delta I_c = I_{EE} (V_{id} / 2V_T)$.
- In the **two quadrant restriction**, the multiplier circuit functions in the latter quadrant of the V_{id} and V_{i2} plan.
- **Gilbert multiplier cell** is a modification of the emitter-coupled cell and the two-quadrant multiplier since modern communication applications employ four-quadrant operations.
- **Gilbert cell-DC analysis / Gilbert cell applications**
The gilbert cell application depends on three (3) main conditions;
 - a) If V_1 or $V_2 < V_T$ then : $\tanh(V_{1,2} / 2V_T) \cong V_{1,2} / 2V_T$
 - b) If one of the inputs of a signal that is large compared to V_T , this effectively multiplies the applied small signal by a square wave, then it acts as a modulator.
 - c) If both inputs are large compared to V_T , then all six transistors in the circuit behave as non-saturating switches.
- **Gilbert cell as multiplier**
The circuit performs an analog multiplication for small amplitude input signals, but when the input amplitude signal becomes larger, a non-linear approach is employed.
- **Pre-warping circuit-inverse hyperbolic tangent**
Because of the non-linearity approach in converting large input signal, warping effect occurs on the signal. So a pre-warping circuit is employed in solving the problem (i.e bringing an inverse hyperbolic tangent to compensate for the hyperbolic tangent transfer characteristic)
- **Complete analog multipliers**

This is made up of 6 transistors (3 pairs) which forms the multiplier core, the differential voltage-to-current converters form the single-ended outputs.

- **Gilbert cell as a balanced modulator**

The gilbert cell can be employed as a balanced-modulator in communications systems by applying a sufficiently large signal directly to cross-coupled pair.

- **Spectra for balanced modulator**

Balanced modulation occurs where there are no output components at the carrier-frequency or its harmonics.

- **Gilbert cell as a phase detector**

The circuit acts as a phase detector when two identical unmodulated-frequency signals are applied at the input. So it gives the output as the phase difference of the two inputs.

SUMMARY OF PHASE LOCKED LOOP (PLL) CIRCUITS

In summary; a phase locked loop is a feedback system that is composed of a **VCO, phase detector, and low pass filter** within its loop. Its purpose is to force the VCO to replicate and track the frequency and phase at the input when in lock.

- **Phase detector:** compares the phase at each input and generates an error signal, $v_e(t)$, proportional to the phase difference between the two inputs. Since an analog circuit acts as a phase detector when two identical unmodulated-frequency signals are applied at the input, we can then say;

$$v_e(t) = A(t)B(t).$$

If,

$$A(t) = A \cos(\omega t + \phi_A)$$

$$B(t) = B \cos(\omega t + \phi_B)$$

$$\text{Then, } A(t)B(t) = (AB/2)[\cos(2\omega t + \phi_A + \phi_B) + \cos(\phi_A - \phi_B)]$$

- **The VCO:** oscillates at an angular frequency. A high loop gain is beneficial for reducing phase errors.
- **Low pass filter:** This circuit attends to two main sources of noise.
 1. Reference noise – This is a low pass transfer function. Usually small since we frequently use a crystal oscillator.
 2. VCO noise – This is a high pass closed loop transfer function. Often high.

We also take a look at some important parameters/circuits in the PLL circuit.

- a) PLL dynamic range
- b) Lock range
- c) Capture range
- d) Approach (to the type of transfer function employed)
- e) Phase frequency detector
- f) Charge pump filter
- g) Closed loop frequency response
- h) PLL phase noise
- i) Reference spurs