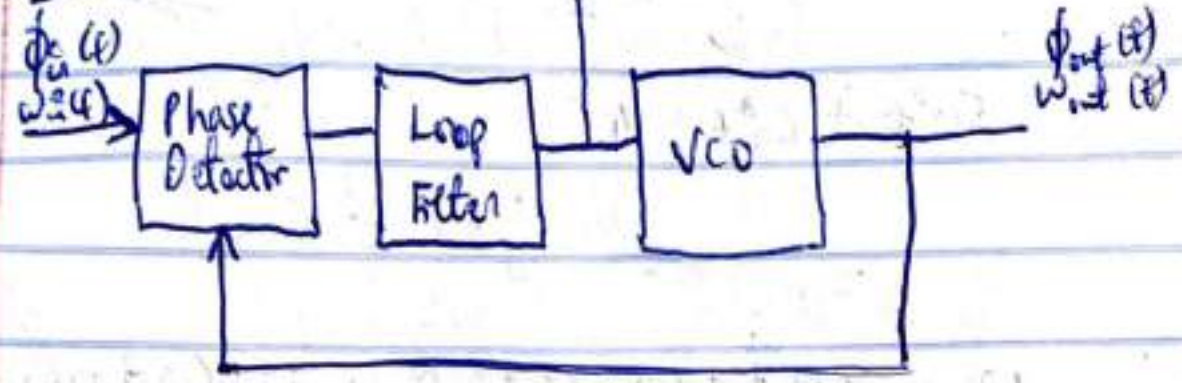


① Phase Locked Loop  
Intro



PLL output can be taken from either,

- $V_{cont}$
- VCO

depending upon the application.

\*  $V_{cont}$  output provides a baseband output that tracks the phase variation at the input.

\* VCO output can be used as a local oscillator or to generate a clock signal for a digital system.

(Either phase or frequency can be used as the input or output variables.)

Relation b/w phase and frequency  $\Rightarrow$

$$\omega(t) = \frac{d\phi}{dt}$$

$$\phi(t) = \phi(\omega) + \int_0^t \omega(t') dt'$$



3 applications for the PLL

- Clock generalization
- Frequency synthesizer
- Clock recovery in a serial data link.

## ② Phase detector

Compares the phase at each input and generates an error signal  $V_e(t)$  proportional to the phase difference between the two inputs.  $K_p$  is the gain of the phase detector ( $V(\text{rad})$ )

$$V_e(t) = K_p [\phi_{\text{out}}(t) - \phi_{\text{in}}(t)]$$

An analog multiplier or mixer can be used as a phase detector.

Recall that the mixer takes the product of 2 inputs  $\Rightarrow$

$$V_e(t) = A(t)B(t). \text{ If}$$

$$A(t) = A \cos(\omega_0 t + \phi_A)$$

$$B(t) = B \cos(\omega_0 t + \phi_B)$$

$$\text{Then } A(t)B(t) = \frac{AB}{2} [\cos(\omega_0 t + \phi_A + \omega_0 t + \phi_B) + \cos(\omega_0 t + \phi_A - \omega_0 t - \phi_B)]$$

$$= \frac{AB}{2} [\cos(2\omega_0 t + \phi_A + \phi_B) + \cos(\phi_A - \phi_B)]$$

\* The doubled freq component must be removed by the lowpass loop filter. Any phase difference then shows up as the control voltage to the VCO, a DC or slowly varying AC signal after filtering.



② VCO

In PLL applications, VCO is treated as a linear, time-invariant system.  
Excess phase of the VCO is the system output.

$$\phi_{out} = K_o \int V_{cont} dt'$$

The VCO oscillates at an angular frequency,  $\omega_{out}$ .

- VCO oscillates at an angular frequency,  $\omega_{out}$ .

- Its freq. is set to a nominal  $\omega_o$  when the control voltage is zero.

- Frequency is assumed to be linearly proportional to the control voltage, with a gain coefficient  $K_o$  or  $K_{VCO}$  (rad/s/V).

$$\omega_{out} = \omega_o + K_o V_{cont}$$

- This to obtain an arbitrary output freq. (within the VCO tuning range of course) a finite  $V_{cont}$  is required.

(From the diagram)

- XOR function produces an output pulse whenever there is a phase misalignment.

- Suppose output freq. ' $\omega_s$ ' is needed; a control voltage  $V_1$  will be necessary to produce this output freq.

- The phase detector can produce this  $V_1$  only by maintaining a phase offset  $\phi_o$  at its output.



- In order to minimize the required phase offset or error, the PLL loop gain  $K_D K_O$ , should be maximized since  $\Rightarrow$


$$\phi_0 = \frac{V_1}{K_D} = \frac{\omega_1 - \omega_0}{K_D K_O}$$

$\therefore$  Thus, a high loop gain is beneficial for reducing phase errors.

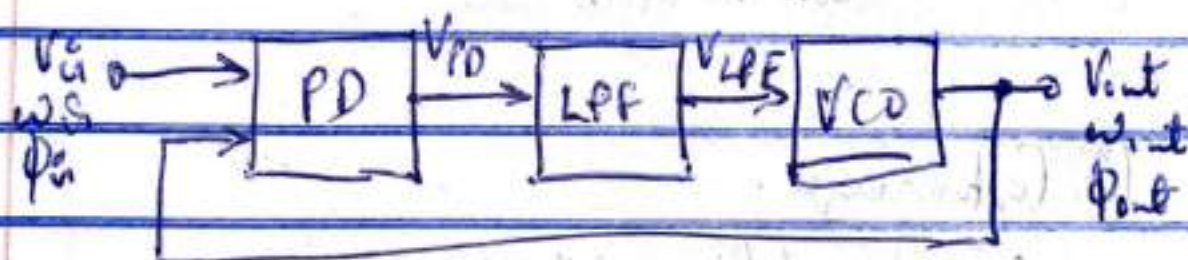(A) PLL dynamic response:

$$\Rightarrow \phi_{in} = \omega_1 t + \phi_0 + \phi_1 u(t-t_1)$$

We introduce a phase step at the input at  $t=t_1$ .



$$\leftarrow V_{out} = V_{LRF}$$

$\Rightarrow$  Frequency step

$$\omega_2 = \omega_1 + \Delta\omega$$

### ⑤ Lock Range

Range of input signal frequencies over which the loop remains locked once it has captured the input signal. This can be limited either by phase detector or the VCO freq range.

$$V_{e-max} = \pm K_D \pi/2$$

When the phase detector output voltage is applied through the loop filter to the VCO.

$$\Delta \omega_{int-max} = \pm K_V \pi/2 = \omega_L (\text{lock range})$$


where  $K_V = K_D K_N$

### ⑥ Capture range

Range of input freq around the VCO center freq, onto which the loop will lock when starting from an unlocked condition.



## PLL is a feedback system

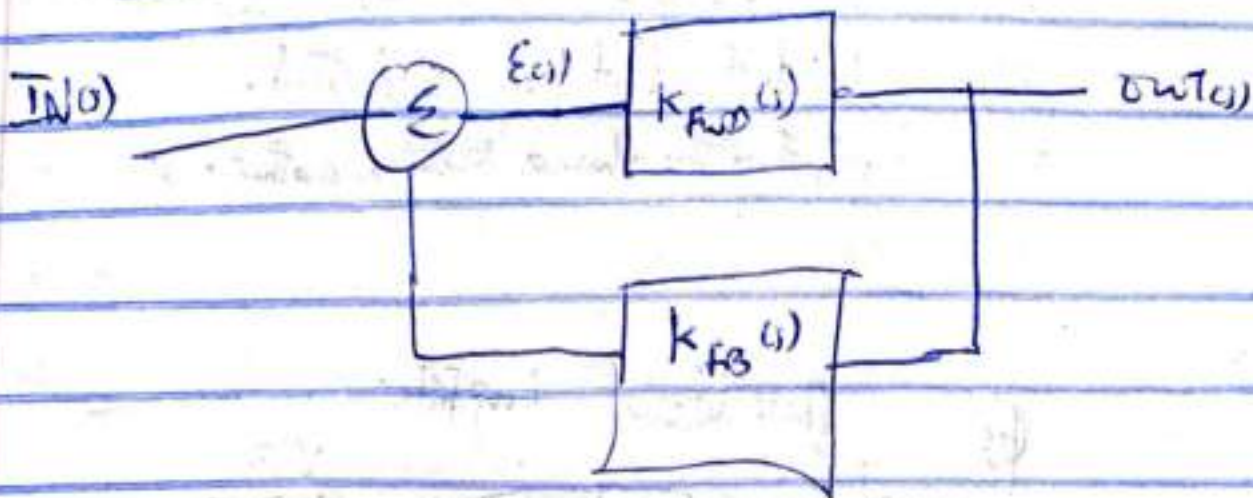

$$\text{Loop Gain: } T(s) = K_{FWD}(s) K_{FB}(s)$$

$$\text{Transfer function: } \frac{OUT(s)}{IN(s)} = H(s) = \frac{K_{FWD}(s)}{1 + K_{FWD}(s) K_{FB}(s)}$$
$$= \frac{K_{FWD}(s)}{1 + T(s)}$$

The loop gain can be described as a polynomial:

$$T(s) = \frac{K' (s+k) (s/\beta)}{s^n (s+\alpha) (s+\beta)}$$

$$\text{Phase Error} = E(s) = \frac{IN(s)}{1 + T(s)}$$

$$\text{Steady State Error} = E_{SS} = \lim_{s \rightarrow 0} [s E(s)] = \lim_{t \rightarrow \infty} e(t)$$


SS error is the error remaining in the loop after all transients have died out.

Frequency and phase tracking loop:

Let's consider PLL with feedback = 1

This means input & output freq are identical.

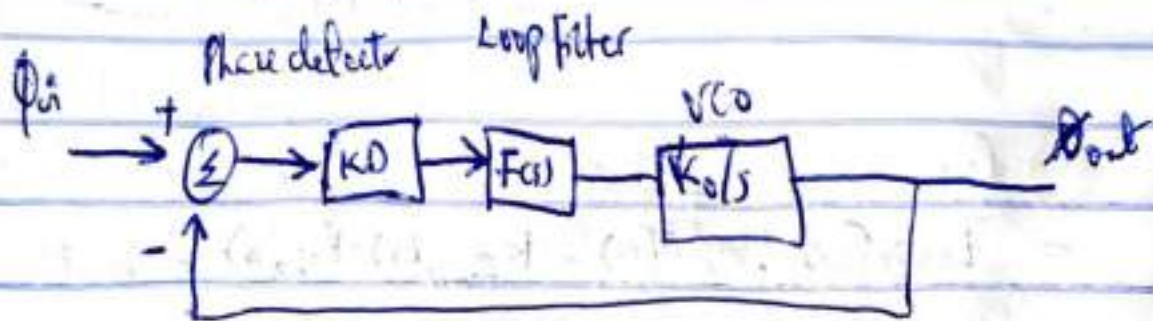Input and output phase should track one another.



$$TF: H(s) = \frac{\text{Forward path gain}}{[1 + T(s)]}$$

$$H(s) = \frac{T(s)}{[1 + T(s)]}$$

$$H(s) = \frac{\phi_{out}}{\phi_{in}} = \frac{K_D K_0 F(s) / s}{1 + K_D K_0 F(s) / s}$$

Phase error function:


$$E_p = \phi_{in} - \phi_{out} = \frac{s \phi_{in}}{s + K_D K_0 F(s)}$$



Open loop gain  $T(s) \Rightarrow$

$$T(s) = K_0 F(s) K_0/s$$

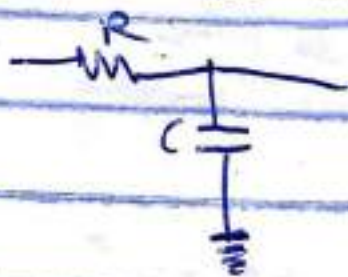We know that the phase detector will be producing an output equal to  $\omega$  at twice the carrier frequency; this same low pass filtering will be needed.  $\omega_c$  must not sample RC low pass network.



This network has a cut-off (3dB) frequency  $\omega_c$ .

$$\omega_c = 1/RC$$

Thus the filter TF is a simple low pass,

$$F(s) = \frac{1}{1 + s/\omega_c}$$

Then,  $T(s)$  becomes second order, Type 1's

$$T(s) = \frac{K_0}{s} \frac{K_0}{1 + s/\omega_c} = \frac{K_0 K_0}{s(1 + s/\omega_c)} = \frac{K_v}{s(1 + \frac{s}{\omega_c})}$$

\* From the bode plot, shows a conflict between stability and minimizing phase error.



Root Locus

↳ This represents the roots of the denominator of the closed loop T.F.

Set  $1+G=0$  and solve for  $S(s)$  = function of  $K_v$ .

$$0 = 1 + \frac{K_v}{s(s + \frac{s}{\omega_1})}$$

$$0 = 1 + \frac{K_v}{s + s^2 \omega_1}$$

$$0 = 1 + \frac{K_v}{\omega_1 s + s^2}$$

$$0 = 1 + \frac{K_v \omega_1}{\omega_1 s + s^2}$$

$$0 = \frac{\omega_1 s + s^2 + K_v \omega_1}{\omega_1 s + s^2}$$

$$\overset{a}{s^2} + \overset{b}{\omega_1} s + \overset{c}{K_v \omega_1} = 0$$

$$s = \frac{-\omega_1 \pm \sqrt{\omega_1^2 - 4K_v \omega_1}}{2}$$



$$s = \frac{-\omega_1}{2} \pm \sqrt{\omega_1^2 - 4Kv\omega_1}$$

$$s = \frac{-\omega_1}{2} \pm \sqrt{\omega_1^2 \left(1 - \frac{4Kv}{\omega_1}\right)}$$

~~$$s = \frac{-\omega_1}{2} \pm \sqrt{\omega_1^2 - 4Kv\omega_1}$$~~

$$s = \frac{-\omega_1}{2} \left(1 \pm \sqrt{1 - \frac{4Kv}{\omega_1}}\right)$$

we see that as  $Kv$  is increased, the roots approach one another then become complex conjugates.

we can have an underdamped response when  $\omega_1 \ll Kv$ .

Think about the inverse Laplace transform of the complex conjugate pole pair:

$$e^{-\omega_1 t/2} \sin\left(\frac{\omega_1}{2} \sqrt{1 - \frac{4Kv}{\omega_1}} t\right)$$

There is an exponentially decaying term determined by the real part of the root that shows how long it takes to settle after a phase or frequency step and a ringing freq dictated by the imaginary part of the pole pair.

when  $\omega_1 \ll Kv$ , we have a high ringing frequency and a long settling time, characteristic of a system that is not very useful.



It is sometimes useful to determine a natural frequency  $\omega_n$  and a damping factor  $\zeta$ . This is standard terminology for 2nd order systems.

The characteristic polynomial denominator  $(1 + T(s))$  is standard form:

either

$$s^2 + 2\zeta\omega_n s + \omega_n^2$$

or

$$\frac{s^2}{\omega_n^2} + \frac{2\zeta}{\omega_n} s + 1$$

For the first  $\Rightarrow$

$$\begin{aligned} (1 + T(s)) &= s^2 + \omega_1 s + K_v \omega_1 \\ &= s^2 + 2\zeta\omega_n s + \omega_n^2 \end{aligned}$$

$$\omega_n = \sqrt{K_v \omega_1}$$

$$2\zeta\omega_n = \omega_1$$

$$2\zeta\sqrt{K_v \omega_1} = \omega_1$$

$$\zeta = \frac{1}{2} \frac{\omega_1}{\sqrt{K_v \omega_1}}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1^2}{K_v \omega_1}} = \frac{1}{2} \sqrt{\frac{\omega_1}{K_v}}$$




This form allows you to use standard eqn and normalized plot plots to describe the freq and transient response of the system.

A large  $K_v$ , which we like for reducing phase error, leads to a small  $\gamma$ , which is bad for stability and settling time.

To obtain a better Transfer function that gives us more flexibility in determining the bandwidth of the filter and stability of the system, we add a zero to the loop filter T.F. & manipulate the root locus and ensure stability.

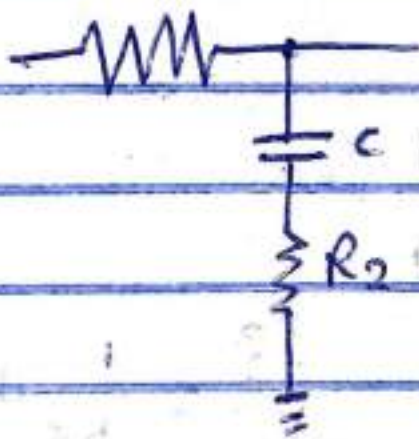Adding a resistor bypass loop filter contributes a zero to its transfer function.



$$F(s) = \frac{1 + s/\omega_2}{1 + s/\omega_1}$$

$$\text{where } \omega_1 = \frac{1}{(R_1 + R_2)C}$$

$$\omega_2 = \left(\frac{1}{R_2 C}\right)$$



Thus the zero frequency is always higher than the pole frequency.

Part. Locus: Calculate the closed loop TF for this TL with the pole zero loop filter

$$\frac{\Phi_o}{\Phi_i} = \frac{(1 + s/\omega_z)}{\frac{s^2}{K_v \omega_1} + s \left( \frac{1}{K_v} + \frac{1}{\omega_2} \right) + 1}$$

Extract  $\omega_n$  and  $\zeta$  from the closed loop TF.

~~$$2\zeta\omega_n = \frac{1}{K_v} + \frac{1}{\omega_2}$$~~

$$\omega_n^2 = K_v \omega_1$$

$$\omega_n = \sqrt{K_v \omega_1}$$

$$2\zeta\omega_n = \frac{1}{K_v} + \frac{1}{\omega_2}$$

$$\omega_n \zeta = \frac{\sqrt{K_v \omega_1}}{2K_v} + \frac{\sqrt{K_v \omega_1}}{2\omega_2}$$

$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_1}{K_v}} + \frac{1}{2} \frac{\omega_n}{\omega_2}$$



Solving for 's', the poles are

$$s = -\zeta\omega_n \pm \omega_n\sqrt{\zeta^2 - 1}$$

## Frequency Response DAY 2

### Phase Error

- No frequency error when the loop is locked  
Input frequency = output frequency.


$$\text{Phase Error} = \epsilon(s) = \frac{IN(s)}{1+T(s)}$$

$$\text{Steady state error} = \epsilon_{ss} = \lim_{s \rightarrow 0} [s \epsilon(s)] = \lim_{t \rightarrow \infty} \epsilon(t)$$

Transient phase error  $\rightarrow$  Inverse Laplace transform of  $\epsilon(s)$ .




## Loop Filter - Op Amp

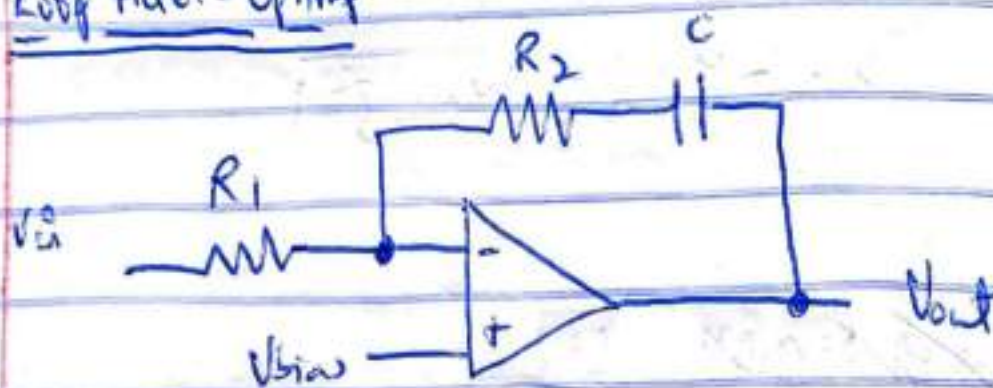

Op-amp can be used to form a filter that includes a pole at  $s=0$  and a finite zero. Virtual ground approximation can be used to analyze the circuit above to obtain  $F(s)$ .

$$F(s) = \frac{V_{out}}{V_{in}} = \frac{1 + sR_2C}{sR_1C}$$

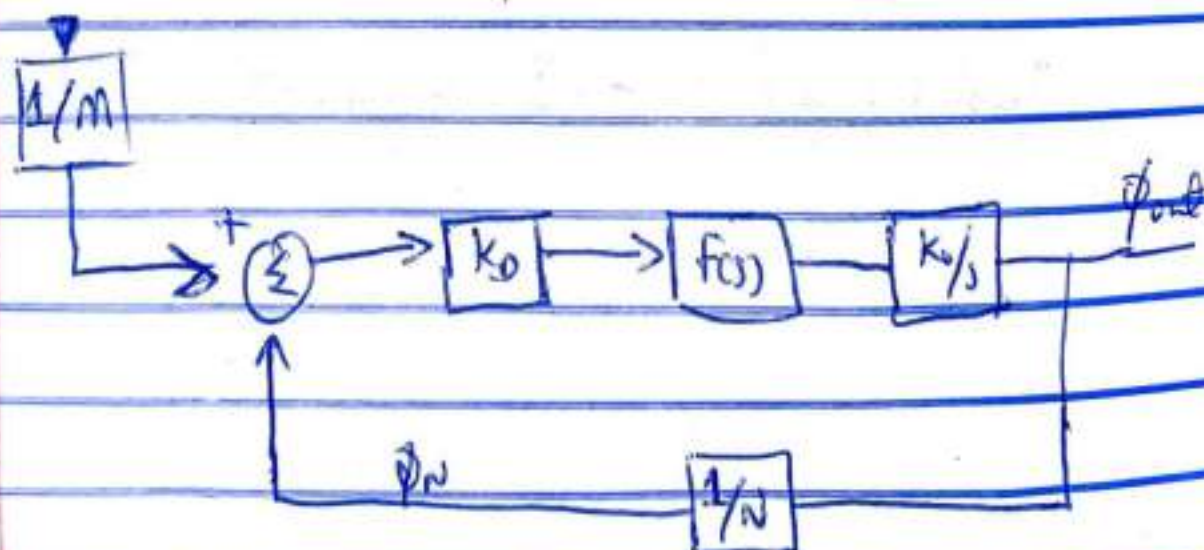Synthesizer PLL  $\rightarrow$  add the divider  $1/s$  to the feedback path.



Thus  $\frac{\phi_{in}}{\phi_{out}} = \frac{1}{N}$  and also,  $N = \frac{\omega_{out}}{\omega_{ref}}$



The open loop gain  $T(s) = \frac{k_v K_o F(s)}{N_s}$

Loop gain is reduced by a factor of  $N$ .

$$F(s) = \frac{1 + s/\omega_2}{s/\omega_1}$$

where  $\omega_1 = 1/R_1 C$      $\omega_2 = 1/R_2 C$

$$1 + T(s) = 1 + \frac{k_v}{N_s} \left( \frac{1 + s/\omega_2}{s/\omega_1} \right) = 0$$


$$1 + T(s) = \frac{N_s s^2}{k_v \omega_1} + \frac{s}{\omega_2} + \frac{1}{N_s} = 0$$

$$\omega_1 = \sqrt{\frac{k_v \omega_1}{N}} = \sqrt{\frac{k_v}{R_1 C N}}$$

$$\zeta = \frac{\omega_1}{2\omega_2} = \frac{R_2}{2} \sqrt{\frac{k_v C}{R_1 N}}$$



# Phase Frequency detector

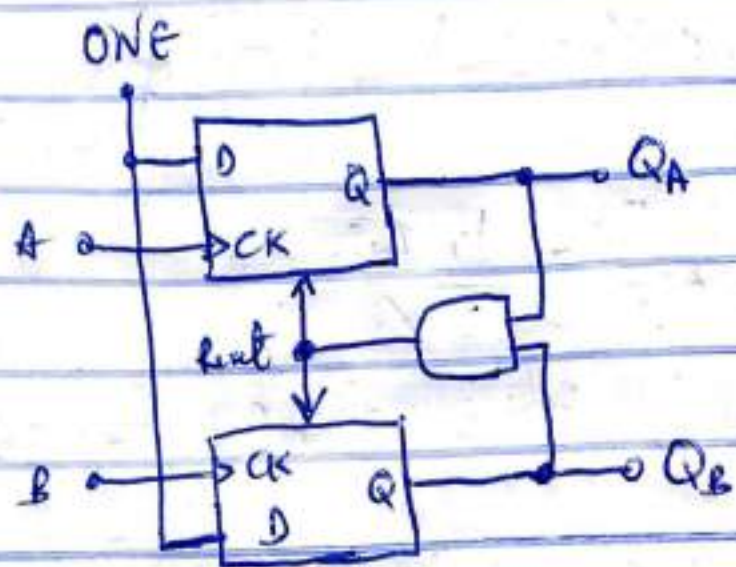



## Analog Multiplier

The emitter-coupled pair  $\Rightarrow$  simple multiplier.


If functions only 2 quadrants so it's called a two-quadrant multiplier

Gilbert multiplier cell allows 4-quadrant multiplication  
for Gilbert Multiplier:

- If  $V_1 < V_T$  and  $V_2 < V_T$  then it works as a multiplier
- If one input signal is large compared to  $V_T$ , then acts as a modulator
- If both inputs large: Non-saturating switches.

Gilbert cell as a balanced modulator

Video Tutorial

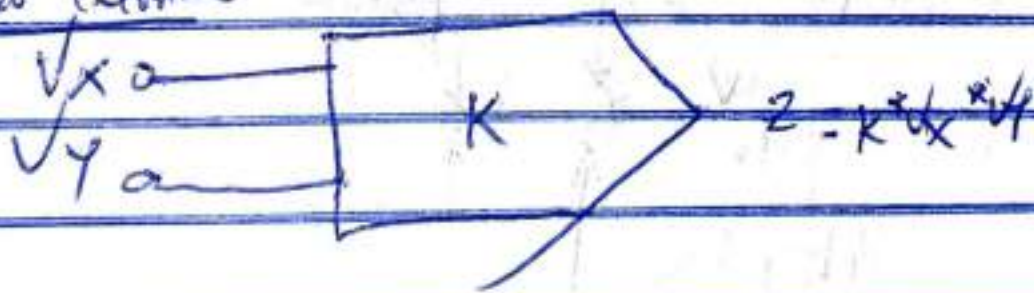

$$V_o = K V_1 V_2$$

Scaling factor  $\nearrow$   
Input signals  $\nearrow \nearrow$




Output is proportional to product of 2 input signals

Type	$V_x$	$V_y$	$V_o$
Single Quadrant	Unipolar	Unipolar	Unipolar
Two Quadrant	Bipolar	Unipolar	Bipolar
4 Quadrant	Unipolar	Bipolar	Bipolar
	Bipolar	Bipolar	Bipolar

Implementation: IC or discrete.

E.g. AD633  
Low cost multiplier

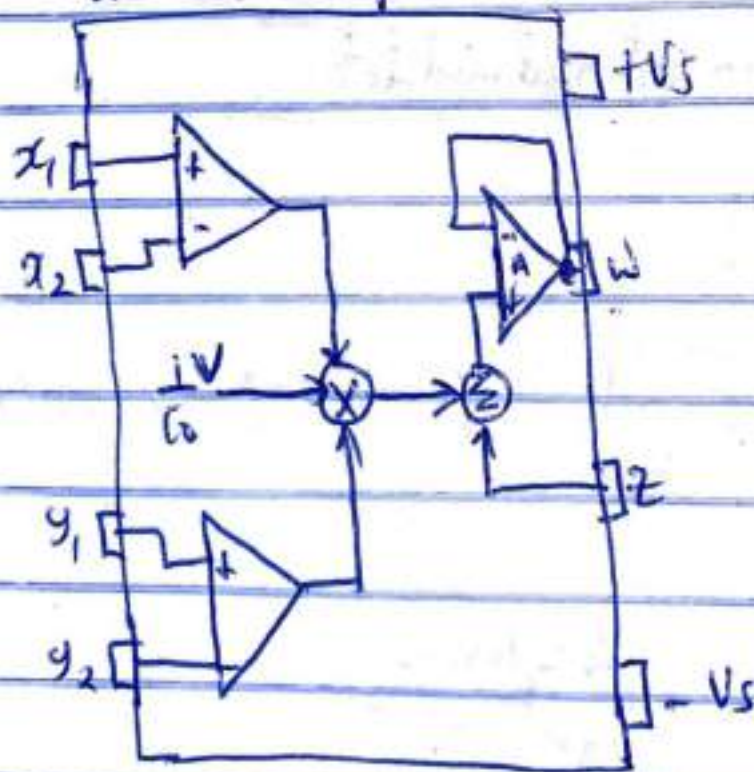

Characteristics  
 - 4 quadrant  
 - FS  $\approx 10V$   
 (full scale)

$$V_o = \left[ \frac{1}{10} (x_1 - x_2)(y_1 - y_2) \right] + z$$



### Important characteristics


- Accuracy = Total error (at Nominal Temperature  $T_{nom}$  and nominal voltage  $V_{s, nom}$ ) - % FS
  - DC offset ( $V_0$  for  $x=y=\phi$ )
  - Nonlinearity
- Dynamic performance
  - Small-signal bandwidth
  - Slew rate (max rate of change in op voltage)
  - Settling time

### Applications of analog multipliers

- Math operations
- Frequency doubling and shifting (i.e. mixers)
- Mod/Demod.

### Math Op's


#### Multiplication

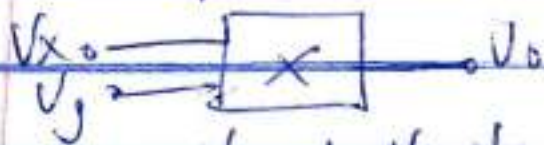

$$V_o = k \cdot V_x \cdot V_y$$




Spring

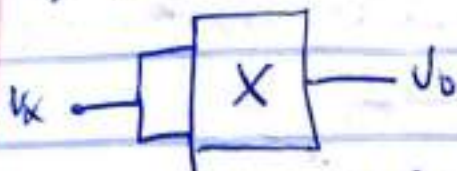

$$V_0 = k \cdot u_x^2$$

Division

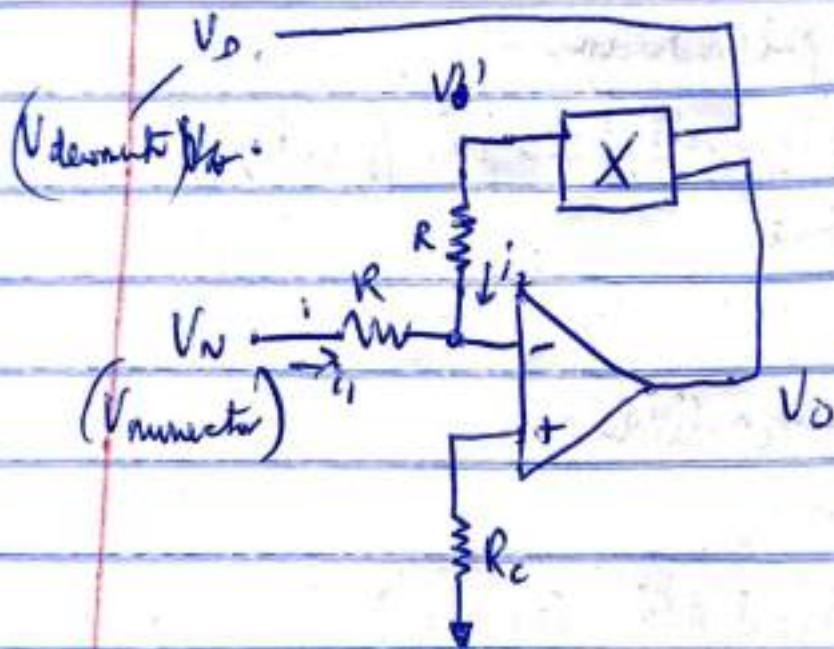

$$V_0' = k \cdot V_0 \cdot V_0$$

$$i_1 + i_2 = 0 \Rightarrow \frac{V_N}{R} + \frac{V_0'}{R} = 0$$


$$\Rightarrow V_N + V_0' = 0$$

$$-V_N = V_0'$$

$$V_0 \Rightarrow V_0 = \frac{V_0'}{k \cdot V_0} = -\frac{1}{k} \frac{V_N}{V_0}$$



Square root

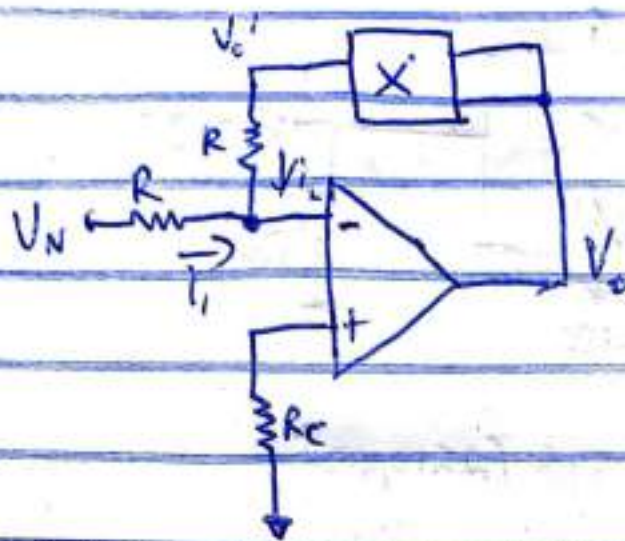

$$V_{o'} = k \cdot V_o^2$$

$$E_1 + i_2 = 0$$

$$\Rightarrow \frac{V_N}{R} + \frac{V_{o'}}{R} = 0$$


$$V_N + V_{o'} = 0$$

$$\Rightarrow V_{o'} = -V_N$$

$$V_o = \sqrt{\frac{V_{o'}}{k}} = \sqrt{\frac{-V_N}{k}}$$



Frequency divider.

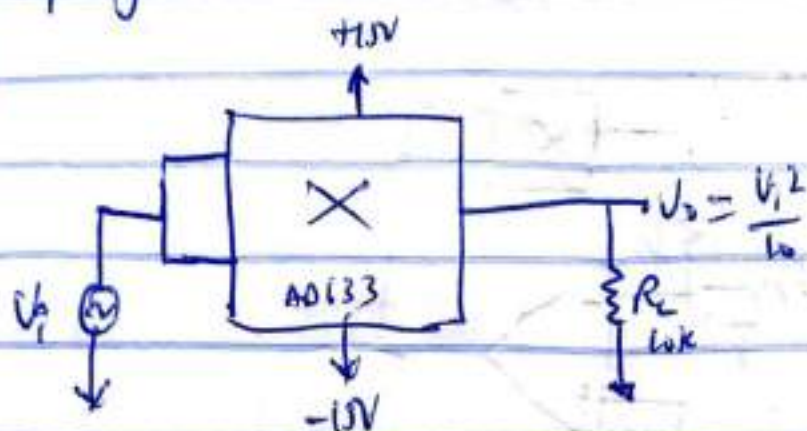

$$V_i = 5 \sin(2\pi 10,000 t)$$

$$\sin(A)\sin(B) = \frac{1}{2} [\cos(A-B) - \cos(A+B)]$$

$$V_o = \frac{V_i^2}{10}$$

$$= \frac{5^2}{10} [\sin(2\pi 10,000 t)]^2$$

$$V_o = 2.5 \left[ \frac{1}{2} (\cos 0) - \frac{1}{2} \cos(2\pi 20,000 t) \right]$$


Time the input  
frequency

$$V_o = \frac{2.5}{2} - \frac{2.5}{2} \cos(2\pi 20,000 t)$$

DC  
offset

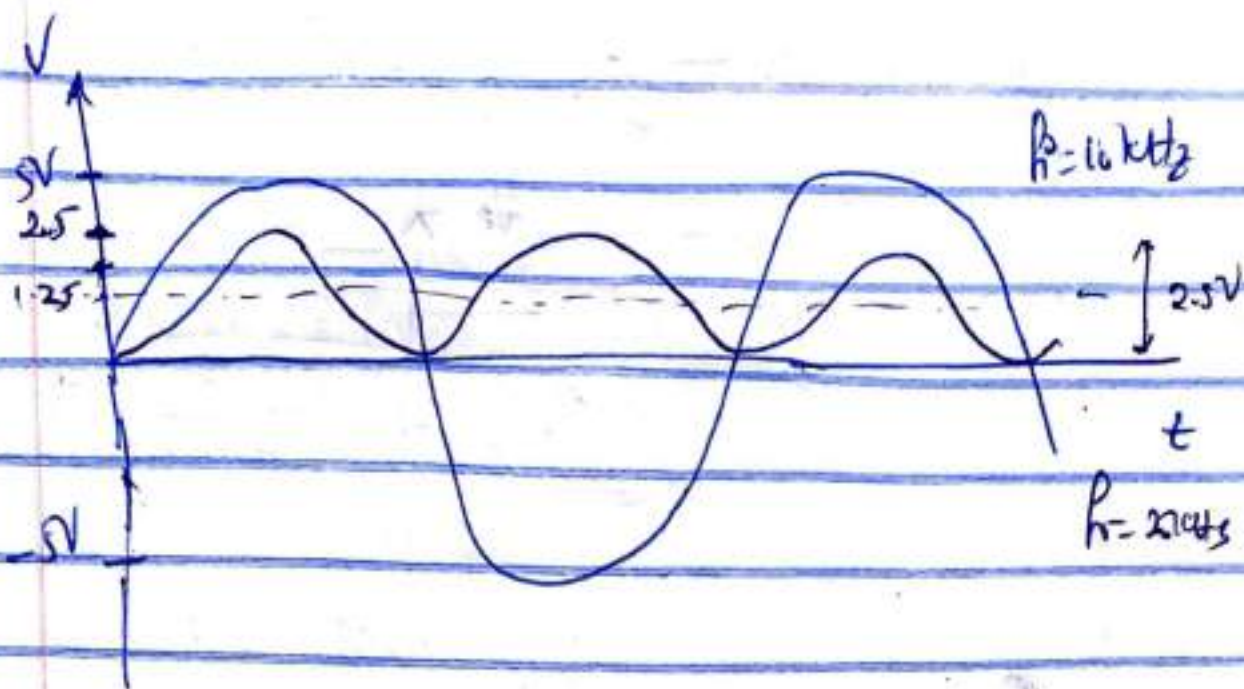Smallest of amplified  
 $1.25V$  and  $f = 20kHz$





### Modulators / Demodulators

**Modulators:** Vary properties of a periodic signal (carrier) with an information signal (modulating signal) to facilitate transmission.

**Demodulators:** Extract the original info signal from the modulated signal.

Modulation schemes  $\rightarrow$  AM, FM, PM.

Analog multiplies  $\rightarrow$  Amplitude Modulation

