

**MADUAGWUNA LOTANNA ONYEDIKACHUKWU**

**18/ENG04/081**

**EEE 316 CIRCUIT THEORY**

**ASSIGNMENT II**

PROBLEMA 10.11

1)  $R = 20 \text{ m}\Omega, L = 20 \text{ mH}, C = 5 \text{ nF}$

sol

2)  $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$   
 $= 10000 \text{ rad/s}$   
 $= 10 \text{ krads}$

admittance input

$Y = j\omega \cdot 1 + \frac{1}{\omega} + \frac{1}{2 + j\omega 2}$   
 $= 0.1 + j\omega \cdot 1 + \frac{1}{\omega} - \frac{j\omega 2}{4 + \omega^2}$

3)  $\omega_1 = \omega_0 = \frac{\beta}{2}$


At resonance  $\text{Im}(Y) = 0$  and

$\omega_0 \cdot 0.1 - \frac{2\omega_0}{4 + \omega_0^2} = 0$

$Q = \frac{R}{\omega_0 L} = \frac{20 \times 10^{-3}}{10000 \times 20 \times 10^{-3}} = 5$

$\omega_0 = 2000 \text{ rad/s}$

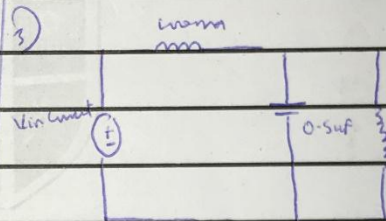$\beta = \frac{\omega_0}{Q} = \frac{10000}{5} = 2000$



$Z_L = j\omega L = j\omega(20 \times 10^{-3}) = j\omega \cdot 0.02$

$\omega_1 = \omega_0 \pm \frac{\beta}{2} = 10000 \pm 1000$

$\omega_1 = 9000 \text{ rad/s}$

$\omega_2 = \omega_0 + \frac{\beta}{2}$

$= 10000 + 1000 = 11000 \text{ rad/s}$


$Z_C = \frac{1}{j\omega C} = \frac{1}{j\omega(0.5 \times 10^{-9})}$

$= 101000 \text{ rad/s}$

$V = \frac{1}{j\omega 5 \times 10^{-4}} + \frac{1}{\omega} + j\omega \cdot 0.02$

$Q = 5, \beta = 2000 \text{ rad/s}$

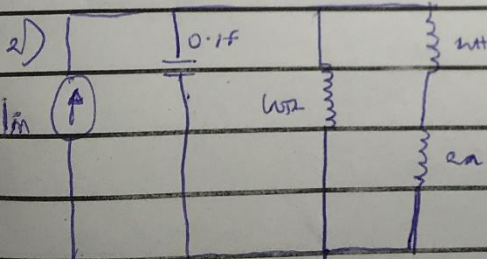$V = 0.2 + j\omega \cdot 0.02 + \frac{1}{j\omega 5 \times 10^{-4}}$



$V = 0.2 + j\omega \cdot 0.02 + \frac{1}{j\omega 5 \times 10^{-4}}$

At resonance  $\text{Im}(Y) = 0$

$\omega = j\omega 5 \times 10^{-4} - 0.2$

$\omega = 2.179 \text{ rad/s}$