

Tanarami KLUKAVORITSELA Adriel

171ENG051038

Mechatronics

EEE 322

1. A parallel resonant circuit has, $R = 100\text{K}\Omega$, $L = 20\text{mH}$
 $L = 20\text{mH}$ and $C = 5\text{nF}$. Calculate ω_0 , ω_1 , ω_2 , Q and B
 $R = 100\text{K}\Omega$, $L = 20\text{mH}$, $C = 5\text{nF}$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3}) \times (5 \times 10^{-9})}} = \frac{1}{\sqrt{1 \times 10^{-10}}}$$

$$= 100000 \text{ rad/s} = 100\text{K rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100 \times 10^3) (20 \times 10^{-3})} = 50$$

$$Q = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 = 2\text{K rad/s}$$

$$\text{Since } Q > 1.0, \omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2000}{2}$$
$$= 100 \times 10^3 - 1000 = 99000$$


$$\omega_1 = 99\text{K rad/s}$$

$$\omega_2 = \omega_0 + \frac{B_p}{2} = 100 \times 10^3 + \frac{2000}{2}$$

$$= 100 \times 10^3 + 1000$$

$$= 101000$$

$$\omega_2 = 101 \text{ K rad/s}$$

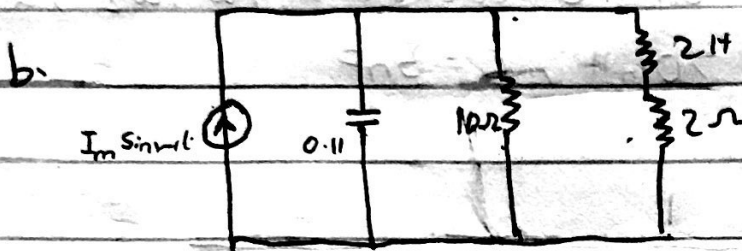

$$Y = \frac{1}{10} + j\omega \cdot 0.11 + \frac{1}{2 + j4\omega} = 0.1 + j\omega \cdot 0.11 + \frac{1}{2 + j4\omega^2}$$

Rationalizing $\frac{1}{2 + j4\omega^2} = \frac{1}{2 + j4\omega^2} \times \frac{2 - j4\omega^2}{2 - j4\omega^2} = \frac{2 - j4\omega^2}{4 - 4j^2\omega^4 + 16\omega^4}$

$$= \frac{2 - j4\omega^2}{4 + 4\omega^4}$$

$$Y = 0.1 + j\omega \cdot 0.11 + \frac{2 - j4\omega^2}{4 + 4\omega^4} = 0.1 + j\omega \cdot 0.11 + \frac{2}{4 + 4\omega^4} - \frac{j4\omega^2}{4 + 4\omega^4}$$

$$Y = 0.1 + \frac{2}{4 + 4\omega^4} + j\omega \cdot 0.11 - \frac{j4\omega^2}{4 + 4\omega^4} = 0.1 + \frac{2}{4 + 4\omega^4} + j(\omega \cdot 0.11 - \frac{\omega^2}{1 + \omega^4})$$

At resonance, $I_n(Y) = 0$

Therefore, $\omega_0 \cdot 0.11 - \frac{\omega_0^2}{1 + \omega_0^4} = 0$

$$0.1 - \frac{2}{4 + 4\omega_0^2} = 0$$

$$0.1 = \frac{2}{4 + 4\omega_0^2}$$


$$0.4 + 0.4\omega_0^2 = 2$$

$$0.4\omega_0^2 = 1.6$$

$$\omega_0^2 = 4$$

$$\sqrt{\omega_0^2} = \sqrt{4}$$

$$\omega_0 = 2 \text{ rad/s}$$

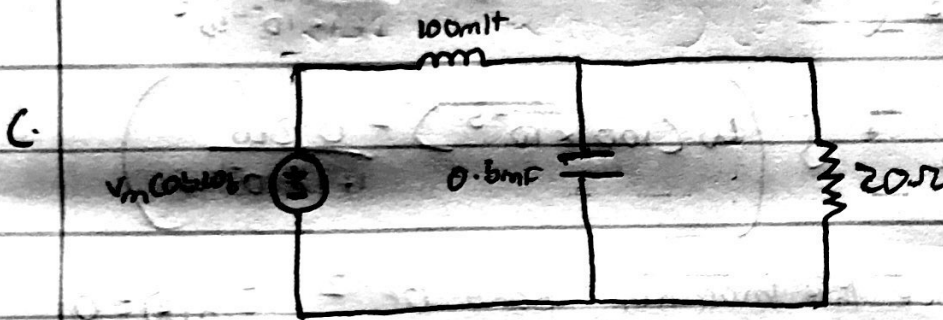

$$Z = j\omega(100 \times 10^{-3}) + \left(\frac{-20}{j\omega(0.5 \times 10^{-3})} \right) = \left(\frac{20}{1} + \frac{1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \right) = \left(\frac{0.01j\omega + 1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \times \frac{j\omega(0.5 \times 10^{-3})}{0.1j\omega + 1} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{0.01j\omega + 1} \right)$$

Rationalizing $\frac{20}{0.01j\omega + 1} = \frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1}$

$$= \frac{j\omega \cdot 2 - 20}{-1 \times 10^{-4} \omega^2 - j\omega \cdot 0.01 + j\omega \cdot 0.01 + 1}$$

$$= \frac{j\omega \cdot 2 - 20}{-1 \times 10^{-4} \omega^2 - 1} = \frac{-20 + j\omega \cdot 2}{-1 \times 10^{-4} \omega^2 - 1}$$

$$= \frac{+(20 - 0.2j\omega)}{+(1 \times 10^{-4} \omega^2 + 1)} = \frac{20 - 0.2j\omega}{1 + 1 \times 10^{-4} \omega^2} = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + \frac{j\omega \cdot 0.2}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = j\omega (100 \times 10^{-3}) + \frac{20}{1 + 1 \times 10^{-4} \omega^2} - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega (100 \times 10^{-3}) - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j \left(\omega (100 \times 10^{-3}) - \frac{0.2\omega}{1 + 1 \times 10^{-4} \omega^2} \right)$$

At resonance the imaginary part of Z, $\text{Im}(Z) = 0$

$$= \omega_0 (100 \times 10^{-3}) - \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = 0$$

$$\omega_0 (100 \times 10^{-3}) = \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

Cross multiply

$$\omega_0 (100 \times 10^{-3}) (1 + 1 \times 10^{-4} \omega_0^2) = 0.2\omega_0$$

$$= 0.1 + 1 \times 10^{-5} \omega_0^2 = 0.2$$

$$= 1 \times 10^{-5} \omega_0^2 = 0.2 - 0.1$$

$$\omega_0^2 = \frac{0.1}{1 \times 10^{-5}}$$

$$\omega_0^2 = 10000$$

$$\omega_0 = \sqrt{10000} = 100 \text{ rad/s}$$