

Ogeme Selby Uduochi

Set 1

17/Eng 04/052

Electrical/Electronics

Course EEE322

① A parallel resonant circuit has,  $R=100k\Omega$ ,  $L=20mH$  and  $C=5nF$ . Calculate  $\omega_1$ ,  $\omega_2$  and  $B$   
 $R=100k\Omega$ ,  $L=20mH$ ,  $C=5nF$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} (5 \times 10^{-9})}} = \frac{1}{\sqrt{1 \times 10^{-10}}}$$

$$= 100000 \text{ rad/s}$$

$$\omega_0 = 100k \text{ rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100 \times 10^3) (20 \times 10^{-3})} = \frac{1}{2 \times 10^{-3}}$$

$$= 50$$

$$Q = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 = 2k \text{ rad/s}$$

Since  $Q > 10$ ,  $\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2000}{2}$

$$= (100 \times 10^3) - 1000 = 99000$$

$$\omega_1 = 99k \text{ rad/s}$$


$$\omega_2 = \omega_0 + \frac{B}{2} = (100 \times 10^3) + \frac{2000}{2}$$

$$= 100 \times 10^3 + 1000$$

$$= 101000$$

$$\omega_2 = 101 \text{ Krad/s}$$

⑥

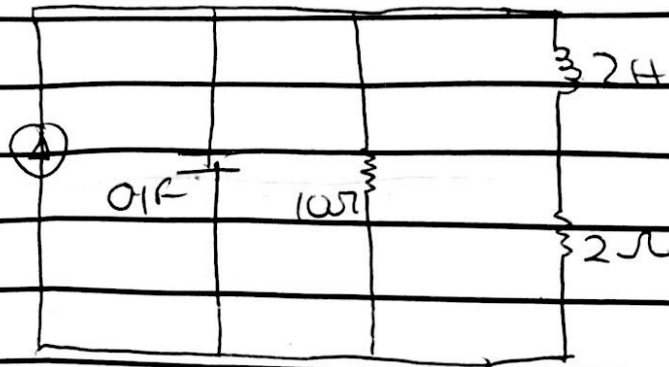

$$Y = \frac{1}{10} + j\omega \cdot 0.1 + \frac{1}{2 + j\omega^2} = 0.1 + j\omega \cdot 0.1 + \frac{1}{2 + j\omega^2}$$

$$\begin{aligned} \text{Rationalizing } \frac{1}{2 + j\omega^2} &= \frac{1}{2 + j\omega^2} \times \frac{2 - j\omega^2}{2 - j\omega^2} \\ &= \frac{2 - j\omega^2}{4 - 4j\omega^2 + 4j\omega^2 - 4\omega^2} \\ &= \frac{2 - j\omega^2}{4 + 4\omega^2} \end{aligned}$$

$$Y = 0.1 + \frac{2 - j\omega^2}{4 + 4\omega^2} = 0.1 + \frac{2}{4 + 4\omega^2} + \frac{-j\omega^2}{4 + 4\omega^2}$$

$$Y = 0.1 + \frac{2}{4 + 4\omega^2} + \frac{j\omega \cdot 0.1 - j\omega^2}{4 + 4\omega^2} = 0.1 + \frac{2}{4 + 4\omega^2} + \frac{j(\omega \cdot 0.1 - \omega^2)}{4 + 4\omega^2}$$

At resonance  $\text{Im}(Y) = 0$

$$\text{Therefore } \frac{\omega \cdot 0.1 - \omega^2}{4 + 4\omega^2} = 0$$

$$0.1 - \omega = 0$$

$$0.1 = \omega$$


$$0.4 + 0.4 \omega^2 = 2$$

$$0.4 \omega^2 = 1.6$$

$$\omega^2 = 4 \quad \sqrt{\omega^2} = \sqrt{4}$$

$$\omega = 2$$

$$\omega_0 = 2 \text{ rad/s}$$

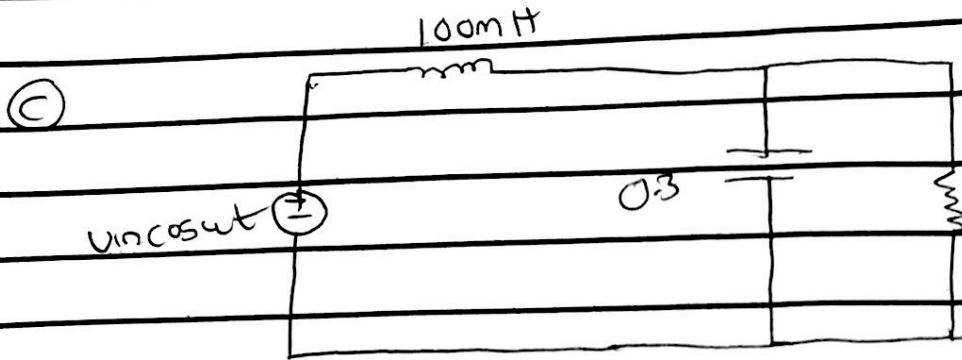

$$Z = j\omega 100 \times 10^{-3} + \left( \frac{20}{j\omega 0.5 \times 10^{-3}} \right) \div \left( \frac{20 + 1}{1 \quad 0.5 \times 10^{-3} j\omega} \right)$$

$$Z = j\omega 100 \times 10^{-3} + \left( \frac{20}{j\omega 0.5 \times 10^{-3}} \right) \div \left( \frac{0.01j + 1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega (100 \times 10^{-3}) + \frac{20}{j\omega 0.5 \times 10^{-3}} \div \left( \frac{0.01j\omega + 1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega (100 \times 10^{-3}) + \left( \frac{20}{j\omega 0.5 \times 10^{-3}} \right) \times \frac{j\omega (0.5 \times 10^{-3})}{0.01j\omega + 1}$$

$$= j\omega (100 \times 10^{-3}) + \left( \frac{20}{0.01j\omega + 1} \right)$$

Rationalizing  $\frac{20}{0.01j\omega + 1} = \frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1}$

$$= j\omega (0.2 - 20)$$

$$\frac{-1 \times 10^{-4} \omega^2 - j\omega 0.01 + j\omega 0.01 - 1}{-1 \times 10^{-4} \omega^2 - 1}$$

$$= j\omega (0.2 - 20)$$

$$= \frac{20}{-1 \times 10^{-4} \omega^2 - 1}$$

$$\frac{-1 \times 10^{-4} \omega^2 - 1}{-1 \times 10^{-4} \omega^2 - 1}$$

$$= \frac{20 - 0.2j\omega}{(1 \times 10^{-4}\omega^2 + 1) (1 + 1 \times 10^{-4}\omega^2)}$$

$$= \frac{20}{(1 \times 10^{-4}\omega^2 + 1)} + \frac{j\omega (0.2)}{(1 + 1 \times 10^{-4}\omega^2)}$$

$$Z = \frac{j\omega (100 \times 10^{-3}) + 20}{(1 + 1 \times 10^{-4}\omega^2) (1 + 1 \times 10^{-4}\omega^2)} - 0.2j\omega$$

$$Z = \frac{20}{(1 + 1 \times 10^{-4}\omega^2)} + \frac{j\omega (100 \times 10^{-3}) - 0.2j\omega}{(1 + 1 \times 10^{-4}\omega^2)}$$

$$Z = \frac{20}{(1 + 1 \times 10^{-4}\omega^2)} + \frac{j\omega (100 \times 10^{-3}) - 0.2j\omega}{(1 + 1 \times 10^{-4}\omega^2)}$$

At resonance ~~the imaginary part of Z~~ the imaginary part of Z

$$\text{Imf } Z = 0$$

$$\frac{\omega (100 \times 10^{-3}) - 0.2\omega}{(1 + 1 \times 10^{-4}\omega^2)} = 0 \quad 3.4 \rightarrow 3.5$$

$$\frac{\omega (100 \times 10^{-3})}{(1 + 1 \times 10^{-4}\omega^2)} = 0.2\omega$$

Cross multiply

$$\omega (100 \times 10^{-3}) (1 + 1 \times 10^{-4}\omega^2) = 0.2\omega (1 + 1 \times 10^{-4}\omega^2)$$

$$= 0.1 + 1 \times 10^{-5}\omega^2 = 0.2$$

$$= 1 \times 10^{-5} \omega^2 = 0.2 - 0.1$$

$$\omega^2 = \frac{0.1}{1 \times 10^{-5}}$$

$$\omega^2 = 10000$$

$$\omega = \sqrt{10000} = 100 \text{ rad/s}$$