

Collins David - C
 17/10/2010
 Mechanics

A

$$Q1 \quad R = \omega \omega R = 1 \times 10^5 \Omega$$

$$L = 20 \text{ mH} = 2 \times 10^{-2} \text{ H}$$

$$C = 5 \text{ nF} = 5 \times 10^{-9} \text{ F}$$

$$i \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-2}) (5 \times 10^{-9})}}$$

$$= \frac{1}{10 \times 10^{-6}}$$

$$= 10^5$$

$$= 100 \text{ k rad/s}$$

$$b \quad Q = \frac{R}{\omega_0 L} = 100,000$$

$$= \frac{100,000 \times 20 \times 10^{-7}}{20}$$

$$= 100$$

$$= 0.05 \times 10^3$$

$$= 50$$

$$C \quad \beta = \omega_0 = \omega_0 \times \omega_0^3 = 2k \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{\beta}{2} = 100000 - \frac{2000}{2}$$

$$= 99,000 = 99k \text{ rad/s}$$

$$\omega_2 = \omega_0 + \frac{\beta}{2} = 100000 + \frac{2000}{2}$$

$$= 101k \text{ rad/s}$$

Q Input admittance is

$$Y = j\omega_0^{-1} + \frac{1}{10} + \frac{1}{2 + j\omega_0 2}$$

$$= 0.1 + j\omega_0^{-1} + \frac{2 - j\omega_0 2}{4 + 4\omega_0^2}$$

at resonance


$$\text{Im}(Y) = 0$$

$$\therefore \omega_0 \cdot 0.1 = 2\omega_0 = 0$$

$$2 + \omega_0^2 = 0$$

$$\omega_0 = 2 \text{ rad/s}$$

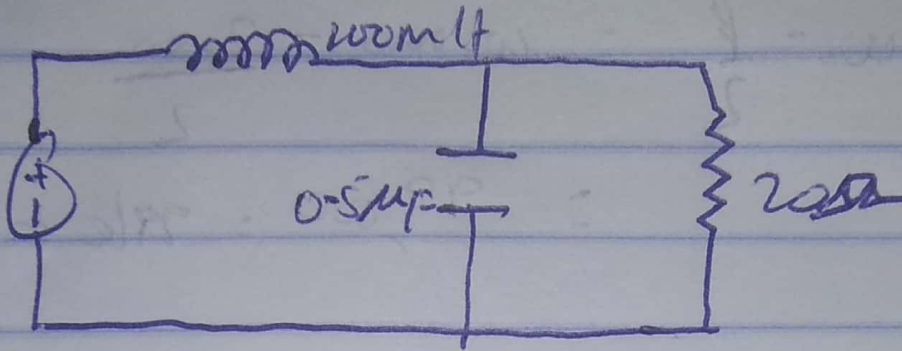Q3 The resonance frequency of the circuit below,



$$\frac{20 + \frac{200}{j\omega}}{20 + \frac{200}{j\omega}} = \frac{400\omega}{20j\omega + 200} = \frac{400\omega}{20j\omega + 200} + \frac{(20j\omega - 200)}{(20j\omega - 200)}$$

$$= 80000j\omega - 80 \times 10^6 + 200j\omega - 40000$$

A resonance if the imaginary part at $\omega = 0$

$$\frac{80 \times 10^4 j\omega}{-400j\omega - 40 \times 10^5} + j\omega(100 \times 10^{-5})$$

$$-80 \times 10^4 \omega + (-40\omega^2) - 40 \times 10^4 \omega$$

$$-40\omega^2 - 40 \times 10^4$$

$$\omega^2 = 10000$$

$$\omega = \sqrt{\omega_0^2}$$

$$\omega = \omega_0 \text{ rad/s} ,$$