

# EZEGBINI CLEMENTINA ONYINYECHUKWU

17/ENG024/027

→ Electrical Circuit Theory II (EEE 322)

Assignment II

i) Given:  $C = 5 \text{ nF} = 5 \times 10^{-9} \text{ F}$ ,  $R = 100 \text{ k}\Omega = 100 \times 10^3 \Omega$ ,  
 $L = 20 \text{ mH} = 20 \times 10^{-3} \text{ H}$

→ Using,  $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\therefore \omega_0 = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}} = 100000 \text{ rad/s} \approx \underline{\underline{100 \text{ krad/s}}}$$

$$\Rightarrow Q = \frac{R}{\omega_0 \times L} = \frac{100 \times 10^3}{100 \times 10^3 \times 20 \times 10^{-3}}$$

$$Q = \underline{\underline{50}}$$

$$\Rightarrow B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 \approx 2 \text{ krad/s}$$

$$\Rightarrow \omega_1 = \omega_0 - \frac{B}{2}$$


$$\omega_1 = 100 \times 10^3 - \frac{2 \times 10^3}{2} = 99000 \text{ rad/s} \approx 99 \text{ krad/s}$$



$$\Rightarrow \omega_2 = \omega_0 + \frac{B}{2}$$

$$\omega_2 = 1000 \times 10^3 + \frac{2 \times 10^3}{2} = 101000 \text{ rad/s} \\ \approx \underline{\underline{101 \text{ Krad/s}}}$$

ii)

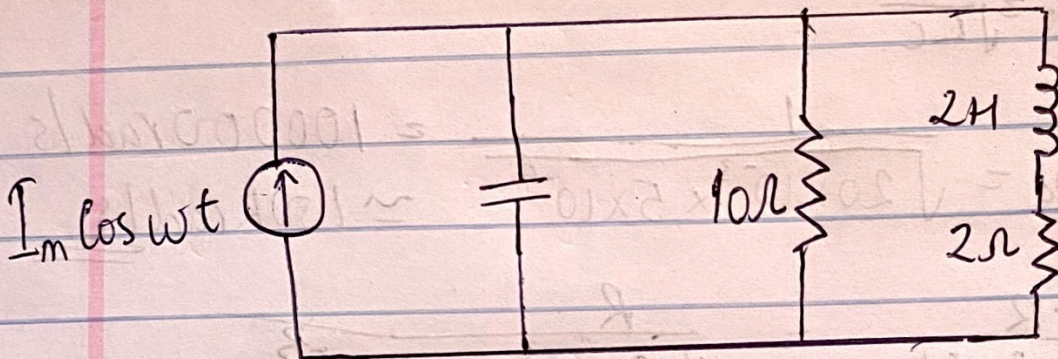

The input admittance is given

$$Y = j\omega \cdot 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2}$$

$$-0.1 + j\omega \cdot 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

$\Rightarrow$  At resonance

$$\text{Im}(Y) = 0$$

$$\omega_0 \times 0.1 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0 \Rightarrow \underline{\underline{\omega_0 = 2 \text{ rad/s}}}$$



$$0.1 = \frac{2}{4 + 4\omega_0^2}$$

$$0.4 + 0.4\omega_0^2 = 2$$


$$0.4\omega_0^2 = 1.6$$

$$\omega_0^2 = 4$$

$$\sqrt{\omega_0^2} = \sqrt{4}$$

$$\omega_0 = 2 \text{ rad/s}$$

ii)

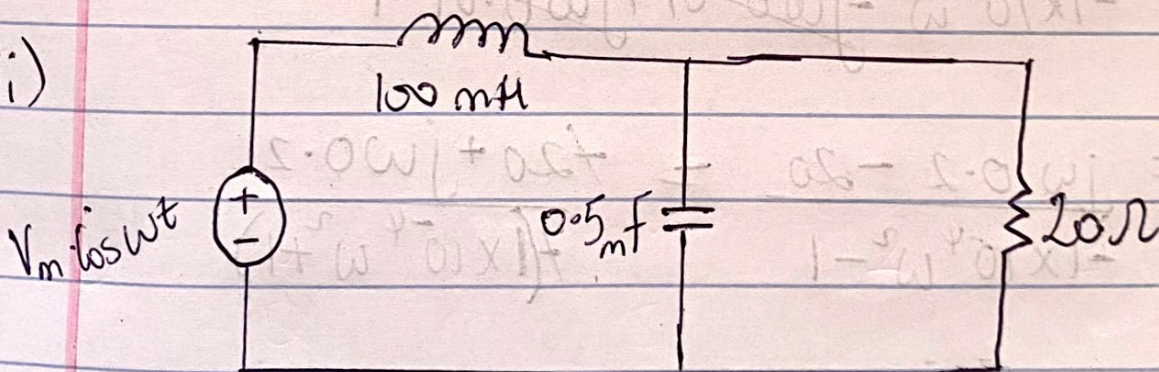

8025 resonant frequency = ?

$$Z = j\omega 100 \times 10^{-3} + \left[ \frac{20}{j\omega (0.5 \times 10^{-3})} \right] = \left( \frac{20}{1} + \frac{1}{0.5 \times 10^{-3} j\omega} \right)$$

$$Z = j\omega (100 \times 10^{-3}) + \left( \frac{20}{j\omega (0.5 \times 10^{-3})} \right) = \frac{(0.01j\omega + 1)}{(0.5 \times 10^{-3} j\omega)}$$



$$Z = j\omega(100 \times 10^{-3}) + \left( \frac{20}{j\omega(0.5 \times 10^{-3})} \times \frac{j\omega(0.5 \times 10^{-3})}{0.01j\omega + 1} \right)$$

$$Z = j\omega(100 \times 10^{-3}) + \left( \frac{20}{0.01j\omega + 1} \right)$$

$$\frac{20}{0.01j\omega + 1} \quad (\text{find its conjugate})$$

$$\frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1}$$

$$Z = \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - j\omega 0.01 + j\omega 0.01 - 1}$$

$$Z = \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - 1} = \frac{-20 + j\omega 0.2}{1 \times 10^{-4} \omega^2 + 1}$$

$$Z = \frac{20 - 0.2j\omega}{1 \times 10^{-4} \omega^2 + 1} = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + \frac{-j\omega 0.2}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = j\omega(100 \times 10^{-3}) + \frac{20}{1 + 1 \times 10^{-4} \omega^2} - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$



$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega(100 \times 10^{-3}) - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j \left( \omega(100 \times 10^{-3}) - \frac{0.2\omega}{1 + 1 \times 10^{-4} \omega^2} \right)$$

→ (a) Resonance The imaginary part of  $Z = 0$

$$\text{Therefore: } Z = \omega_0(100 \times 10^{-3}) - \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = 0$$

$$\omega_0(100 \times 10^{-3}) = \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

$$\cancel{\omega_0}(100 \times 10^{-3})(1 + 1 \times 10^{-4} \omega_0^2) = 0.2 \cancel{\omega_0}$$

$$\Rightarrow 0.1 + 1 \times 10^{-5} \omega_0^2 = 0.2$$

$$\Rightarrow 1 \times 10^{-5} \omega_0^2 = 0.2 - 0.1$$

$$\omega_0^2 = \frac{0.1}{1 \times 10^{-5}} = 10000$$

$$\sqrt{\omega^2} = \sqrt{10000} \Rightarrow \omega_0 = \underline{\underline{100 \text{ rad/s}}}$$