

Q. 18/ENGG04/082

18/ENGG04/082

Circuit Theory

A parallel resonant circuit has  $R = 100 \text{ k}\Omega$ ,  $L = 20 \text{ mH}$   
 &  $C = 5 \text{ nF}$ . Calculate  $\omega_0$ ,  $\omega_1$ ,  $\omega_2$  &  $B$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3})(5 \times 10^{-9})}} = 100000 \text{ rad/s}$$

$\omega_0 = 100 \text{ krad/s}$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100000)(20 \times 10^{-3})} = \frac{1}{20 \times 10^{-3}} = 50$$

$$B = \omega_0 \cdot Q = \frac{100 \times 10^3}{50} = 2000 = 2 \text{ krad/s}$$

Since  $Q > 10$ ,  $\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2000}{2}$


$$= 99000$$

$\omega_1 = 99 \text{ krad/s}$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2000}{2}$$
$$= 100 \times 10^3 + 1000$$
$$= 101000$$

$\omega_2 = 101 \text{ krad/s}$

(b)

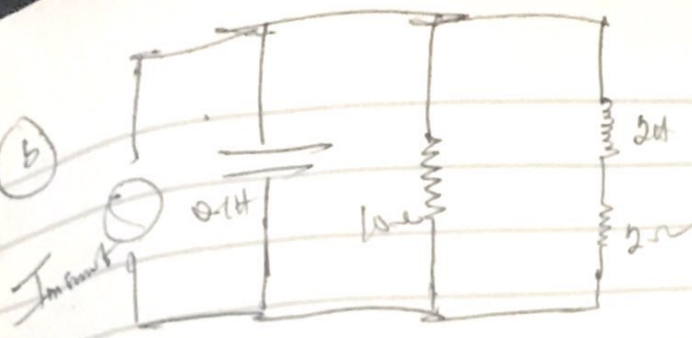

$$Y = \frac{1}{10} + j\omega \cdot 0.1 + \frac{1}{2+j\omega 2} = 0.1 + j\omega \cdot 0.1 + \frac{1}{2+j\omega 2}$$

Rationalizing

$$\frac{1}{2+j\omega 2} = \frac{1}{2+j\omega 2} \times \frac{2-j\omega 2}{2-j\omega 2} = \frac{2-j\omega 2}{4-j\omega 4+j\omega 4+\omega^2 4}$$

$$= \frac{2-j\omega 2}{4+4\omega^2}$$

$$Y = 0.1 + j\omega \cdot 0.1 + \frac{2-j\omega 2}{4+4\omega^2} = 0.1 + j\omega \cdot 0.1 + \frac{2}{4+4\omega^2} - \frac{j\omega 2}{4+4\omega^2}$$

$$Y = 0.1 + \frac{2}{4+4\omega^2} + j\omega \cdot 0.1 - \frac{j\omega 2}{4+4\omega^2} = 0.1 + \frac{2}{4+4\omega^2} + j \left( \omega \cdot 0.1 - \frac{\omega 2}{4+4\omega^2} \right)$$

At resonance  $I = (Y) = 0$

$$\omega \cdot 0.1 - \frac{\omega 2}{4+4\omega^2} = 0$$

$$0.1 - \frac{2}{4+4\omega^2} = 0$$

$$0.1 = \frac{2}{4+4\omega^2}$$

$$0.4 + 0.4\omega^2 = 2$$


$$0.4\omega^2 = 1.6$$

$$\omega^2 = 4$$

$$\omega = 2$$

$$\omega = 2 \text{ rad/s}$$

(c)

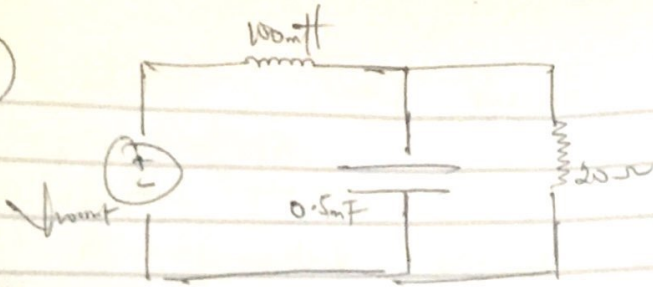

$$Z = j\omega 100 \times 10^{-3} + \left( \frac{20}{j\omega(0.5 \times 10^{-3})} + \left( \frac{20}{1} + \frac{1}{0.5 \times 10^{-3} j\omega} \right) \right)$$

$$= j\omega(100 \times 10^{-3}) + \left( \frac{20}{j\omega(0.5 \times 10^{-3})} + \left( \frac{0.01j\omega + 1}{0.5 \times 10^{-3} j\omega} \right) \right)$$

$$= j\omega(100 \times 10^{-3}) + \left( \frac{20}{j\omega(0.5 \times 10^{-3})} \times \frac{j\omega(0.5 \times 10^{-3})}{0.01j\omega + 1} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left( \frac{20}{0.01j\omega + 1} \right)$$

Partial fractioning  $\frac{20}{0.01j\omega + 1} = \frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1}$

$$= \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - j\omega 0.01 + j\omega 0.01 - 1}$$

$$= \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - 1}$$

$$= \frac{-(20 - 0.2j\omega)}{-(1 \times 10^{-4} \omega^2 + 1)} = \frac{20 - 0.2j\omega}{1 + 1 \times 10^{-4} \omega^2} = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega \frac{0.2}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega(100 \times 10^{-3}) - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j \left( \omega(100 \times 10^{-3}) - \frac{0.2\omega}{1 + 1 \times 10^{-4} \omega^2} \right)$$

At resonance  $\omega_0(100 \times 10^{-3}) - \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = 0$

$$\omega_0(100 \times 10^{-3}) = \frac{0.2\omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

$$\omega_0 (100 \times 10^{-3}) (141 \times 10^{-4} \omega_0) = 0.2 \text{ W} \\
1 \times 10^{-5} \omega_0^2 = 0.2 - 0.1 \\
\omega_0^2 = 0.1$$

$$\frac{0.1}{1 \times 10^{-5}}$$

$$\omega_0^2 = 10000$$

$$\omega_0 = \sqrt{10000}$$

$$\omega_0 = 100 \text{ rad/s}$$