

$$i) R = 100 \times 10^3 \Omega \quad L = 20 \times 10^{-3} \text{ H} \quad C = 5 \times 10^{-9} \text{ F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$

$$\omega_0 = 100000 \text{ rad/s} = 100 \text{ K rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{100000 \times 20 \times 10^{-3}} = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100000}{50} = 2000 \text{ rad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100000 - \frac{2000}{2}$$

$$= 99000 = 99 \text{ K rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100000 + \frac{2000}{2}$$

$$= 101000 = 101 \text{ K rad/s}$$

$$ii) C = 0.1 \text{ F}$$

$$R = 10 \Omega \quad L = 2 \text{ H}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{2 \times 0.1}}$$

$$= 2.2 \text{ rad/s}$$

$$\text{iii) } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$L = 100 \times 10^{-3} \text{ H} \quad C = 0.5 \times 10^{-3} \text{ F}$$

$$\omega_0 = \frac{1}{\sqrt{100 \times 10^{-3} \times 0.5 \times 10^{-3}}}$$

$$\approx 141.4 \text{ rad/s}$$