

EMMANUEL EHEGBE

17/ENG 02/020

COMPUTER ENGINEERING

i) A parallel resonant circuit has  $R = 100 \text{ k}\Omega$ ,  $L = 20 \text{ mH}$ ,  $C = 5 \text{ nF}$ . Calculate  $\omega_0$ ,  $\omega_1$ ,  $\omega_2$  &  $Q$ .

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3}) \times (5 \times 10^{-9})}} = 100 \text{ krad/s}^{-1}$$

$$\rightarrow B = \frac{\omega_0}{Q} = \frac{1}{RC} = \frac{1}{100 \times (5 \times 10^{-9})} = 2 \text{ krad/s}^{-1}$$

from above  $\omega_0 = 100 \text{ krad/s}^{-1}$  &  $B = 2 \text{ krad/s}^{-1}$

$$\therefore Q = \frac{\omega_0}{B} = \frac{100 \times 10^3}{2 \times 10^3} = 50$$

Since  $Q \geq 10$


$$\rightarrow \omega_1 = \omega_0 - B/2 = 100 \times 10^3 - 2 \times 10^3/2 = 99 \text{ krad/s}$$

$$\omega_2 = \omega_0 + B/2 = 100 \times 10^3 + 2 \times 10^3/2 = 101 \text{ krad/s}$$

ii) Determine the resonant frequency of the circuit

below

$1 \text{ m} \cos \omega t$

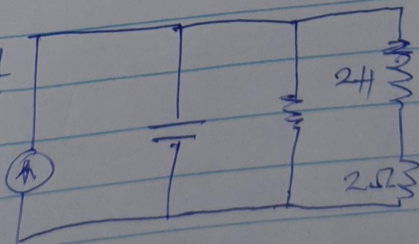

The input admittance is  $Y = j\omega \cdot 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2}$

$$= 0.1 + j\omega \cdot 0.1 + 2 - \frac{j\omega 2}{4 + 4\omega^2}$$


at resonance

$$\text{Im}(Y) = 0$$

$$\omega \cdot 0.1 = \frac{2\omega}{4 + 4\omega^2} = 0$$

$$\omega_0 = 2 \text{ rad s}^{-1}$$

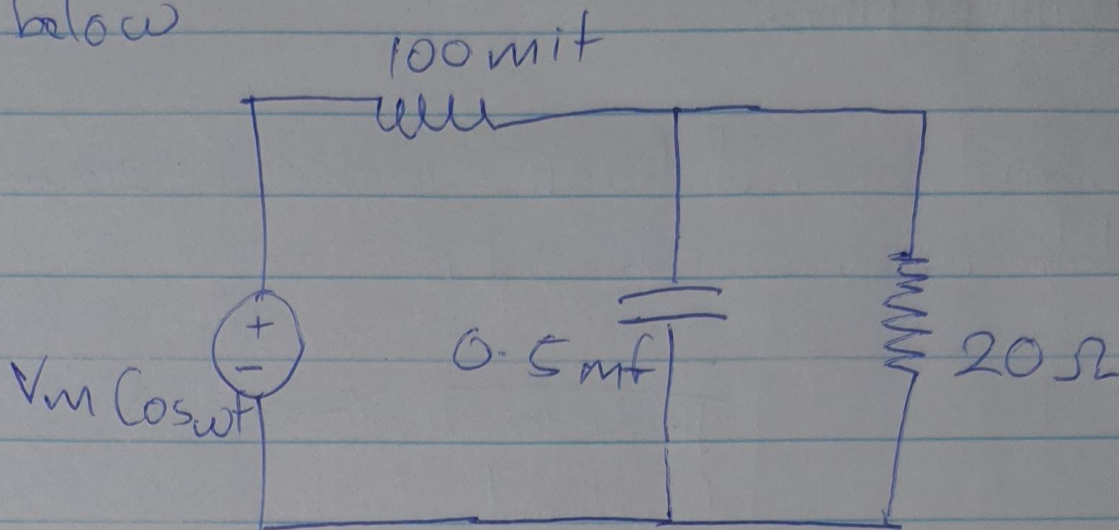iii Calculate the resonant frequency of the circuit below



At resonance of the imaginary part at  $\omega = 0$

$$\underline{80,000j\omega} + \underline{j\omega(100 \times 10^{-3})}$$

$$-400j\omega - 4000000$$

$$= 80000\omega + [-40\omega^2] - 400000$$

$$= 4000000 - 40\omega^2 = 0$$

$$-40\omega^2 = -400000$$

$$\omega^2 = \underline{\underline{-400000}}$$

$$-40 = 10000$$

$$\omega = \sqrt{10000} = 100 \text{ rad s}^{-1}$$