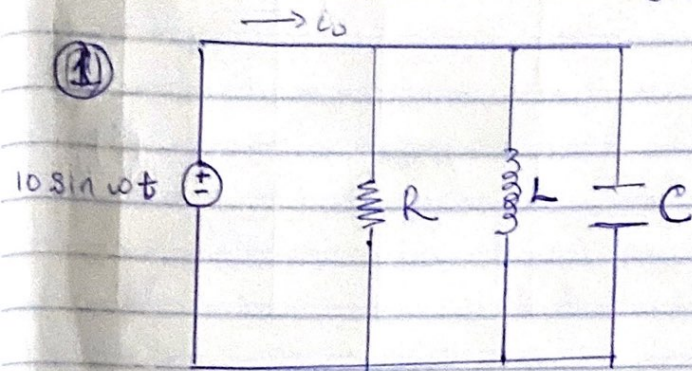


Bakare Sharafadeen omogbolahan

17/Eng04/014

EEE 322 [Circuit theory].



Find (i) ω_0 , Q and B

①

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}} =$$
$$= \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$

$$= \frac{1}{\sqrt{100 \times 10^{-12}}}$$

$$\omega_0 = \frac{10^5}{100 \text{ Krad/s}}$$

②

$$Q = \frac{R}{\omega_0 L} = \frac{100,000}{100,000 \times 20 \times 10^{-3}}$$

$$= \frac{1}{20} \times 10^3$$

$$= 0.05 \times 10^3$$

$$Q = 50$$

$$\textcircled{c} B = \omega_0 / a = \frac{100 \times 10^3}{50}$$

$$B = 2000 \text{ rad/s}$$

$$B = 2 \text{ Krad/s}$$

② Calculate ω_1, ω_2

$$\textcircled{1} \omega_1 = \omega_0 - \frac{B}{2} = 100000 - \frac{2000}{2}$$

$$\omega_1 = 100000 - 1000$$

$$\omega_1 = 99,000$$

$$\omega_1 = 99 \text{ Krad/s}$$

$$\textcircled{2} \omega_2 = \omega_0 + \frac{B}{2} = 100000 + \frac{2000}{2}$$

$$= 100000 + 1000$$


$$= 101000 \text{ rad/s}$$

$$\omega_2 = 101 \text{ Krad/s}$$

③

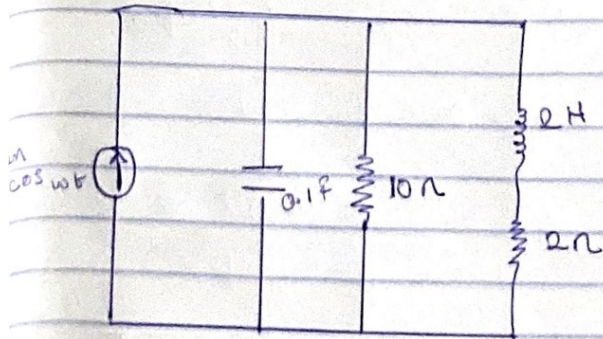QUESTION 2

Determine the resonant frequency of the circuit in fig 14.28



Solution

The input admittance is


$$Y = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2}$$
$$= 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance, $\text{Im}(Y) = 0$ and.

$$\omega_0 0.1 = \frac{2\omega_0}{4 + 4\omega_0^2} \Rightarrow$$

$$\omega_0 = 2 \text{ rad/s}$$

QUESTION 3

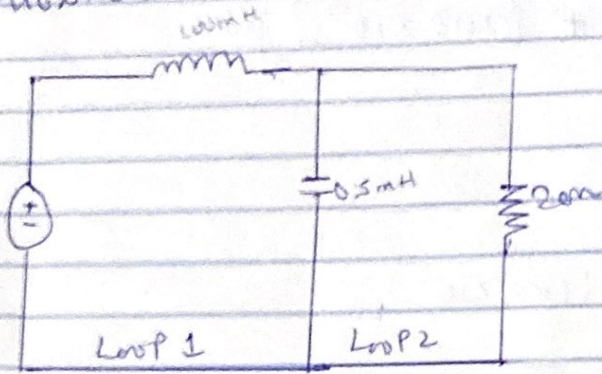

$$100\text{mH} = (100 \times 10^{-3})\text{H} \rightarrow L$$

$$0.5\text{mF} = (0.5 \times 10^{-3})\text{F} \rightarrow C$$

$$20\Omega \rightarrow R$$

frequency domain

$$(100 \times 10^{-3})j\omega$$

$$(0.5 \times 10^{-3}) = \frac{1}{2000} = \frac{2000}{j\omega}$$

$$20\Omega$$

From Loop 2.

R||C

$$\frac{20 \times \frac{2000}{j\omega}}{20 + \frac{2000}{j\omega}}$$

ie Product of
sum of

$$\frac{20 \times \frac{2000}{j\omega}}{20 + \frac{2000}{j\omega}}$$

$$\Rightarrow \frac{40000}{20j\omega + 2000} \Rightarrow \frac{40000}{20j\omega + 2000} \times \frac{(20j\omega - 2000)}{(20j\omega - 2000)}$$

$$\Rightarrow \frac{80,000j\omega - 80,000,000}{-400j\omega - 4000000}$$

$$-400j\omega - 4000000$$

From Loop 1

$R = L + [R||C]$ since the inductor is in series.

$$\frac{80000j\omega - 8000000\omega + [100 \times 10^{-3}]j\omega}{-400j\omega - 4000000}$$

at resonance $\text{Im}(Z)$

$$= \frac{80,000j\omega}{-400j\omega - 4000000} + j\omega(100 \times 10^{-3})$$

$$80000\omega_0 + [-40\omega_0^2] - 400000\omega_0$$

$$400000 - 40\omega^2 = 0$$

$$\omega^2 = 10000$$

$$\omega = 100 \text{ rad/s.}$$