

NAME: KAKIRA (MRAN - NURA

MATRIC: 17EN9021040

DEPARTMENT: COMPUTER ENGR.

COURSE: EEE 322

1) A parallel resonant circuit has $R = 100 \text{ k}\Omega$, $L = 20 \text{ mH}$ and $C = 3 \text{ }\mu\text{F}$.
Calculate ω_0 , ω_1 , ω_2 , Q and B

$$R = 100 \text{ k}\Omega, L = 20 \text{ mH}, C = 3 \text{ }\mu\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-2})(3 \times 10^{-6})}} = \frac{1}{\sqrt{6 \times 10^{-8}}} = 100000 \text{ rad/s}$$

$$\omega_0 = 100 \text{ krad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100 \times 10^3) \times (20 \times 10^{-3})} = \frac{1}{20 \times 10^{-3}} = 50$$

$$Q = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 = 2 \text{ krad/s}$$


$$\text{Since } Q > 10, \omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2000}{2} = 100 \times 10^3 - 1000 = 99000$$

$$\omega_1 = 99 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2000}{2} = 100 \times 10^3 + 1000 = 101000$$

$$\omega_2 = 101 \text{ krad/s}$$

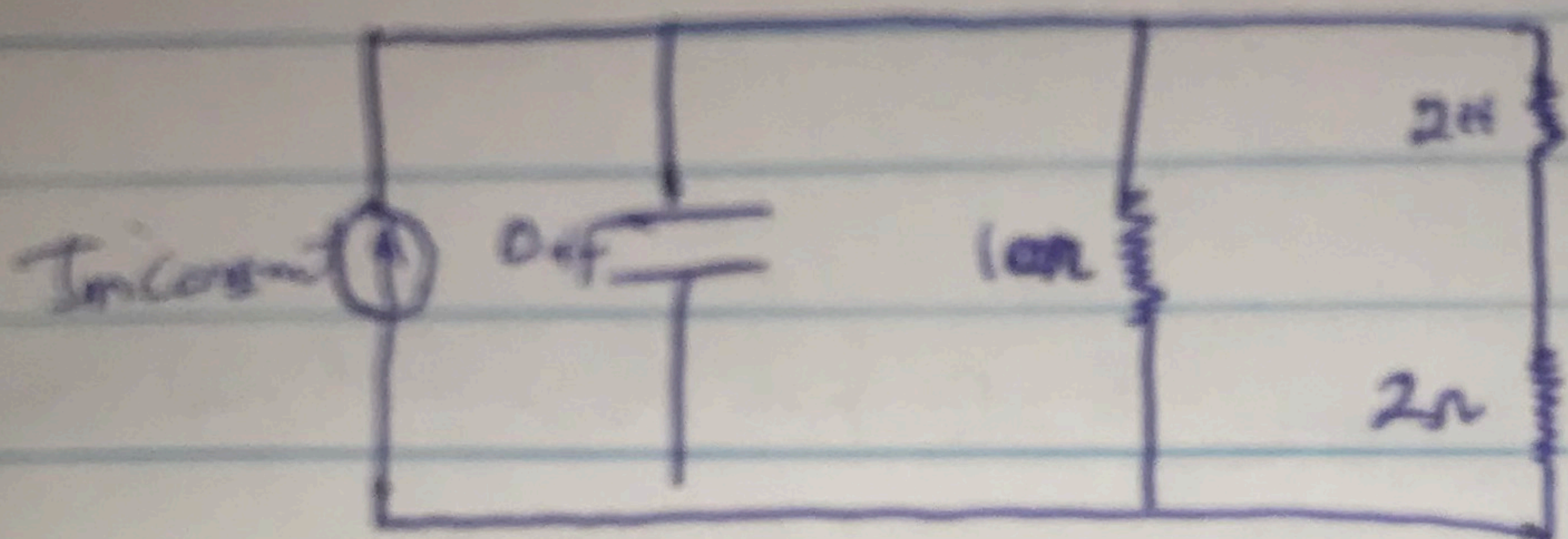b) Determine the resonant frequency of the circuit below.



$$Y = \frac{1}{j\omega 0.4} + j\omega 0.1 + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{1}{2 + j\omega 2}$$

$$\text{Rationalising } \frac{1}{2 + j\omega 2} = \frac{1}{2 + j\omega 2} \times \frac{2 - j\omega 2}{2 - j\omega 2} = \frac{2 - j\omega 2}{4 - 4j\omega 2 + 4j\omega 2 + 4\omega^2} = \frac{2 - j\omega 2}{4 + 4\omega^2}$$

$$Y = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2} = 0.1 + j\omega 0.1 + \frac{2}{4 + 4\omega^2} - \frac{j\omega 2}{4 + 4\omega^2}$$

$$Y = 0.1 + \frac{2}{4 + 4\omega^2} + \frac{j\omega 0.1 - j\omega 2}{4 + 4\omega^2} = 0.1 + \frac{2}{4 + 4\omega^2} + j\left(\frac{\omega 0.1 - 2}{4 + 4\omega^2}\right)$$

At resonance, $\text{Im}(Y) = 0$

$$\text{Therefore, } \frac{\omega 0.1 - 2}{4 + 4\omega^2} = 0$$

$$0.1 = \frac{2}{4 + 4\omega_0^2}$$


$$0.4 + 0.4\omega_0^2 = 2$$

$$0.4\omega_0^2 = 1.6$$

$$\omega_0^2 = 1.6 / 0.4 = 4$$

$$\omega_0^2 = 4; \omega_0 = \sqrt{4} = 2$$

$$\omega_0 = 2 \text{ rad/s}$$

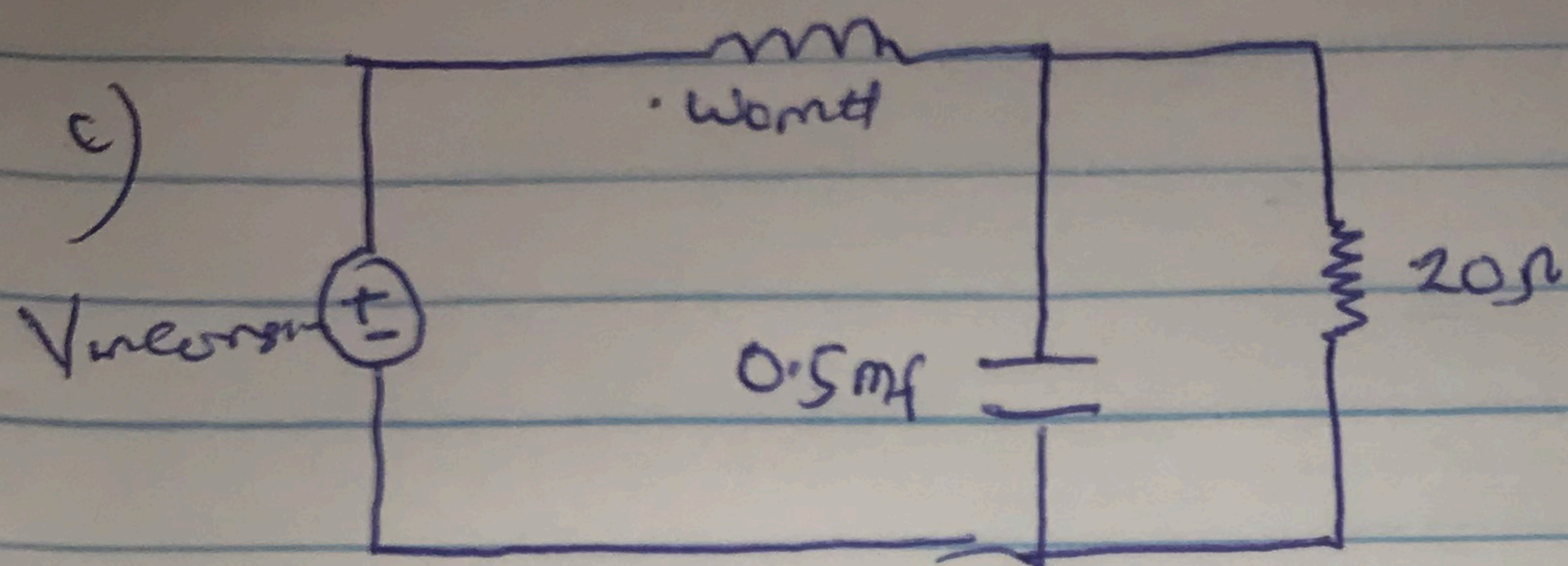

$$Z = j\omega 100 \times 10^{-3} + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \parallel \frac{1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \parallel \frac{1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \times \frac{j\omega(0.5 \times 10^{-3})}{0.01j\omega + 1} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{0.01j\omega + 1} \right)$$

Rationalizing $\frac{20}{0.01j\omega + 1} = \frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1}$

$$= \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - j\omega 0.01 + j\omega 0.01 - 1} = \frac{j\omega 0.2 - 20}{-1 \times 10^{-4} \omega^2 - 1} = \frac{-20 + j\omega 0.2}{-1 \times 10^{-4} \omega^2 - 1}$$

$$Z = j\omega(100 \times 10^{-3}) + \frac{20}{1 \times 10^{-4} \omega^2 + 1} - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2} = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega(100$$

$$\times 10^{-3}) \approx \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$\Rightarrow \omega_b^2 = \frac{0.1}{1 \times 10^{-3}} = 10000 \Rightarrow \omega_b = \sqrt{10000}$$

$$\omega_b = 100 \text{ rad/s}$$