

OLOMOWEWE RASHIDA OMOWUNMI

17/ENG04/057

ELECTRICAL ELECTRONICS ENGINEERING

ELECTRICAL CIRCUIT THEORY EEE322

ASSIGNMENT 2


QUESTION:

Exercise


Q A parallel resonant circuit has $R = 100\text{k}\Omega$, $L = 20\text{mH}$, and $C = 5\text{nF}$. Calculate ω_0 , ω_1 , ω_2 , Q and B .

Answer: 100krad/s , 97krad/s , 50 , 2krad/s

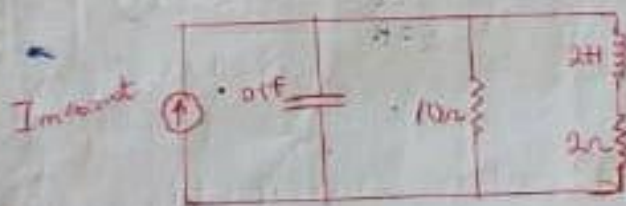(i) Determine the resonant frequency of the circuit below:



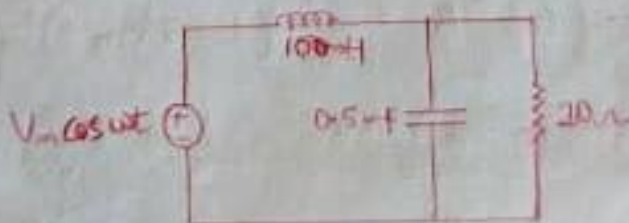(ii) Calculate the resonant frequency of the circuit below:



OLOMOWEWE RASHIDA OMOWUNMI

171ENG041057

ELECTRICAL ELECTRONICS ENGINEERING

ELECTRICAL CIRCUIT THEORY II EEE 322 (ASS II)


Question 1.

① A Parallel resonant circuit has $R = 100\text{K}\Omega$, $L = 20\text{mH}$, and $C = 5\text{nF}$. Calculate ω_0 , ω_1 , ω_2 , δ and B .

Solution;

Representing a Parallel resonant circuit.

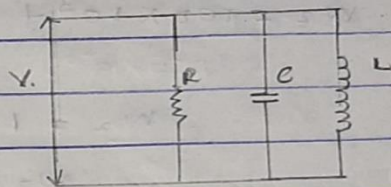Step 1; Calculating resonant frequency ω_0 using the formula for ω_0 of Parallel Ckt;



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Where; $L = 20 \times 10^{-3}$, $C = 5 \times 10^{-9}$

$$\therefore \omega_0 = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$

$$\omega_0 = 100000$$

$$\omega_0 = 100\text{K rad/s}$$

Step 2; Calculating the Quality factor, Q ;

using the formula for Q of a parallel circuit;

$$Q = \frac{R}{\omega_0 L}$$

Where; $R = 100\text{K}\Omega$, $L = 20 \times 10^{-3}$, $\omega_0 = 100\text{K rad/s}$

$$Q = \frac{100 \times 10^3}{100 \times 10^3 \times 20 \times 10^{-3}}$$

$$Q = 50$$

Step 3; Calculating the bandwidth B ;

using the formula for Bandwidth;

$$B = \frac{\omega_0}{Q}$$

$\omega_0 = 100\text{K rad/s}$, $Q = 50$

$$B = \frac{100 \times 10^3}{50} = 2000$$

\therefore Bandwidth $B = 2\text{K rad/s}$

Step 4: Calculating ω_1, ω_2 .

i. Recall that when $Q \geq 10$ High Q occurs,

$$\therefore \omega_1 \approx \omega_0 - \frac{B}{2}$$

$$\omega_2 \approx \omega_0 + \frac{B}{2}$$

$$\omega_0 = 100 \text{ k rad/s}, \quad B = 2 \text{ k rad/s}$$

$$\therefore \omega_1 \approx 100 \times 10^3 - \frac{2 \times 10^3}{2}$$

$$\omega_1 \approx 99000$$

$$\omega_1 \approx 99 \text{ k rad/s}^{-1}$$

$$\therefore \omega_2 \approx 100 \times 10^3 + \frac{2 \times 10^3}{2}$$

$$\omega_2 \approx 101000$$


$$\omega_2 \approx 101 \text{ k rad/s}^{-1}$$

In conclusion;

$$\omega_0 = 100 \text{ k rad/s}^{-1}, \quad Q = 50, \quad B = 2 \text{ k rad/s}^{-1}, \quad \omega_1 \approx 99 \text{ k rad/s}^{-1}, \quad \omega_2 \approx 101 \text{ k rad/s}^{-1}$$

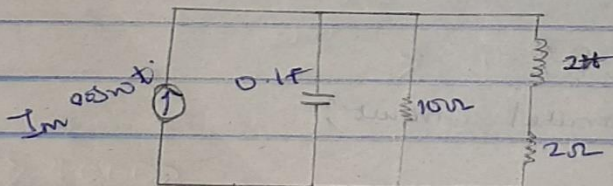QUESTION 2:

Determine the resonant frequency of the circuit below;



Solution:

Recall that;

Admittance; $Y = H(\omega) = I/V$ (Current being supplied)

In an R-L-C parallel circuit; (admittance)

$$Y = H(\omega) = I/V = 1/R + j\omega C + 1/j\omega L$$

From the circuit given above;

$$\therefore Y = H(\omega) = j\omega C + 1/R_1 + 1/R_2 + 1/j\omega L \quad \dots (i)$$

Where; $C = 0.1$, $R_1 = 10$, $R_2 = 2$, $L = 2$

Inserting these values into eq (i)

$$\therefore Y = H(\omega) = j\omega(0.1) + \frac{1}{10} + \frac{1}{2+j\omega 2} \quad \text{eqn (2)}$$

From eqn (2)

$$\frac{1}{2+j\omega 2} \Rightarrow \frac{1}{2+j\omega 2} * \frac{2-j\omega 2}{2-j\omega 2}$$

$$\Rightarrow \frac{2-j\omega 2}{4+4\omega^2} \quad \text{--- (3)}$$

\therefore Replace eqn (3) in eqn (2)

$$\therefore Y = H(\omega) = j\omega(0.1) + \frac{1}{10} + \frac{2-j\omega 2}{4+4\omega^2}$$

Separating into the real and imaginary part;

$$\text{Real part} = \left(\frac{1}{10} + \frac{2}{4+4\omega^2} \right)$$

$$\text{Imaginary part} = \left(j\omega(0.1) - \frac{2j\omega}{4+4\omega^2} \right)$$

Recall, at resonance; Imaginary part = 0.

$$\therefore j\omega(0.1) - \frac{2j\omega}{4+4\omega^2} = 0$$

$$\therefore j \left(\omega(0.1) - \frac{2\omega}{4+4\omega^2} \right) = 0$$

$$\therefore 0.1\omega_0 - \frac{2\omega_0}{4+4\omega_0^2} = 0$$

$$0.1\omega_0(4+4\omega_0^2) = 2\omega_0 = 0$$

$$0.4\omega_0 + 0.4\omega_0^3 - 2\omega_0 = 0$$

$$0.4\omega_0^3 = 1.6\omega_0$$

$$0.4\omega_0^2 = 1.6$$


$$\omega_0^2 = 4$$

$$\omega_0 = 2 \text{ rad/s}$$

\therefore The resonant frequency $\omega_0 = 2 \text{ rad/s}$.

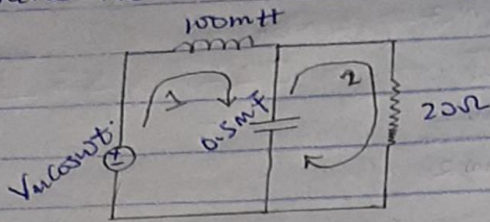Question 3,

Determine the resonant frequency of the circuit below;



Solution;

Resolving the circuit above;

Convert Parameters to s-domain;

$$\therefore R = 20\Omega$$

$$C = \frac{1}{j\omega(0.5 \times 10^{-3})}$$

$$C = \frac{2000}{j\omega}$$

$$L = j\omega(100 \times 10^{-3})$$


From LOOP 2;

$$\therefore 20 * \frac{2000}{j\omega} = \frac{20 + \frac{2000}{j\omega}}{j\omega}$$

$$\Rightarrow \frac{40000}{j\omega} = \frac{20j\omega + 2000}{j\omega}$$

$$R||C \Rightarrow \frac{40000}{20j\omega + 2000}$$

Circuit becomes;

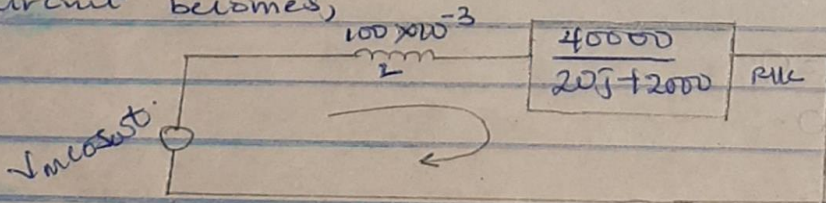

From circuit; L in Series with (R||C)

$$H(\omega) = \frac{V}{I} = \frac{40000}{20j\omega + 2000} + (100 \times 10^{-3} j\omega)$$

$$\frac{V}{I} = \frac{40000}{20j\omega + 2000} + j\omega \cdot 10^{-1}$$

$$\text{where; } \frac{40000}{20j + 2000} \Rightarrow \frac{40000}{20j + 2000} * \frac{(20j - 2000)}{(20j - 2000)}$$

$$\Rightarrow \frac{800000j\omega - 80000000}{-400\omega^2 - 4000000}$$

$\therefore \frac{V}{I}$ become;

$$\frac{V}{I} = \frac{800000j\omega - 80000000 + j\omega(0.1)}{-400\omega^2 - 4000000}$$

Separating Real and imaginary part;

$$\frac{V}{I} \text{ Real; } \left(\frac{-80000000}{-400\omega^2 - 4000000} \right)$$

$$\text{Imaginary; } \left(\frac{800000j\omega}{-400\omega^2 - 4000000} \right) + j\omega(0.1)$$

Recall at Resonance Imaginary Part = 0

$$\therefore \frac{800000j\omega_0}{-400\omega_0^2 - 4000000} + 0.1j\omega = 0$$

$$j \left(\frac{800000\omega}{-400\omega^2 - 4000000} + 0.1\omega \right) = 0$$

$$\therefore 800000\omega_0 + 0.1\omega_0(-400\omega_0^2 - 4000000) = 0$$

$$800000\omega_0 - 40\omega_0^3 - 4000000\omega_0 = 0$$

$$400000\omega_0 - 40\omega_0^3 = 0$$

$$400000\omega_0 = 40\omega_0^3$$

$$400000 = 40\omega_0^2$$

$$\omega_0^2 = 10000$$

$$\omega_0 = \sqrt{10000}$$

$$\omega_0 = 100 \text{ rad/s}$$