

EZENKATA VICTOR CHUMA
17/ENG04/026
Electrical/Electronics

1) A parallel resonant circuit has
 $R = 100 \text{ k}\Omega$, $L = 20 \text{ mH}$ and $C = 5 \text{ nF}$.
calculate ω_0 , ω_1 , ω_2 , Q and B .

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3})(5 \times 10^{-9})}}$$
$$= 100 \text{ k rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100 \times 10^3)(20 \times 10^{-3})}$$
$$= 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2 \text{ k rad/s}$$

Since $Q > 10$, $\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2000}{2}$


$$\omega_1 = 99 \text{ k rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2000}{2}$$

$$= 100 \times 10^3 + 1000$$

$$\omega_2 = 101 \text{ k rad/s}$$

b)

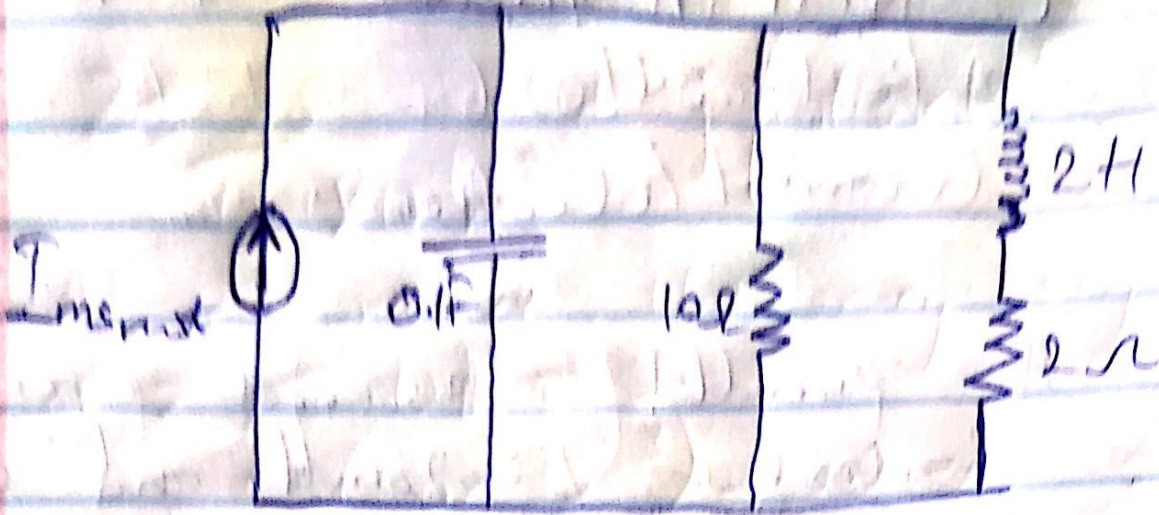

$$Y = \frac{1}{10} + j\omega 0.1 + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{1}{2 + j\omega 2}$$

Rationalizing;

$$Y = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

$$Y = 0.1 + j\omega 0.1 + \frac{2}{4 + 4\omega^2} - \frac{j\omega 2}{4 + 4\omega^2}$$

$$Y = 0.1 + \frac{2}{4 + 4\omega^2} + j\omega 0.1 - \frac{j\omega 2}{4 + 4\omega^2}$$

$$Y = 0.1 + \frac{2}{4 + 4\omega^2} + j \left(\omega 0.1 - \frac{\omega 2}{4 + 4\omega^2} \right)$$

At resonance, $\text{Im}(Y) = 0$

Therefore, $\omega 0.1 - \frac{\omega 2}{4 + 4\omega^2} = 0$

$$0.1 - \frac{2}{4 + 4\omega^2} = 0$$


$$0.1 = \frac{2}{C(1 + 4\omega_0^2)}$$

$$0.4 + 0.4\omega_0^2 = 2$$

$$\omega_0^2 = 4$$

$$\omega_0 = 2 \text{ rad/s}$$

c)

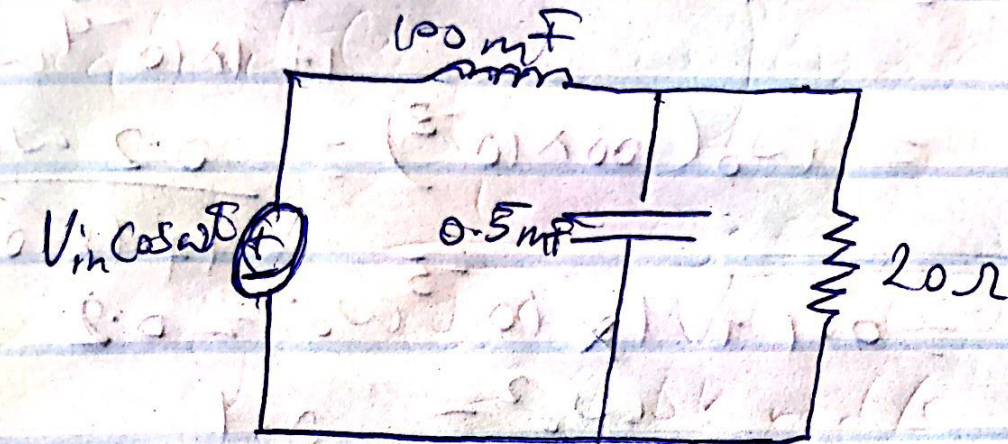

$$Z = j\omega 100 \times 10^{-3} + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \cdot \frac{20 + 1}{1 + 0.5 \times 10^{-3} j\omega} \right)$$

$$Z = j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \cdot \frac{0.01j\omega + 1}{0.5 \times 10^{-3} j\omega} \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{0.01j\omega + 1} \right)$$

Rationalizing;

$$Z = j\omega(100 \times 10^{-3}) + \frac{20}{1 + 1 \times 10^{-4} \omega^2} - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j\omega(100 \times 10^{-3}) - \frac{0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 + 1 \times 10^{-4} \omega^2} + j \left(\omega(100 \times 10^{-3}) - \frac{0.2 \omega}{1 + 1 \times 10^{-4} \omega^2} \right)$$

At resonance, the imaginary part of Z , $\text{Im}(Z) = 0$

$$= \omega_0(100 \times 10^{-3}) - \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = 0$$

$$= \omega_0(100 \times 10^{-3}) = \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

$$= 0 = 1 + 1 \times 10^{-4} \omega_0^2 = 0.2$$

$$\omega_0^2 = \frac{0.1}{1}$$

$$\omega_0 = 10 \times 10^{-5} = 5$$

$$\omega_0 = 100 \text{ rad/s}$$