

OBAKPO EMMANUEL

17/ENG05/024

MECHATRONICS ENGINEERING
822 822 ASS. 2

(i)

$$R = 100 \text{ k}\Omega$$

$$L = 20 \text{ mH}$$

$$C = 5 \text{ nF}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}} = 100 \text{ rad/s}_{//}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \text{ k}}{100 \text{ rad/s} \times 20 \times 10^{-3}} = 50_{//}$$


$$B = \frac{\omega_0}{Q} = \frac{100,000}{50} = 2 \text{ krad/s}_{//}$$

Since $Q > 10$, we regard it as a high Q circuit

$$\omega_1 = \omega_0 - \frac{B}{2} = 100,000 - 1000 = 99 \text{ krad/s}_{//}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100,000 + 1000 = 101 \text{ krad/s}_{//}$$

(ii)

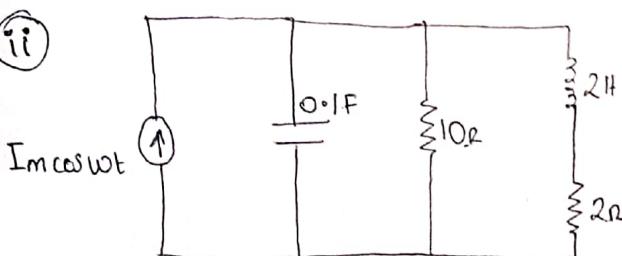

$$\begin{aligned} \text{The admittance } Y &= 0.1j\omega + \frac{1}{10} + \frac{1}{2+2j\omega} \\ &= 0.1 + 0.1j\omega + \frac{2-2j\omega}{(2+2j\omega)(2-2j\omega)} \\ Y &= 0.1 + 0.1j\omega + \frac{2-2j\omega}{4+4j\omega^2} \end{aligned}$$

at resonance, Imaginary part of $Y = 0$

$$\therefore 0.1j\omega_0 - \frac{2\omega_0}{4+4\omega_0^2} = 0$$

$$0.1\omega_0 = \frac{2\omega_0}{4 + 4\omega_0^2}$$

$$0.4\omega_0 + 0.4\omega_0^3 = 2\omega_0$$

$$0.4\omega_0^3 = 2\omega_0 - 0.4\omega_0$$

$$0.4\omega_0^3 = 1.6\omega_0$$

$$0.4\omega_0^2 = 1.6$$


$$\omega_0^2 = 1.6 / 0.4$$

$$\omega_0^2 = 4$$

$$\omega_0 = 2 \text{ rad/s}$$

iii)

$\sqrt{m} \cos \omega t$

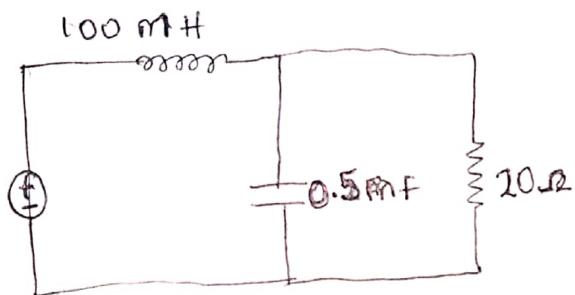

$$Z = j\omega (100 \times 10^{-3}) + \frac{20 \times \frac{2000}{j\omega}}{20 + \frac{2000}{j\omega}}$$

$$Z = j\omega (100 \times 10^{-3}) + \frac{40,000}{20j\omega + 2000} \times \left(\frac{20j\omega - 2000}{20j\omega + 2000} \right)$$

$$Z = j\omega (100 \times 10^{-3}) + \frac{(8 \times 10^5)j\omega - 8 \times 10^7}{-400\omega^2 - 4 \times 10^6}$$

At resonance $\text{Im}(Z) = 0$

$$\therefore g(\omega_0 (100 \times 10^{-3})) + \frac{(8 \times 10^5)\omega_0}{-400\omega_0^2 - 4 \times 10^6} = 0$$

$$(8 \times 10^5)\omega_0 = 40\omega_0^3 + (4 \times 10^5)\omega_0$$

$$40\omega_0^3 = (8 \times 10^5)\omega_0 - (4 \times 10^5)\omega_0$$

$$40\omega_0^3 = (4 \times 10^5)\omega_0$$

$$40\omega_0^2 = 4 \times 10^5$$

$$\omega_0^2 = \frac{4 \times 10^5}{40} = 10000$$

$$\omega_0 = \sqrt{10000}$$

$$\omega_0 = 100 \text{ rad/s}$$