

EZEFUNA DAVID

17/ENGG5/013

MECHATRONICS ENGINEERING

Q1)  $R = 100 \text{ k}\Omega = 100000\Omega = 1 \times 10^5 \Omega$

$$L = 2 \text{ mH} = 0.0002 \text{ H} = 2 \times 10^{-4} \text{ H}$$

$$C = 5 \text{ nF} = 5 \times 10^{-9} \text{ F}$$

i)  $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-4}) \times 5 \times 10^{-9}}} = \frac{1}{\sqrt{100 \times 10^{-12}}} = \frac{1}{10 \times 10^{-6}} = 10^5 = 100 \text{ krad/s}$


b)  $Q = \frac{R}{\omega_0 L} = \frac{100,000}{100,000 \times 20 \times 10^{-7}} = \frac{10^3}{20} = 0.05 \times 10^3 = 50$

c)  $B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2 \text{ krad/s}$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100000 - \frac{2000}{2} = 99,000 = 99 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100000 + \frac{2000}{2} = 101 \text{ krad/s}$$

Q2)

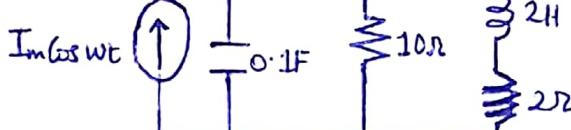

The input admittance is

$$Y = j\omega \cdot 1 + \frac{1}{10} + \frac{1}{2+j\omega 2} = 0 \cdot 1 + j\omega \cdot 1 + \frac{2-j\omega 2}{4+4\omega^2}$$


at Resonance

$$\text{Im}(Y) = 0$$

$$\therefore \omega \cdot 0 \cdot 1 = \frac{2\omega_0}{4+\omega_0^2} = 0$$

$$\omega_0 = 2 \text{ rad/s}$$

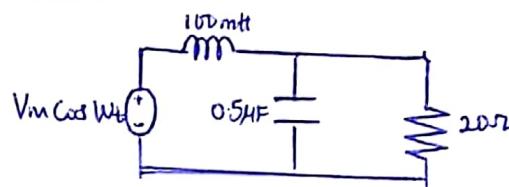Q3) Calculate the resonant frequency of the circuit below



$$20 + \frac{2000}{j\omega}$$

$$\frac{j\omega}{20 + \frac{2000}{j\omega}} = \frac{40000}{20j\omega + 2000} - \frac{40000}{20j\omega + 2000} + \frac{(20j\omega - 2000)}{(20j\omega - 2000)}$$

$$= \frac{80000j\omega - 80 \times 10^6}{-400j\omega - 40 \times 10^5} + 100 \text{ mH}$$

At Resonance of the imaginary part at  $\omega = 0$

$$= \frac{80 \times 10^4 j\omega}{-400j\omega - 40 \times 10^5} + j\omega (100 \times 10^{-3})$$

$$= 80 \times 10^4 \omega + (-40\omega^2) - 40 \times 10^4 \omega$$

$$0 = 40 \times 10^4 - 40\omega^2 - 40\omega^2 = -40 \times 10^4$$

$$\omega^2 = 100000$$

$$\omega = \sqrt{100000}$$

$$\omega = 100 \text{ rad/s}$$