

Amoo OLUWAFERANMI MARK
 18/EN04/077
 Electric Circuit Theory II
 Electronics Engineering

Assignment II

(1) $R = 100 \Omega$
 $L = 20 \text{ mH}$
 $C = 5 \text{ nF}$

(2) $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 10^{-3} \times 5 \times 10^{-9}}}$
 $= 100000 \text{ rad/s}$
 $= 100 \text{ krad/s}$

(1) $\omega_1 = \omega_0 - \frac{B}{2}$

$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{100 \times 10^3 \times 2 \times 10^{-3}}$
 $= 50$

$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50}$
 $= 2000 \text{ rad/s}$


$\omega_1 = 100 \times 10^3 - \frac{2000}{2}$

$\omega_1 = 99000 \text{ rad/s}$

$\omega_2 = \omega_0 + \frac{B}{2}$

$= 100 \times 10^3 + \frac{2000}{2}$
 $= 101000 \text{ rad/s}$

$Q = 50$
 $B = 2000 \text{ rad/s}$

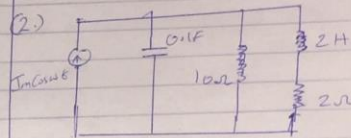

Solution


The input admittance is

$Y = j\omega \cdot 0.1 + \frac{1}{2 + j\omega 2}$
 $= 0.1 + j\omega \cdot 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$

At resonance, $\text{Im}(Y) = 0$ and

$\omega \cdot 0.1 - \frac{2\omega}{4 + 4\omega^2} = 0$

$\omega_0 = 2 \text{ rad/s}$

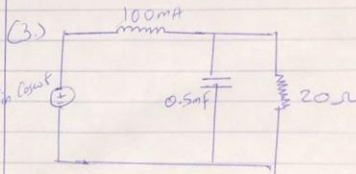

$Z_L = j\omega L$
 $= j\omega (10 \times 10^{-3})$
 $= j\omega 0.01$

$Z_C = \frac{1}{j\omega C}$
 $= \frac{1}{j\omega (0.5 \times 10^{-9})}$
 $= \frac{1}{j\omega 5 \times 10^{-4}}$

$V = j\omega \cdot 0.1 + \frac{1}{20} + \frac{1}{j\omega 5 \times 10^{-4}}$

$V = 0.2 + j\omega \cdot 0.1 + \frac{1}{j\omega 5 \times 10^{-4}}$

At resonance $\text{Im}(Y) = 0$

$\omega_0 = j\omega 5 \times 10^{-4} - 0.2$

$\omega_0 = 2.179 \text{ rad/s}$