

Otho Expo - Ekspansiyang

Circuit theory

H/EnGos/011

Mechanics

- ① A parallel resonant circuit has $R = 100 \text{ k}\Omega$, $L = 20 \text{ mH}$, and $C = 5 \text{ mF}$. Calculate ω_c , ω_1 , ω_2 , Q and B .

$$\begin{aligned}\omega_c &= \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3}) \times (5 \times 10^{-3})}} \\ &= 100 \text{ krad/s}\end{aligned}$$

$$\begin{aligned}B &= \frac{\omega_c}{Q} = \frac{1}{R C} = \frac{1}{100 \times (5 \times 10^{-3})} \\ &= 2 \text{ krad/s}\end{aligned}$$

From the equations above we know that $\omega_0 = 100 \text{ krad/s}$


$$\therefore Q = \frac{\omega_0}{B} = \frac{100 \times 10^3}{2 \times 10^3} = 50$$

$$Q \geq 10$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2 \times 10^3}{2} = 99 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2 \times 10^3}{2} = 101 \text{ krad/s}$$

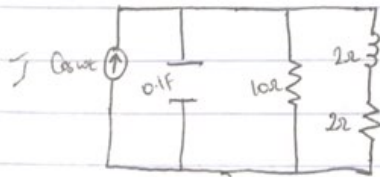Determine the resonant frequency of the circuit below.



The Input admittance is

$$Y = j\omega 0.1 + \frac{1}{10} + \frac{1}{2+j\omega 2}$$

$$= 0.1 + j\omega 0.1 + \frac{2-j\omega 2}{4+\omega^2}$$


at resonance

$$\text{Im}(Y) = 0$$

$$\omega_0 0.1 = \frac{2\omega_0}{4+\omega_0^2} = 0$$

$$\omega_0 = 2 \text{ rad/s}$$

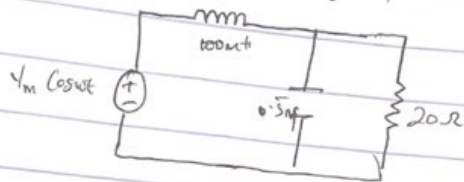Calculate the resonant frequency of the circuit below



$$\frac{20 + \frac{2000}{j\omega}}{20 + \frac{2000}{j\omega}} = \frac{40000}{20j\omega + 2000} - \frac{40000}{20j\omega + 2000} + \frac{(20j\omega - 2000)}{(20j\omega - 2000)}$$

$$= \frac{80000j\omega - 80000000}{-400j\omega - 4000000} + 100 \text{ mH}$$

At resonance of the imaginary parts at $\omega = 0$

$$\frac{80000j\omega}{-400j\omega - 4000000} + \omega [100 \times 10^{-3}]$$

$$= \frac{800000\omega}{-400000 - 4000000\omega} - 4000000\omega$$

$$= 400000 - 40\omega^2 = 0$$

$$-40\omega^2 = -400000$$

$$\omega^2 = 10000$$

$$\omega = \sqrt{10000}$$

$$\omega = 100 \text{ rad/s}$$