

$$i) \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3}) \times (5 \times 10^{-3})}}$$

$$= 100 \text{ k rad/s}$$

$$B = \frac{\omega_0}{Q} = \frac{1}{RC} = \frac{1}{100 \times (5 \times 10^{-3})}$$

$$= 2 \text{ k rad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{100 \times 10^3}{2 \times 10^3} = 50$$

Since $Q \gg 10$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2 \times 10^3}{2} = 99 \text{ k rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2 \times 10^3}{2} = 101 \text{ k rad/s}$$

ii) Input admittance:

$$Y = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2}$$

$$= 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + \omega^2}$$

at Resonance

$$\text{Im}(Y) = 0$$

$$\omega_0 \cdot 0.1 = \frac{2\omega_0}{4 + \omega_0^2} = 0$$

$$\omega_0 = 2 \text{ rad/s}$$

$$\begin{aligned}
 3) \quad \frac{20 + \frac{200}{j\omega}}{20 + \frac{200}{j\omega}} &= \frac{4000}{20j\omega + 2000} - \frac{4000}{20j\omega + 2000} + \frac{(20j\omega - 200)}{(20j\omega - 2000)} \\
 &= \frac{8000j\omega - 800000}{-400j\omega - 40000} + 100mH
 \end{aligned}$$

At resonance of the imaginary part at $\omega = 0$

$$\frac{80000j\omega}{-400j\omega - 40000} + j\omega [100 \times 10^{-3}]$$

$$= 80000\omega + [-40\omega^2] - 40000\omega$$

$$= 40000 - 40\omega^2 = 0$$

$$-40\omega^2 = -40000$$

$$\omega^2 = 1000$$

$$\omega = \sqrt{1000}$$

$$\omega = 100 \text{ rad/s}$$