

Human Adepoju
171ENG051002
Mechatronics Engineering

1) $R = 100 \text{ k}\Omega$; $L = 20 \text{ mH}$, $C = 5 \text{ nF}$

$$R = 100 \times 10^3 = 100000 \quad L = 20 \times 10^{-3} \text{ H} \quad C = 5 \times 10^{-9}$$

2) $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$

$$\begin{aligned} &= \frac{1}{\sqrt{100 \times 10^{-12}}} = \frac{1}{10 \times 10^{-6}} \\ &= 10^{-1} \times 10^6 \\ &= 10^5 \\ &= 100 \text{ Krads} \end{aligned}$$

3) $Q = \frac{R}{\omega_0 L} = \frac{100000}{100 \times 100 \times 20 \times 10^{-3}}$

$$= \frac{1}{20} \times 10^3$$

$$= 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 \text{ rad/s}$$

$$= 2 \text{ k/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100,000 - \frac{2000}{2}$$

$$= 100,000 - 1000$$

$$= 99,000$$

$$99 \text{ k rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100,000 + \frac{2000}{2}$$

$$100,000 + 1000$$

$$= 101,000 \text{ rad/s}$$

$$= 101 \text{ k rad/s}$$

2) Input admittance

$$Y = j\omega 0.1 + \frac{1}{\omega} + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 +$$


$$\frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance $\text{Im}(Y) = 0$ and

$$\omega 0.1 - \frac{2\omega 0}{4 + 4\omega^2} = 0 \Rightarrow$$

$$\therefore \omega_0 = 2 \text{ rad/s}$$

Question 3.

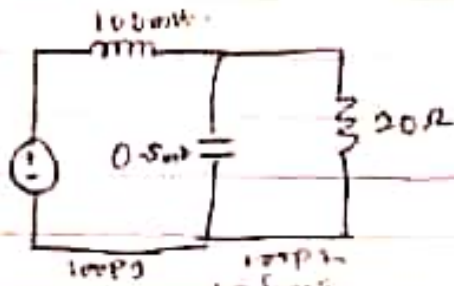

| | |
|--|--|
| $100\text{mH} = (100 \times 10^{-3})\text{H} \rightarrow L$ $0.5\text{mF} = (0.5 \times 10^{-3})\text{F} \rightarrow C$ $20\Omega \rightarrow R$ | <p>Frequency domain.</p> $(100 \times 10^{-3})j\omega\text{H}$ $(0.5 \times 10^{-3}) = \frac{1}{2000} = 2000/j\omega$ 20Ω |
|--|--|

From loop 2

R || C

$$20 \times \frac{2000}{j\omega}$$

i.e. Resistor

$$20 + \frac{2000}{j\omega}$$

5m.

$$\Rightarrow \frac{40000}{20j\omega + 2000} \Rightarrow \frac{40000}{20j\omega + 2000} \times \frac{(20j\omega - 2000)}{(20j\omega + 2000)} \text{ (rationalization)}$$

$$\Rightarrow \frac{800000j\omega - 80000000}{-400j\omega - 4000000}$$

Back to loop 1.

$R = L + (R || C)$ since the inductor is in series

$$\frac{800000j\omega - 80000000}{-400j\omega - 4000000} + 100(100 \times 10^{-3})j\omega$$

at resonance: $\text{Im}(R)$

$$= \frac{800000j\omega}{-400j\omega - 4000000} + j\omega(100 \times 10^{-3})$$

$$800000\omega_0 + (-40\omega_0^2) - 4000000 = 0$$

$$400000 - 40\omega^2 = 0$$

$$\omega^2 = 10000$$

$$\omega = 100 \text{ rad/s}$$

□