

NAME: Orlade Emmanuel O.


DEPARTMENT: Mechatronics Engineering

MATRIC NUMBER: 17/ENG105/037

EEE 322 Assignmab

① $R = 100k\Omega$; $L = 20mH$; $C = 5\mu F$, P_{avg} ; ω_0 , ω_1 , ω_2 , Q , B .

Solution

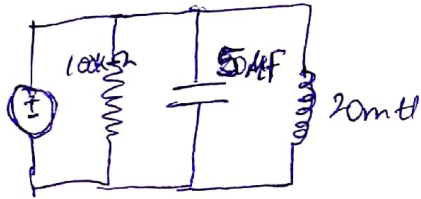

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(20 \times 10^{-3}) \times (5 \times 10^{-6})}} = 100,000 \text{ rad/s} = \underline{\underline{100 \text{ k rad/s}}}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100,000}{100,000 \times (20 \times 10^{-3})} = \frac{1}{(20 \times 10^{-3})} = \underline{\underline{50}}$$


$$B = \frac{\omega_0}{Q} = \frac{100,000}{50} = 2000 \text{ rad/s} = \underline{\underline{2 \text{ k rad/s}}}$$

since $Q > 10$, the circuit is regarded as a high frequency circuit.

$$\omega_1 = \omega_0 - \frac{B}{2} = 100,000 - \frac{2000}{2} = 99,000 \text{ rad/sec} = \underline{\underline{99 \text{ k rad/s}}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100,000 + \frac{2000}{2} = 101,000 \text{ rad/s} = \underline{\underline{101 \text{ k rad/s}}}$$

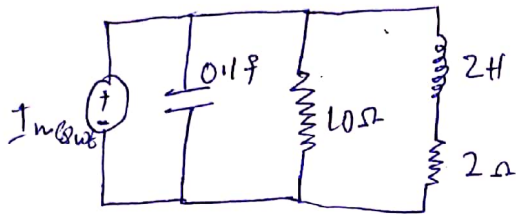
② Determine the resonant frequency of the circuit below;



Solution

~~For the circuit, the admittance, Y is;~~

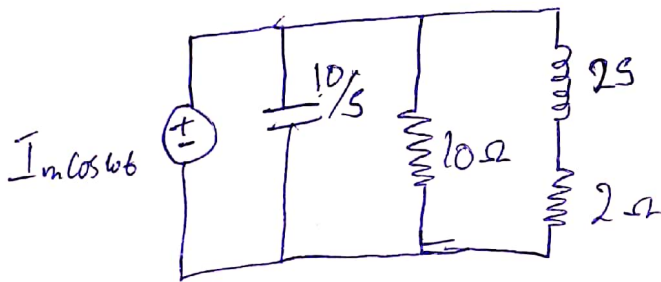∴ Transform the circuit from the 'Time-Domain' to the 'Frequency-Domain'



From the circuit, the admittance Y is;

$$Y = \frac{S}{10} + \frac{1}{10} + \frac{1}{2S+2} \Rightarrow 0.1 + j\omega 0.1 + \frac{2 - j\omega}{4 + 4\omega^2}$$

(where; $S = j\omega$)

Resonance occurs when the imaginary part of $Y = 0$


$$\therefore 0.1\omega_0 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0$$

$$\Rightarrow 0.4\omega_0 + 0.4\omega_0^3 = 2\omega_0$$

$$\Rightarrow 0.4\omega_0^3 = 16\omega_0$$

$$\therefore 0.4\omega_0^2 = 16$$
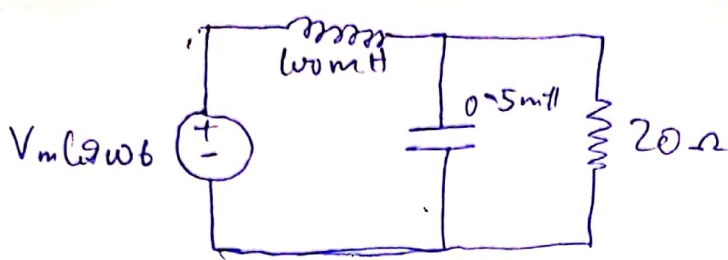
$$\therefore \omega_0 = \underline{\underline{2 \text{ rad/s}}}$$



$$Z = j\omega(100 \times 10^{-3}) + \frac{20 * \frac{2000}{j\omega}}{20 + \frac{200}{j\omega}}$$

$$\therefore Z = j\omega(100 \times 10^{-3}) + \frac{40,000}{20j\omega + 2000} \times \left(\frac{20j\omega - 2000}{20j\omega - 2000} \right)$$

$$\therefore Z = j\omega(100 \times 10^{-3}) + \frac{(8 \times 10^5)j\omega - 8 \times 10^7}{-400\omega^2 - 4 \times 10^6}$$

At resonance, $\text{Im}(Z) = 0$

$$\therefore \omega_0(100 \times 10^{-3}) + \frac{(8 \times 10^5)\omega_0}{-400\omega_0^2 - 4 \times 10^6} = 0$$

$$(8 \times 10^5)\omega_0 = 40\omega_0^3 + (9 \times 10^5)\omega_0$$

$$40\omega_0^3 = (8 \times 10^5)\omega_0 - (4 \times 10^5)\omega_0$$

$$40\omega_0^3 = (4 \times 10^5)\omega_0$$

$$\therefore \omega_0^2 = \frac{4 \times 10^5}{40}$$

$$\therefore \omega_0 = \sqrt{10000}$$

$$\therefore \omega_0 = \underline{\underline{100 \text{ rad/s}}}$$

3)