

YINOLUWA OYELEYE EMMANUEL

COMPUTER ENG EEE 322 18/ENG02/106

a) $R = 100k\Omega$
 $L = 20mH$
 $C = 5nF$

Calc $\omega_0, \omega_1, \omega_2, Q$ and B

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$
$$= \frac{100000}{\cancel{100000}} = 100k\text{rad/s}$$

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}} = \sqrt{\left(\frac{1}{2 \times 100 \times 10^3 \times 5 \times 10^{-9}}\right)^2 + \frac{1}{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$
$$= 100005$$

$$\omega_1 = \frac{-1}{2RC} + 100005$$

$$\omega_1 = \frac{-1}{2 \times 100 \times 10^3 \times 5 \times 10^{-9}} + 100005$$
$$= -1000 + 100005$$
$$= 99005$$
$$= 99k\text{rad/s}$$

$$\omega_2 = \frac{+1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$1000 + 100005$$
$$101000$$
$$101k\text{rad/s}$$