

1) A parallel resonant circuit has $R = 100\text{K}\Omega$, $L = 20\text{mH}$, and $C = 5\text{nF}$. Calculate ω_0 , ω_1 , ω_2 , Q and B .

Solution

$$R = 100\text{K}\Omega$$

$$L = 20\text{mH}$$

$$C = 5\text{nF} = 5 \times 10^{-9}\text{F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}} = \frac{1}{\sqrt{1 \times 10^{-10}}} = 100,000$$

$$* \omega_0 = 100\text{Krad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2}, \quad \omega_2 = \omega_0 + \frac{B}{2}$$

find Q and B

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{100 \times 10^3 \times 20 \times 10^{-3}} = \frac{100}{2} = 50$$

$$* Q = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 1000}{50} = 2000 \text{ rad/s}$$

$$B = 2\text{Krad/s}$$


$$\omega_1 = \omega_0 - \frac{B}{2} = 100,000 - \frac{2000}{2} = 99,000$$

$$* \omega_1 = 99\text{Krad/s}$$

$$\omega_2 = \omega_0 + \frac{\beta}{2} = 100,000 + \frac{1000}{2} = 100,500$$

$$* \omega_2 = 100 \text{ Krad/s}$$

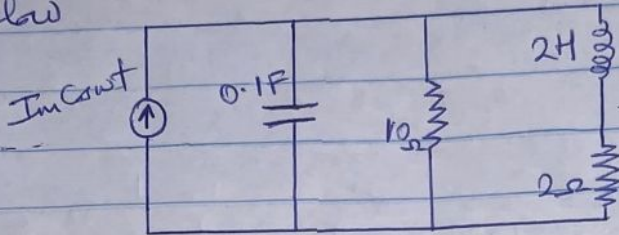(2) Determine the resonant frequency of the circuit below



Resonant Frequency, $\omega_0 = ?$

Solution

$$C = 0.1 \text{ F}$$

$$L = 2 \text{ H}$$

$$R_1 = 10 \Omega, R_2 = 2 \Omega \quad \text{Connected in parallel}$$

$$R_T = ?$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{10} + \frac{1}{2}$$

$$\frac{1}{R_T} = \frac{1 + 5}{10} = \frac{6}{10} = \frac{3}{5}$$


$$R_T = \frac{5}{3} = 1.67 \Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 0.1}} = \frac{1}{0.4472135955}$$

$$\omega_0 = \sqrt{5} = 2.236067977$$

$$\omega_0 \approx \underline{\underline{2.24 \text{ rad/s}}}$$

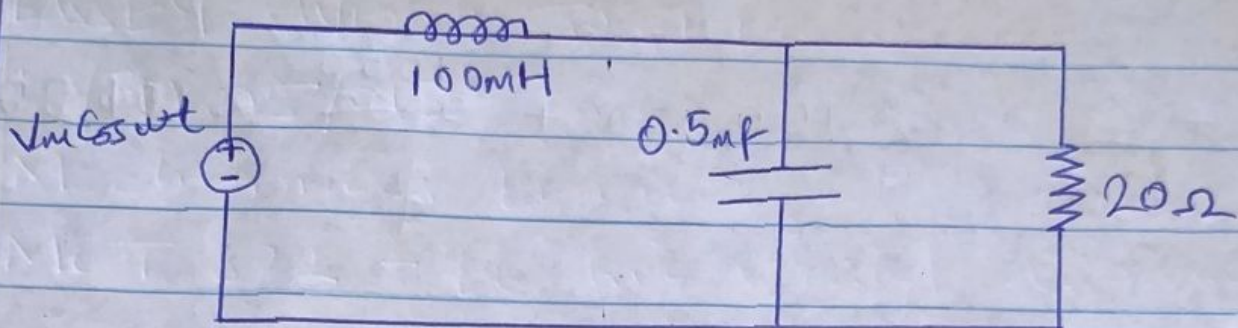(3) Calculate the resonant frequency of the circuit below:



Solution

$$C = 0.5\text{mF} = 0.0005\text{F}$$

$$L = 100\text{mH} = 0.1\text{H}$$

$$R = 20\Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.5 \times 10^{-3} \times 0.1}} = \frac{1}{\sqrt{5 \times 10^{-5}}}$$

$$\omega_0 = 141.4213562 \text{ rad/s}$$

$$\omega_0 \approx \underline{\underline{141.42 \text{ rad/s}}}$$