

Describe a zener diode regulator

The important application of the zener diode as a voltage regulator is that the voltage across the diode in the reverse bias region is almost constant.

The function of the regulator is to provide a constant output voltage to a load which is connected in parallel with it in spite of variations in the supply voltage or the variation in the load current and the zener diode will continue to regulate the voltage until the diode current falls below the minimum $I_{z(\min)}$ value in the reverse breakdown region.

In the zener diode regulator, the resistor R_s is connected in series with the zener diode to limit the current from the zener diode to limit the current from the supply. The diode with the voltage source is connected across the combination. The diode is connected across the combination. The diode is connected across the combination. The diode is connected across the combination.


When no load is connected to the circuit, the load current will be zero. The zener diode will pass the maximum current flowing in the circuit.

through the zener diode when a load is connected to the circuit.


Also, a small value of the series resistor R_s will result in a greater diode current when the load resistor R_L is connected and large as this will increase the power dissipation requirement of the diode.

The load is connected in parallel with the zener diode, so the voltage across R_L is always the same as the zener voltage ($V_L = V_Z$).

 Sketch the symbol & I-V characteristics curve.



I-V characteristics curve.

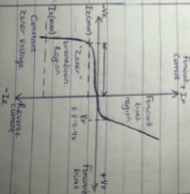

Note: Drawings show how the diode is connected in the circuit.

2. max power = 5W, $V_s = 20V$

max current (I_z) = 500mA

i. Minimum value of the series resistor to the diode

$$V_z = \frac{P_{\text{max}}}{I_z} = \frac{5}{500 \times 10^{-3}} = 10V$$

$$R_s = \frac{V_s - V_z}{I_z} = \frac{20 - 10}{500 \times 10^{-3}} = \frac{10 \times 10^3}{500} = \frac{10000}{500} = \underline{\underline{20\Omega}}$$

ii. Current across the diode at full load of 500mA

$$I_L = \frac{V_z}{R_L} = \frac{10}{500} = 0.02A \text{ or } 20mA$$

$$I_z = I_s - I_L$$

$$I_z = (500 - 20)mA = \underline{\underline{480mA}} \text{ or } \underline{\underline{0.48A}}$$

Minimum value of the series resistor to the diode = 20Ω

Current across the diode at full load of 500mA = 480mA