

a) Given $R = 100k\Omega$ $C = 5\mu f$ $L = 20mH$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-9}}}$$

$$= 100,000 \text{ rad/s} \quad \text{or} \quad 100 \text{krad/s}$$

$$\Rightarrow B = \frac{1}{RC} = \frac{1}{(100 \times 10^3)(5 \times 10^{-9})}$$

$$= \frac{1}{(100 \times 5 \times 10^{-6})}$$

$$= 2000 \text{ rad/s} \quad \text{or} \quad 2 \text{krad/s}$$

$$\Rightarrow Q = \frac{\omega_0}{B} \quad \text{from} \quad B = \frac{\omega_0}{Q}$$

$$= \frac{100 \times 10^3}{2 \times 10^3} = 50 \quad \text{[Q is dimensionless]}$$

$$\Rightarrow \omega_1 \text{ \& } \omega_2$$

$$\omega_1 = \omega_0 - B/2 \quad \text{Since } Q \gg 10$$

$$\omega_2 = \omega_0 + B/2 \quad \text{Since } Q \gg 10$$

$$\therefore \omega_1 = (100 \times 10^3) - \left(\frac{2 \times 10^3}{2}\right) = 99 \text{krad/s}$$

$$\therefore \omega_2 = (100 \times 10^3) + \left(\frac{2 \times 10^3}{2}\right) = 101 \text{krad/s}$$

a) Using the parallel admittance form

a) Using the parallel admittance formula for admittance

$$Y = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$

$$\therefore Y = \frac{1}{10} + j\omega \cdot 1 + \frac{1}{2 + j\omega 2}$$

$$\therefore Y = 0.1 + j\omega \cdot 1 + \frac{1}{2 + j\omega 2} \quad \text{Rationalizing}$$

$$\therefore Y = 0.1 + j\omega \cdot 1 + \left(\frac{1}{2 + j\omega 2}\right) \times \frac{2 - j\omega 2}{2 - j\omega 2}$$

$$\therefore Y = 0.1 + j\omega \cdot 1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

of admittance

But at resonance, the magnitude of the imaginary part = 0

ie $Y = 0$ thus ($\omega = \omega_0$)

$$\therefore 0 = \omega_0 \cdot 0.1 + \frac{-\omega_0 \cdot 2}{4 + \omega_0^2 \cdot 4}$$

$$\therefore 0 = \omega_0 \cdot 0.1 - \frac{\omega_0 \cdot 2}{4 + \omega_0^2 \cdot 4}$$

$$\therefore \frac{\omega_0 \cdot 2}{4 + \omega_0^2 \cdot 4} = 0.1 \omega_0$$

$$\therefore \omega_0 \cdot 2 = \omega_0 (0.4 + 0.4 \omega_0^2) \quad \text{d/s by } \omega_0$$

$$\therefore 2 = 0.4 + 0.4 \omega_0^2$$

$$\therefore 2 - 0.4 = 0.4 \omega_0^2$$

$$1.6 = 0.4 \omega_0^2$$

$$\therefore \frac{1.6}{0.4} = \omega_0^2$$

$$\therefore 4 = \omega_0^2 \quad \text{thus } \omega_0 = \sqrt{4} = 2 \text{ rad/s}$$

$$\therefore \omega_0 = 2 \text{ rad/s.}$$

ii) Using the series addition formula for impedance.

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

But R and C are in parallel thus we have

$$Z = j\omega 100 \times 10^{-3} + \left(20 \times \frac{1}{j\omega (0.5 \times 10^{-3})} \right) \div \left(\frac{20}{1} + \frac{1}{j\omega 0.5 \times 10^{-3}} \right)$$

5×10^{-2} Solving the brackets

$$\Rightarrow \left(\frac{20}{j\omega (0.5 \times 10^{-3})} \div \frac{20(0.5 \times 10^{-3})j\omega + 1}{j\omega (0.5 \times 10^{-3})} \right)$$

$$\Rightarrow \frac{20}{j\omega (0.5 \times 10^{-3})} \times \frac{(0.5 \times 10^{-3})j\omega}{0.01j\omega + 1}$$

thus the impedance equation becomes

$$Z = j\omega 100 \times 10^{-3} + \left(\frac{20}{j\omega (0.5 \times 10^{-3})} \times \frac{(0.5 \times 10^{-3})j\omega}{1 + 0.01j\omega} \right)$$

$$Z = j\omega 100 \times 10^{-3} + \frac{20}{1 + 0.01j\omega}$$

Rationalizing the values we get

$$Z = j\omega 100 \times 10^{-3} + \frac{20}{1 + 0.01j\omega} \times \frac{1 - 0.01j\omega}{1 - 0.01j\omega}$$

$$Z = j\omega 100 \times 10^{-3} + \frac{20 - 0.2j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

But at resonance, the magnitude of the imaginary part of impedance = 0
ie $Z = 0$ thus $(\omega = \omega_0)$

$$0 = \omega_0 100 \times 10^{-3} - \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

$$\therefore \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = \omega_0 100 \times 10^{-3}$$

$$\therefore 0.2 \omega_0 = \omega_0 (100 \times 10^{-3}) (1 + 1 \times 10^{-4} \omega_0^2)$$

$$\therefore 0.2 \omega_0 = 100 \times 10^{-3} \omega_0 + 100 \times 10^{-7} \omega_0^3 \quad \text{div by } \omega_0$$

$$0.2 = 100 \times 10^{-3} + 100 \times 10^{-7} \omega_0^2$$

$$0.2 - 100 \times 10^{-3} = 100 \times 10^{-7} \omega_0^2$$

$$1 \times 10^{-1} = 100 \times 10^{-7} \omega_0^2$$

$$\therefore \omega_0^2 = \frac{1 \times 10^{-1}}{100 \times 10^{-7}}$$

$$\omega_0^2 = 10,000$$

taking sqrt of both sides.

$$\sqrt{\omega_0^2} = \sqrt{10,000}$$

$$\therefore \omega_0 = 100 \text{ rad/s}$$