

Opeyaji Al'amin Opedapo

15/ENG04/050

Electrical/Electronic Engr.

Assignment Solution

$$1) R = 100 \text{ k}\Omega = 100 \times 10^3 \\ L = 20 \text{ mH} = 20 \times 10^{-3} \text{ H} \\ C = 5 \text{ }\mu\text{F} = 5 \times 10^{-6} \text{ F}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \\ = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-6}}} = 100000 \\ = 100 \text{ krad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{100 \times 10^3 \times 20 \times 10^{-3}} \\ = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} \\ = 2 \text{ krad/s}$$

$$\omega_1 = \omega_0 - \frac{B}{2} = 100 \times 10^3 - \frac{2 \times 10^3}{2} \\ = 99 \text{ krad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 100 \times 10^3 + \frac{2 \times 10^3}{2} \\ = 101 \text{ krad/s}$$

$$(ii) \frac{20 + 2000}{j\omega} = \frac{40000}{20j\omega + 2000} \quad \frac{40000}{20j\omega + 2000} \quad \frac{(20j\omega - 2000)}{(20j\omega - 2000)}$$

$$\frac{20 + 2000}{j\omega}$$

$$= \frac{80,000j\omega - 800,000 + 100\text{mH}}{-400j\omega - 4000000}$$

At resonance imaginary part at $\omega = 0$
 $\frac{800000}{j\omega} + j\omega (100 \times 10^{-3})$
 $-400j\omega - 4000000$

$$\frac{800000}{-400\omega - 400000} + [400 \times 10^{-3}] \omega$$

$$\Rightarrow 800000\omega + [-40\omega^2] - 400000\omega$$

$$\Rightarrow 400000 - 40\omega^2 = 0$$


$$-40\omega^2 = -400000\omega$$

$$\omega^2 = \frac{400000}{40}$$

$$\omega^2 = 10000$$

$$\omega = \sqrt{10000}$$

$$\omega = 100 \text{ rad/s}$$

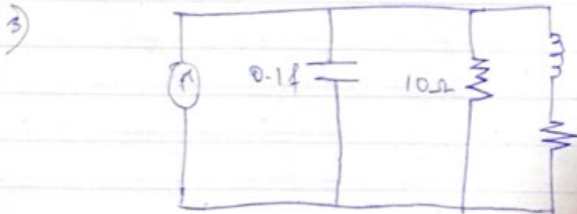

The input admittance is

$$Y = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2}$$

$$\frac{-0.1 + j\omega 0.1 + 2 - j\omega 2}{4 + 4\omega^2}$$

At resonance

$$\text{Im}(Y) = 0$$

$$\omega_0 0.1 = \frac{2\omega_0}{4 + 4\omega_0^2} = 0$$

$$\omega_0 = 2 \text{ rad/s}$$