

Q11)

a)  $R = 100k\Omega$

$L = 20mH$

$C = 5\mu F$

Calculate  $\omega_0, \omega_1, \omega_2, Q$  and  $B$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{20 \times 10^{-3} \times 5 \times 10^{-6}}}$$

$= 100k\text{rad/s}$

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC} + \left(\frac{1}{2 \times 100 \times 10^3 \times 5 \times 10^{-6}}\right)^2 + \frac{1}{20 \times 10^{-3} \times 5 \times 10^{-6}}$$

$= 100005$

$$\omega_1 = \frac{-1}{2RC} + 100005$$

$$= \frac{-1}{2 \times 100 \times 10^3 \times 5 \times 10^{-6}} + 100005$$

$$= -1000 + 100005$$

$= 99005$

$= 99k\text{rad/s}$

$$\omega_2 = \frac{1}{2RL} + \sqrt{\left(\frac{1}{2RL}\right)^2 + \frac{1}{LC}}$$

$1000 + 100005$

$10000$

$100k\text{rad/s}$

$$Q = \frac{\omega_0}{B}$$

$$B = \omega_2 - \omega_1$$

$$= (101 - 99) \text{ krad/s}$$

$$= 2 \text{ krad/s}$$

$$Q = \frac{100 \times 10^3}{2 \times 10^3}$$

$$= 50 \parallel$$


$$\omega_0 = 100 \text{ krad/s}$$

$$\omega_1 = 99 \text{ krad/s}$$

$$\omega_2 = 101 \text{ krad/s}$$

$$Q = 50$$

$$B = 2 \text{ krad/s}$$

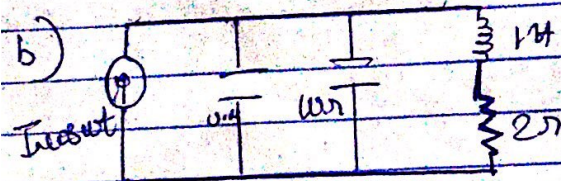

$$Y = \frac{1}{\omega} + j\omega \cdot 0.1 + \frac{1}{j\omega^2}$$

$$\frac{1}{2 + j\omega^2} = \frac{1}{2 + j\omega^2} \times \frac{1 - j\omega^2}{1 - j\omega^2}$$

$$= \frac{2 - j\omega^2}{4 + 4\omega^2}$$

(Rationalize)

$$Y = \frac{1}{\omega} + j\omega \cdot 0.1 + \frac{2 - j\omega^2}{4 + 4\omega^2}$$

$$= \frac{1}{\omega} + j\omega \cdot 0.1 + \frac{2}{4 + 4\omega^2} - \frac{2j\omega}{4 + 4\omega^2}$$

$$= \frac{1}{\omega} + \frac{2}{4 + 4\omega^2} + j\omega \cdot 0.1 - \frac{2j\omega}{4 + 4\omega^2}$$

$$= \frac{1}{\omega} + \frac{2}{4 + 4\omega^2} + j \left[ \frac{\omega \cdot 0.1 - 2\omega}{4 + 4\omega^2} \right]$$

At resonance, the imaginary part of  $Z_{in}(j\omega) = 0$

$$\frac{0.1 - 2}{4 + 4\omega_1^2} = 0$$

$$\frac{0.1 - 2}{4 + 4\omega_1^2} = 0$$

$$0.1 - 2 = 0$$

$$0.4 + 0.4\omega_1^2 = 2$$

$$0.4\omega_1^2 = 2 - 0.4$$


$$\omega_1^2 = \frac{1.6}{0.4}$$

$$\omega_1^2 = 4$$

$$\omega_0 = \sqrt{4}$$

$$\omega_0 = 2 \text{ rad/s}$$

$$\omega_1 = 2 \text{ rad/s}$$

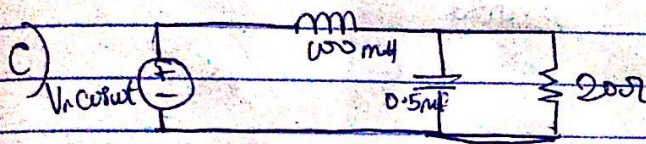

$$Z_{in}(j\omega) = j\omega(100 \times 10^{-3}) + \frac{20}{j\omega(0.5 \times 10^{-6})} + \frac{20}{1 + j\omega(0.5 \times 10^{-6})}$$

$$= j\omega(100 \times 10^{-3}) + \frac{20}{j\omega(0.5 \times 10^{-6})} + \frac{20}{0.5 \times 10^{-6} j\omega + 1}$$

$$= j\omega(100 \times 10^{-3}) + \frac{20}{j\omega(0.5 \times 10^{-6})} + \frac{20 \times 0.5 \times 10^{-6}}{0.5 \times 10^{-6} j\omega + 1}$$

$$= j\omega(100 \times 10^{-3}) + \frac{20}{0.01j\omega + 1}$$

$$\frac{20}{0.01j\omega + 1} \times \frac{0.01j\omega - 1}{0.01j\omega - 1} \quad (\text{Rationalize})$$

$$\frac{0.2j\omega - 20}{1 \times 10^{-4}\omega^2 + 1} = \frac{-0.2j\omega + 20}{1 \times 10^{-4}\omega^2 + 1}$$

$$= j\omega(100 \times 10^{-3}) + \frac{20}{1 \times 10^{-4}\omega^2 + 1} + \frac{-0.2j\omega}{1 \times 10^{-4}\omega^2 + 1}$$

$$= \frac{20}{1 \times 10^{-4}\omega^2 + 1} + \frac{-0.2j\omega}{1 \times 10^{-4}\omega^2 + 1} + j\omega(100 \times 10^{-3})$$

$$\frac{2 + 2s}{1 \times 10^4 s^2 + 1} + j \left[ \frac{-0.2 \omega}{1 \times 10^{-4} \omega^2 + 1} + \omega \times 100 \times 10^{-3} \right]$$

At resonance (imaginary part is 0)

$$-0.2 \omega_0 + \omega_0 \times 100 \times 10^{-3} = 0$$

$$\frac{1 \times 10^{-4} \omega_0^2 + 1}{1 \times 10^{-4} \omega_0^2 + 1}$$

$$\omega_0 \times 100 \times 10^{-3} - 0.2 \omega_0 = 0$$

$$\frac{1 \times 10^{-4} \omega_0^2 + 1}{1 \times 10^{-4} \omega_0^2 + 1}$$

Divide by  $\omega_0$

$$\frac{\omega_0 \times 100 \times 10^{-3}}{\omega_0} = \frac{0.2 \omega_0}{1 \times 10^{-4} \omega_0^2 + 1} \times \frac{1}{\omega_0} = 0$$

$$\omega_0 \times 10^{-3} = \frac{0.2}{1 \times 10^{-4} \omega_0^2 + 1}$$

$$1 \times 10^{-5} \omega_0^2 + \omega_0 \times 10^{-3} = 0.2$$

$$\omega_0^2 = \frac{0.2 - \omega_0 \times 10^{-3}}{1 \times 10^{-5}}$$

$$\omega_0^2 = \frac{0.1}{1 \times 10^{-6}} = 10,000$$

$$\omega_0 = \sqrt{10,000}$$

$$= 100 \text{ rad/s}$$