

1.) $R = 100\text{k}\Omega$, $L = 20\text{mH}$, $C = 5\text{mF}$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2 \times 10^{-3})(5 \times 10^{-4})}} = \frac{1}{\sqrt{1 \times 10^{-6}}} = 100000 \text{ rad/s}$$

$$\omega_0 = 100\text{k rad/s}$$

$$Q = \frac{R}{\omega_0 L} = \frac{100 \times 10^3}{(100 \times 10^3)(20 \times 10^{-3})} = \frac{1}{20 \times 10^{-3}} = 50$$

$$Q = 50$$

$$B = \frac{\omega_0}{Q} = \frac{100 \times 10^3}{50} = 2000 \approx 2 \text{ krad/s}$$


$$Q > 10, \omega_1 = \frac{\omega_0 - B}{2} = \frac{100 \times 10^3 - 2000}{2} = 100 \times 10^3 - 1000$$

$$\omega_1 = 99000 \approx 99 \text{ krad/s}$$

$$\omega_2 = \frac{\omega_0 + B}{2} = \frac{100 \times 10^3 + 2000}{2} = 100 \times 10^3 + 1000$$

$$\omega_2 = 101 \text{ krad/s}$$

2.)

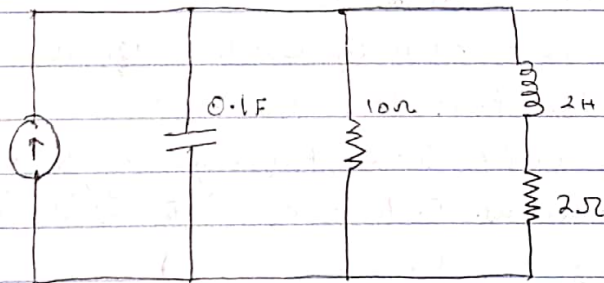

$$Y = \frac{1}{I_0} + \frac{j\omega \cdot 0.1}{2 + j\omega 2} = 0.1 + \frac{j\omega \cdot 0.1}{2 + j\omega 2}$$

$$\frac{1}{2 + j\omega 2} = \frac{1}{2 + j\omega 2} \times \frac{2 - j\omega 2}{2 - j\omega 2} = \frac{2 - j\omega 2}{4 + \omega^2}$$

$$Y = 0.1 + \frac{j\omega \cdot 0.1}{4 + \omega^2} + \frac{2 - j\omega 2}{4 + \omega^2} = 0.1 + \frac{j\omega \cdot 0.1 + 2 - j\omega 2}{4 + \omega^2}$$

$$Y = 0.1 + \frac{2}{4 + \omega^2} + \frac{j\omega \cdot 0.1 - \omega 2}{4 + \omega^2} = \frac{0.1 + 2}{4 + \omega^2} + j \left(\frac{\omega \cdot 0.1 - \omega 2}{4 + \omega^2} \right)$$

At Resonance, $\text{Im}(Y) = 0$

$$\text{Therefore, } \frac{\omega \cdot 0.1 - \omega 2}{4 + \omega^2} = 0$$

~~W = 1~~

$$0.1 = \frac{2}{4 + 4\omega^2} = 0$$

$$0.1 = \frac{2}{4 + 4\omega^2}$$

$$0.4 + 0.4\omega^2 = 2$$


$$0.4\omega^2 = 1.6$$

$$\omega^2 = 0.4 \times 10$$

$$\omega^2 = 4$$

$$\omega = \sqrt{4} = 2 \text{ rad/s}$$

②

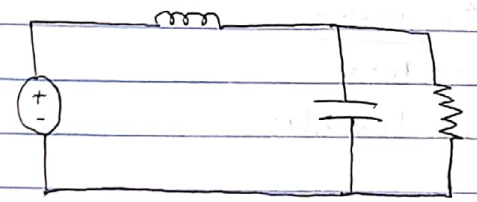

$$Z = j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \parallel \left(\frac{20 + 1}{0.5 \times 10^{-3} j\omega} \right) \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \parallel \left(\frac{0.01 j\omega + 1}{0.5 \times 10^{-3} j\omega} \right) \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{j\omega(0.5 \times 10^{-3})} \times \left(\frac{j\omega(0.5 \times 10^{-3})}{0.01 j\omega + 1} \right) \right)$$

$$= j\omega(100 \times 10^{-3}) + \left(\frac{20}{0.01 j\omega + 1} \right)$$

$$\frac{20}{j\omega \cdot 1 + 1} = \frac{20}{0.01 j\omega + 1} \times \frac{0.01 j\omega - 1}{0.01 j\omega - 1}$$

$$= \frac{j\omega \cdot 0.2 - 20}{-1 \times 10^{-4} \omega^2 - 1} = \frac{-20 + j\omega \cdot 0.2}{-1 \times 10^{-4} \omega^2 - 1}$$

$$Z = j\omega(100 \times 10^{-3}) + \frac{20}{1 \times 10^{-4} j\omega^2 + 1} - \frac{0.2 j\omega}{1 + 1 \times 10^{-4} \omega^2} = \frac{20}{1 \times 10^{-4} \omega^2} + j\omega(100 \times 10^{-3}) - \frac{0.2 j\omega}{1 + 1 \times 10^{-4} \omega^2}$$

$$Z = \frac{20}{1 \times 10^{-4} j\omega^2} + j(\omega(100 \times 10^{-3}) - \frac{0.2 \omega}{1 + 1 \times 10^{-4} \omega^2})$$

At resonance, the imaginary part is 0

$$\therefore 100(100 \times 10^{-3}) = \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2} = 0$$

$$\omega_0 (100 \times 10^{-3}) = \frac{0.2 \omega_0}{1 + 1 \times 10^{-4} \omega_0^2}$$

$$100 \times 10^{-2} (1 + 1 \times 10^{-4} \omega_0^2) = 0.2$$

$$100 \times 10^{-2} + 1 \times 10^{-5} \omega_0^2 = 0.2$$

$$1 \times 10^{-5} \omega_0^2 = 0.2 - 100 \times 10^{-3} = 0.1$$

$$1 \times 10^{-5} \omega_0^2 = 0.1$$

$$\omega_0^2 = \frac{0.1}{10^{-5}}$$

$$\omega_0^2 = \frac{0.1}{10^{-5}}$$

$$\omega_0^2 = 10000$$

$$\omega_0 = \sqrt{10000}$$

$$\omega_0 = 100 \text{ rad/s}$$