

NAME: ITUA EHIAGHE E




MATRIC NO: 181ENGG011012

DEPT: CHEMICAL ENGINEERING

COURSE CODE & TITLE: ENGI 222 BASIC ELECTRICAL ENGINEERING

1- Zener diode as a voltage regulator

The zener diode is like a general purpose signal diode. When biased in the forward direction, it behaves just like a normal signal diode, but when a reverse voltage is applied to it, the voltage remains constant for a wide range of current. There is a limit for reverse voltage, cause it will continue to increase until it reaches the breakdown voltage. (Avalanche Breakdown region). This ability to control itself (have a constant voltage in the reverse region, irrespective of the current flowing) can be used to great effect to regulate or stabilize a voltage source against supply or load variations. The fact that the voltage across the diode in the breakdown region is almost constant turns out to be an important application of the zener diode as a voltage regulator

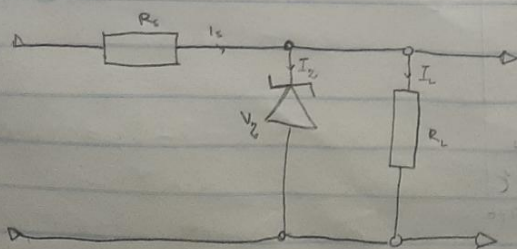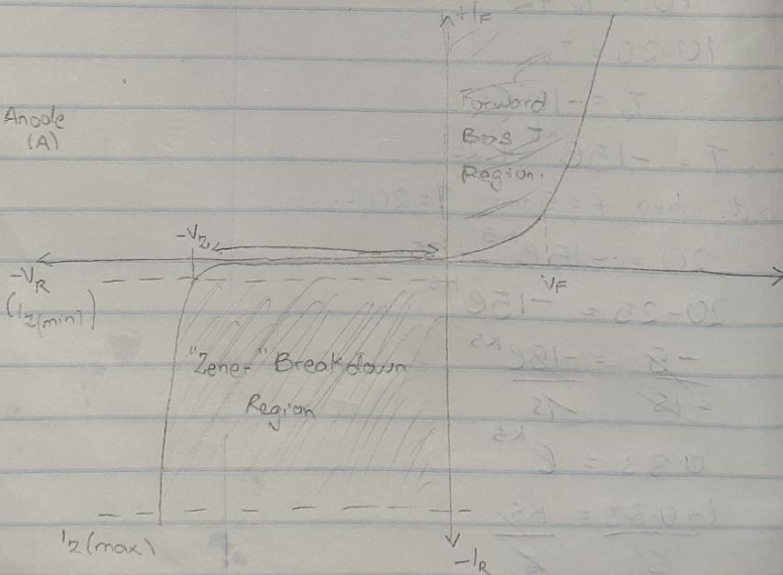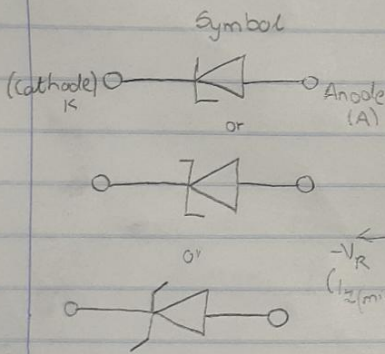

Power of Zener  
 $P = BW$

$I_{max} = 500mA$

$V_S = 24V$

$= \frac{24 \times 2}{\pi}$

$R_S = \frac{V_S - V_Z}{I_Z}$

$I_Z = 500mA$

$V_S = 12.732$

$V_Z = ?$

but  $P = I V_Z$

$\frac{P}{I} = V_Z$

$\therefore V_Z = \frac{P}{I}$

$V_Z = 10V$

$R_S = \frac{12.732 - 10}{0.5}$

$R_S = 5.464 \Omega$

Then  $I_0 = I_Z$

$I_L = \frac{V_Z}{R_L}$

$R_L = 500 \Omega$

$I_L = \frac{10V}{500}$

$I_Z = 500mA$

Power of Zener diode

$$P = 5W$$

$$I_{max} = 500mA$$

$$V_s = \frac{2 \times V_{max}}{\pi}$$

$$= \frac{2 \times 20}{\pi} = 12.732V$$

$$R_s = \frac{V_s - V_z}{I_z}$$

$$\& I_z = 500mA$$

$$V_s = 12.732V$$

$$V_z = ?$$

$$\text{but } P = I V_z$$

$$\frac{P}{I} = V_z$$

$$\therefore V_z = \frac{5W}{500mA} = 10V$$

$$V_z = 10V$$

$$R_s = \frac{(12.732 - 10)V}{500mA}$$

$$R_s = \underline{\underline{5.464\Omega}}$$

$$\text{Then } I_o = I_z + I_L$$

$$I_L = \frac{V_z}{R_L}$$

$$R_L = 500\Omega$$

$$I_L = \frac{10V}{500\Omega} = 0.02A = 20mA$$

$$I_z = 500mA - 20mA = \underline{\underline{480mA}}$$